

**ROCHESTER INSTITUTE OF TECHNOLOGY  
MICROELECTRONIC ENGINEERING**

# Feedback in Electronic Circuits

**Dr. Lynn Fuller**

Webpage: <http://people.rit.edu/lffeee/>

Microelectronic Engineering

Rochester Institute of Technology


82 Lomb Memorial Drive

Rochester, NY 14623-5604

Tel (585) 475-2035

Email: [Lynn.Fuller@rit.edu](mailto:Lynn.Fuller@rit.edu)

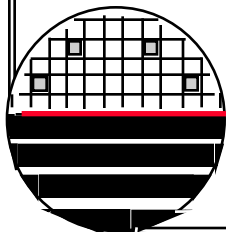MicroE webpage: <http://www.microe.rit.edu>



*OUTLINE*

Introduction

Advantages of Feedback

Generalized Approach

Voltage Shunt Feedback

Voltage Series Feedback

Current Shunt Feedback


Current Series Feedback


Examples for each

References

Homework Questions

Old Exam Questions

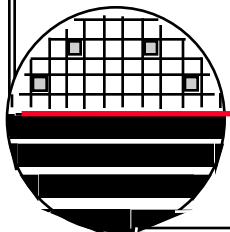

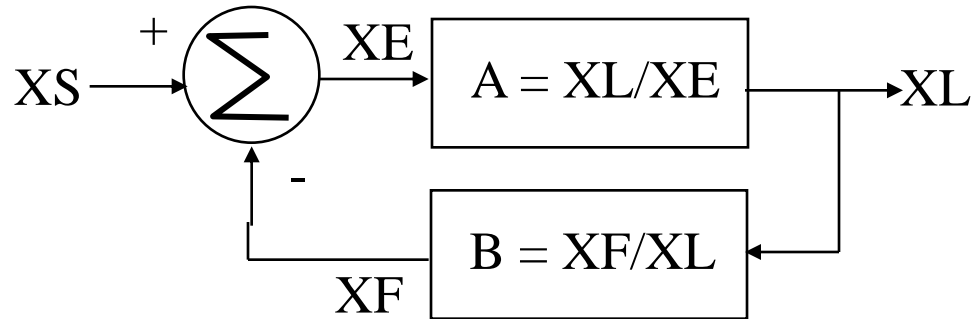*INTRODUCTION*

Consider the feedback amplifier shown.

$$\begin{aligned} XL &= A XE = A (XS - XF) = A (XS - BXL) \\ &= A XS - A B XL \text{ or } XL(1+AB)=A XS \end{aligned}$$

$$A_f = XL/XS = A/(1+AB)$$

In this analysis, A is defined as the gain of the amplifier without feedback, known as the open loop gain, B is the gain of the feedback network,  $T = -AB$  is known as the loop gain, and  $A_f$  is the gain of the amplifier with feedback, known as the closed loop gain.


## INTRODUCTION

**NEGATIVE FEEDBACK:** If the loop gain is negative for any circuit then that circuit has negative feedback. For negative feedback the closed loop gain is:

$$A_f = \frac{A}{1 + AB}$$

**POSITIVE FEEDBACK:** If the loop gain is positive for any circuit then that circuit has positive feedback.  $A_f = A / (1 - AB)$ . Note that if  $AB = 1$  the gain  $A_f = \text{infinity}$  and the circuit will oscillate. That is no input is needed. Which is useful if you want an oscillator.

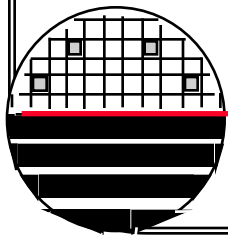We will continue by discussing only negative feedback.



## NEGATIVE FEEDBACK DECREASES SENSITIVITY

Decrease in Sensitivity – Suppose A changes by x%. How much would Af change?  
To answer this question lets compute the sensitivity of Af with respect to A:

Sensitivity symbol  
(not integral)

$$S_A^{Af} = \frac{\text{Incremental change in Af}}{\text{Incremental change in A}} = \frac{\Delta Af / Af}{\Delta A / A}$$

$$\Delta Af = \frac{\delta Af}{\delta A} \Delta A = \frac{\delta \left( \frac{A}{1+AB} \right)}{\delta A} \Delta A = \frac{1}{(1+AB)^2} \Delta A$$


$$\frac{\Delta Af}{Af} = \frac{\frac{1}{(1+AB)^2} \Delta A}{\frac{A}{1+AB}} = \frac{1}{(1+AB)^2} \frac{\Delta A}{A} = \frac{1}{1+AB} \frac{\Delta A}{A}$$

$$S_A^{Af} = \frac{1}{1+AB}$$

So we see that the sensitivity of the gain Af to changes in gain A is less than 1 which is an improvement over an amplifier without feedback.

***NEGATIVE FEEDBACK DECREASES SENSITIVITY***

Decrease in Sensitivity –

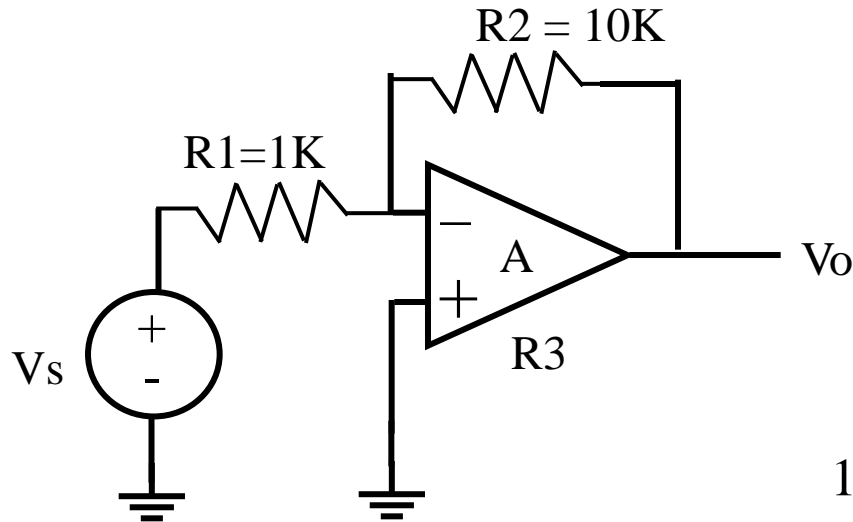


The gain without feedback,  $A$ , is large but not precise (may change from one op amp to the next).

The gain with feedback,  $A_f$ , is  $-R_2/R_1 = -10$  which is precise (and lower than  $A$ )
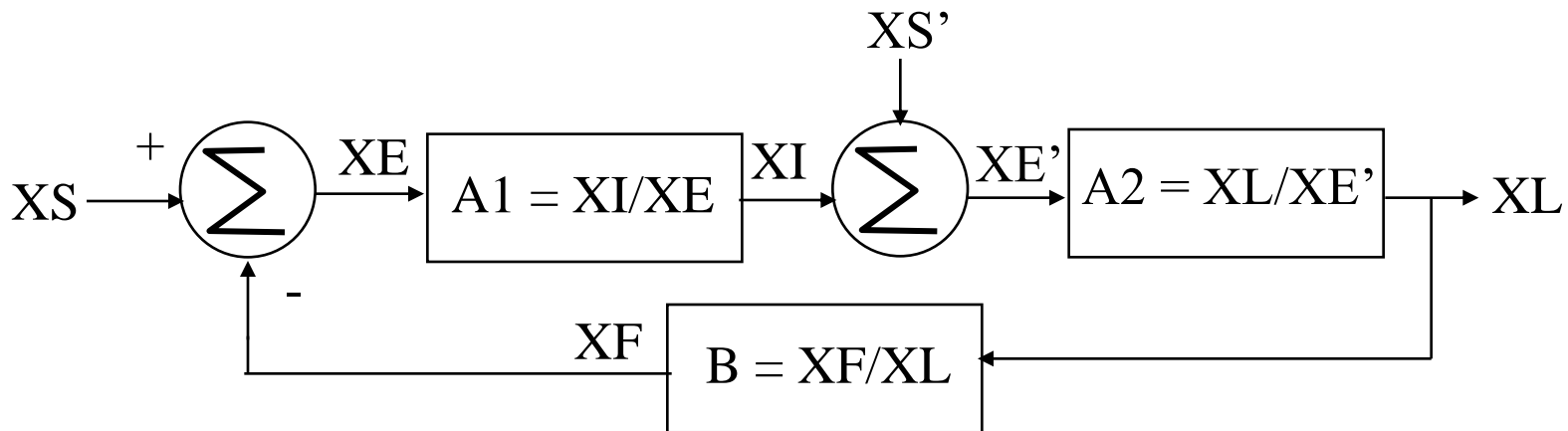
## *NEGATIVE FEEDBACK DECREASES DISTORTION*

**Reduction in Distortion:** Suppose an amplifier consists of two stages,  $A_1$  and  $A_2$  such that  $A = A_1 A_2$  and that distortion is modeled as the addition of an unwanted signal  $X_{S'}$  as shown in the figure below.



$$X_L = A_2 X_{E'} = A_2 (X_I + X_{S'})$$

$$X_L = A_2(A_1 X_E + X_{S'}) = A_2 (A_1(X_S - X_F) + X_{S'})$$

$$X_L = A_2(A_1(X_S - B X_L) + X_{S'})$$

## *NEGATIVE FEEDBACK DECREASES DISTORTION*

$$X_L = A_2 X_{E'} = A_2 (X_I + X_{S'})$$

$$X_L = A_2 (A_1 X_E + X_{S'}) = A_2 (A_1 (X_S - X_F) + X_{S'})$$

$$X_L = A_2 (A_1 (X_S - B X_L) + X_{S'})$$


$$X_L = A_2 A_1 X_S - A_2 A_1 B X_L + A_2 X_{S'}$$

$$X_L = \frac{A_1 A_2}{(1 + A_1 A_2 B)} \left[ X_S + \frac{X_{S'}}{A_1} \right]$$

If  $X_{S'}$  were some unwanted signal, say distortion, we could decrease the effect of  $X_{S'}$  by introducing it as close as possible to the output of the amplifier. In other words make  $A$ , as large as possible, use feedback to achieve the desired gain and also reduce distortion introduced after  $A_1$ . In many amplifiers distortion is introduced in the output stage, (crossover, etc.)




# NEGATIVE FEEDBACK DECREASES DISTORTION

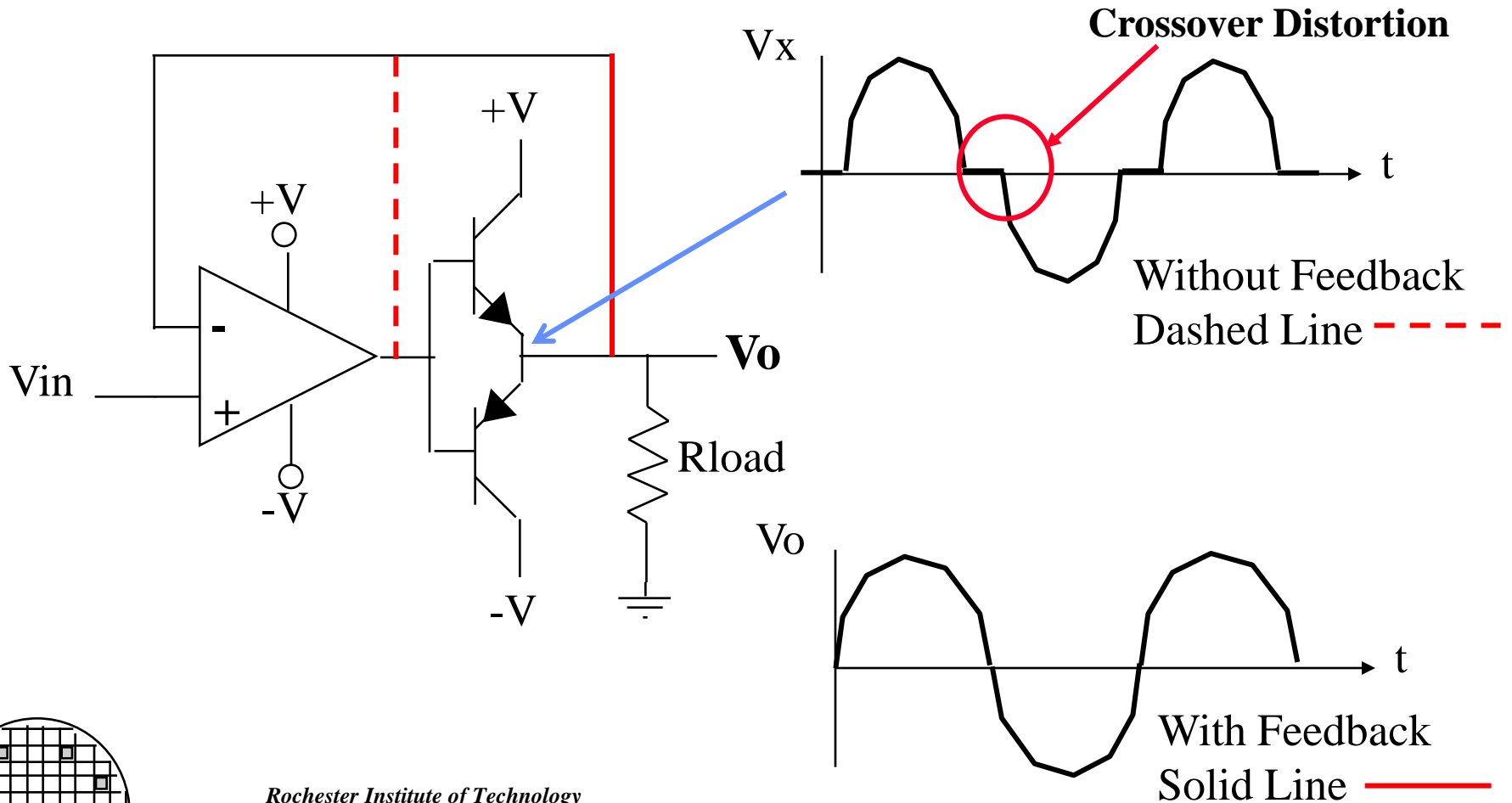

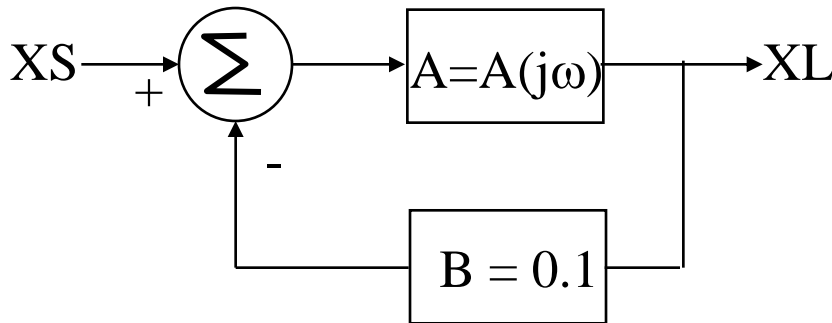**NEGATIVE FEEDBACK INCREASES BANDWIDTH**

Bandwidth is the frequency range where the amplifier gain is flat.



$$A(j\omega) = \frac{1000}{1 + j f/f_1}$$


Let  $f_1 = 1000 \text{ hz}$

$A = 1000 = 60\text{dB}$

40dB

$A_f = 10 = 20\text{dB}$


0dB

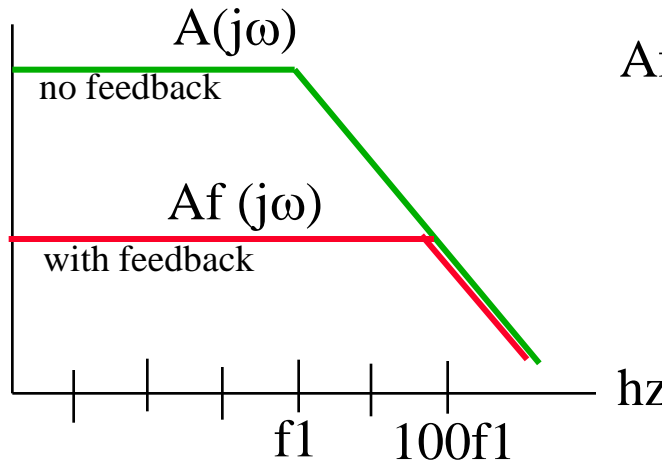

$$A_f(j\omega) = \frac{A}{1+AB} = \frac{\frac{1000}{1+jf/f_1}}{1 + \frac{100}{1+jf/f_1}}$$

$$= \frac{1000}{1+jf/f_1 + 100}$$
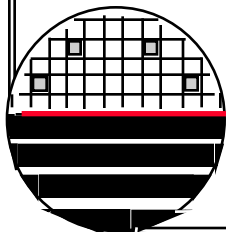
$$A_f(j\omega) = \frac{1000}{101} \frac{1}{1+jf/(101 f_1)}$$




## ***SUMMARY OF ADVANTAGES OF NEGATIVE FEEDBACK***

**Negative feedback reduces the gain of an amplifier compared to the gain without feedback:**

**However, an amplifier with negative feedback has the following improvements**

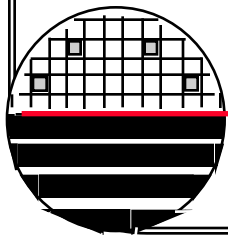
1. The gain with feedback is less sensitive to the amplifier gain value itself
2. Feedback can reduce unwanted distortion.
3. Feedback increases the bandwidth



# REVIEW OF TWO PORT EQUIVALENT CIRCUITS


$$I_1 = y_{11} V_1 + y_{12} V_2$$

$$I_2 = y_{21} V_1 + y_{22} V_2$$

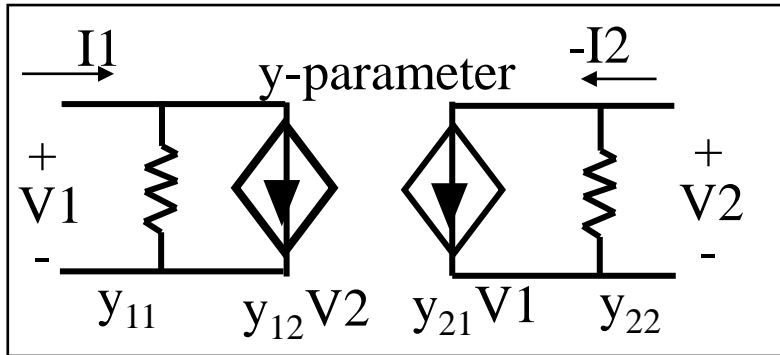


$$I_1 = g_{11} V_1 + g_{12} V_2$$

$$I_2 = g_{21} V_1 + g_{22} V_2$$

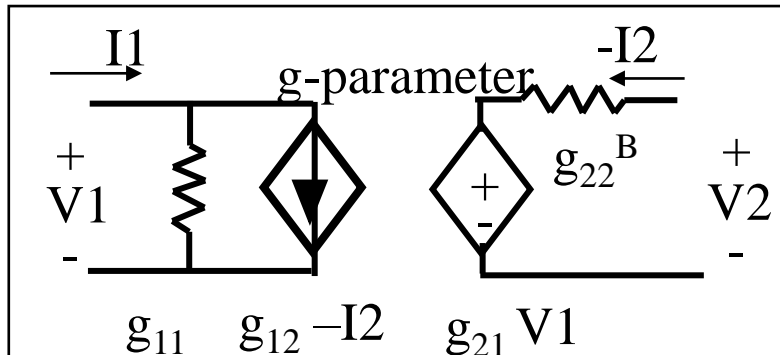


$$V_1 = h_{11} I_1 + h_{12} V_2$$

$$I_2 = h_{21} I_1 + h_{22} V_2$$

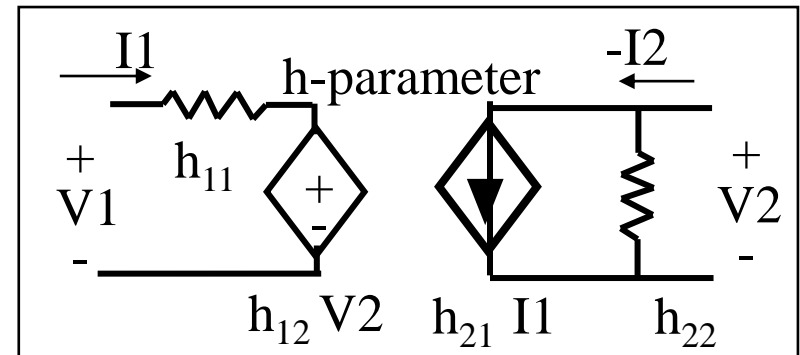

$$V_1 = z_{11} I_1 + z_{12} V_2$$

$$I_2 = z_{21} I_1 + z_{22} V_2$$

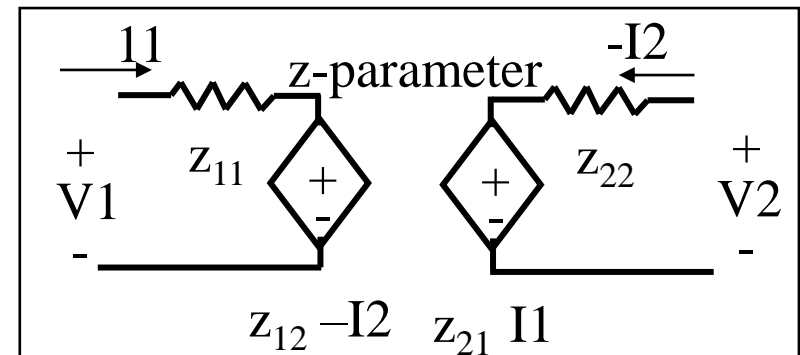


## *GENERALIZED APPROACH*





### **A Generalized Approach for the Analysis of Feedback Amplifiers:**

The components of a feedback amplifier are:

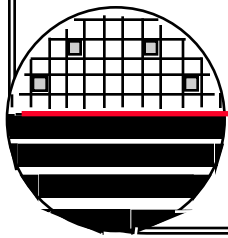1. An Amplifier (y,g,h,z parameter two-port model)
2. A Feedback Network (y,g,h,z parameter two-port model)
3. A Sampling Network (series or parallel connections)
4. A Mixing or Comparing Network (connections)
5. A Load (a resistor)
6. A Source (Thevenin or Norton equivalent)







# AMPLIFIER MODELS

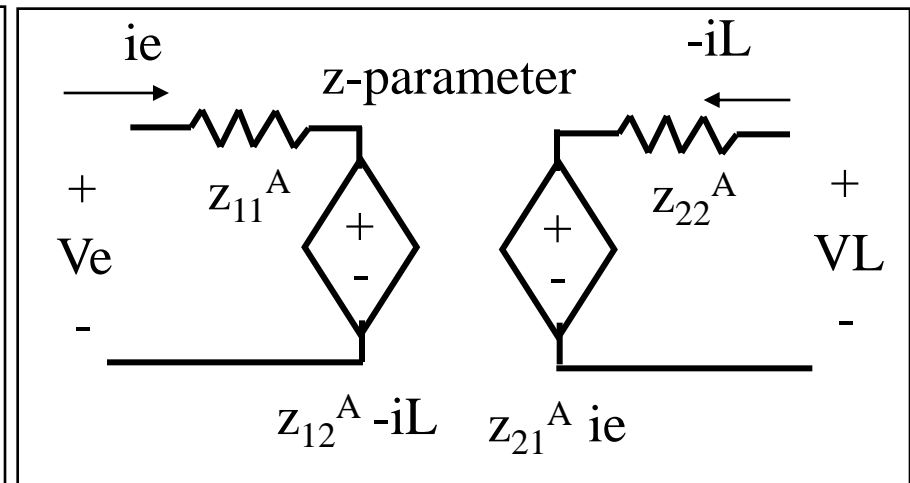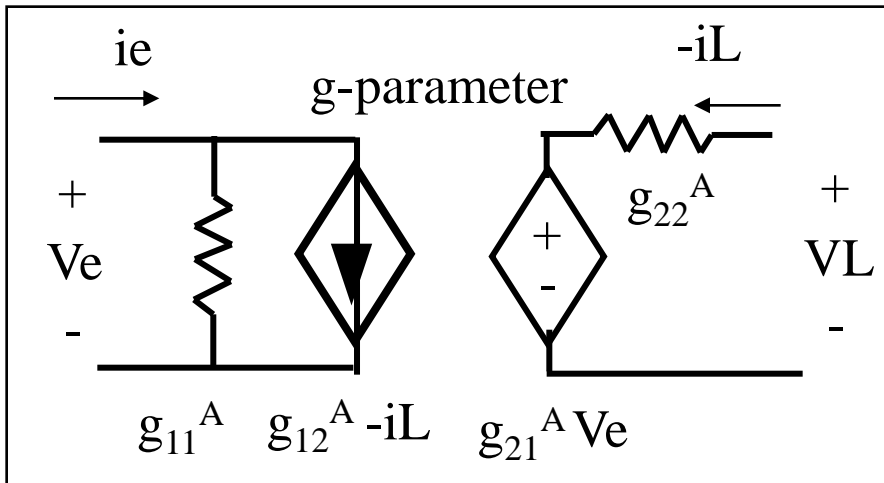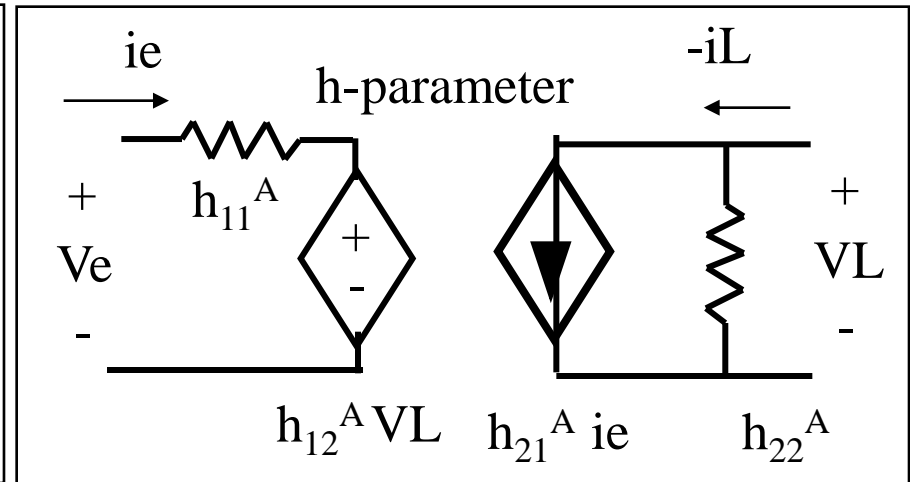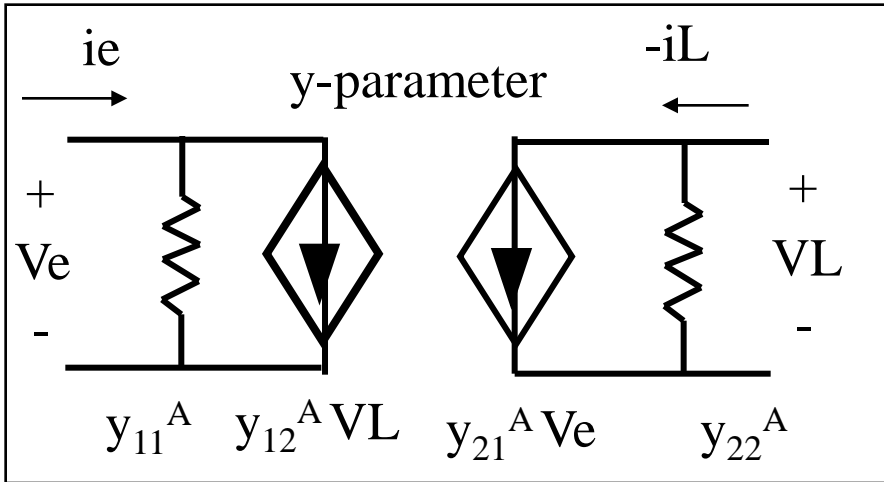

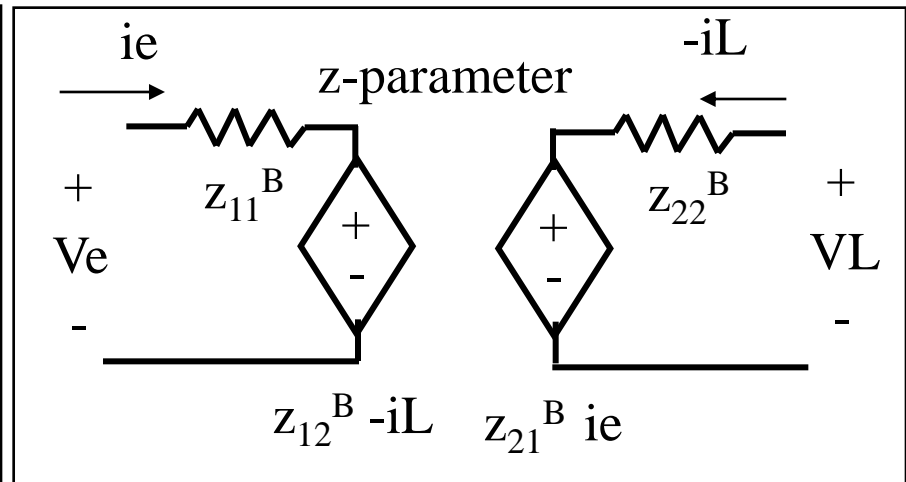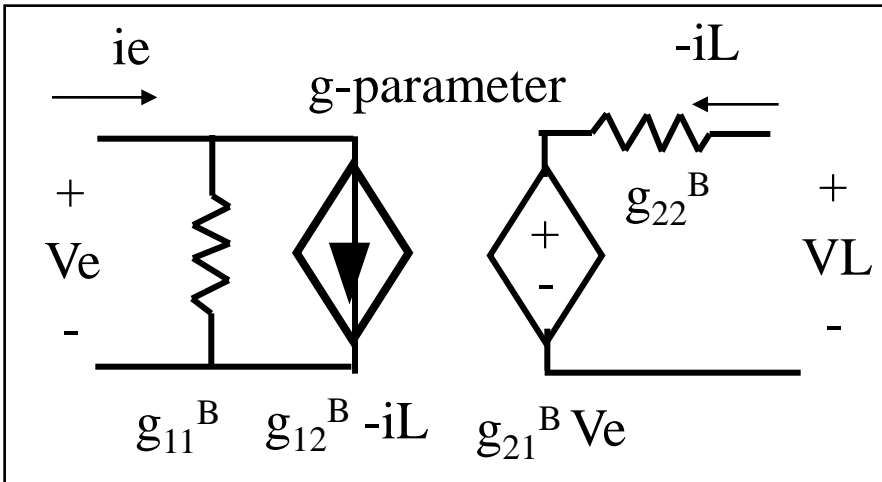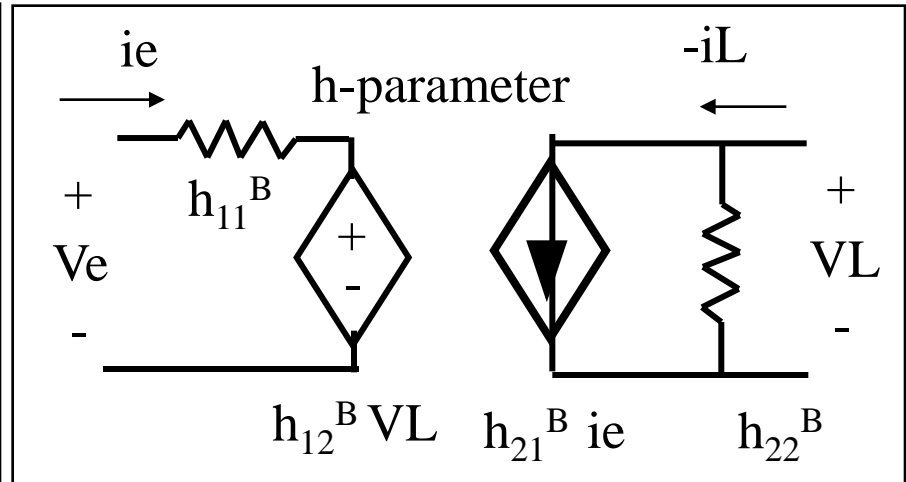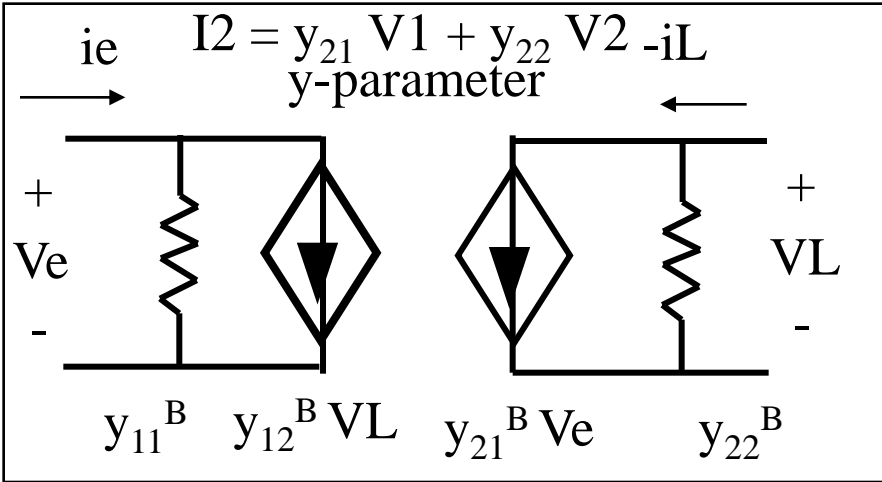**FEEDBACK NETWORK MODELS**


~~$I1 = y_{11} V1 + y_{12} V2$~~

$I2 = y_{21} V1 + y_{22} V2$   
y-parameter




## *SAMPLING, MIXING, LOAD, SOURCE*

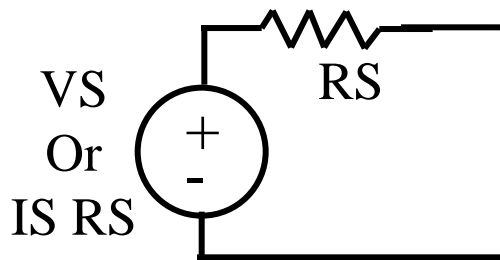3. The sampling network consists of the wires used to connect the feedback network to the amplifier. Sampling can be done in parallel (voltage sampling) or in series (current sampling) with the load.
4. The mixing network consists of the wires used to connect the feedback network to the amplifier. Mixing can be in parallel (shunt) or series with the source.
5. The load is a resistor connected to the output of the amplifier.
6. The source is represented by its Thevinin or Norton equivalent circuit.



Thevinin

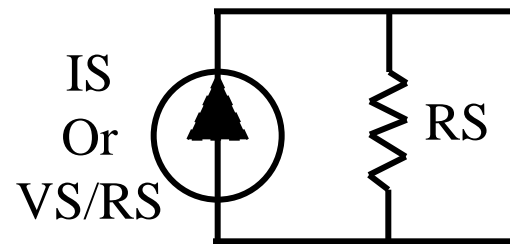


Norton



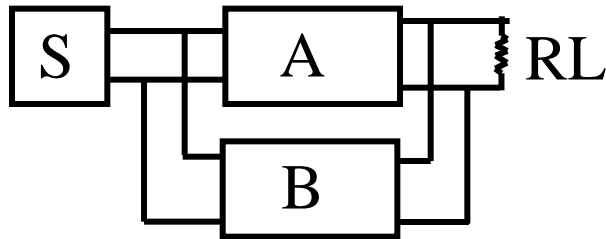
## FEEDBACK AMPLIFIER CONFIGURATIONS

Since A and B are being considered as two-port networks there are four ways in which these two-port networks can be connected to provide feedback as shown below:


Voltage-Shunt Feedback  
(use  $y$  parameters)



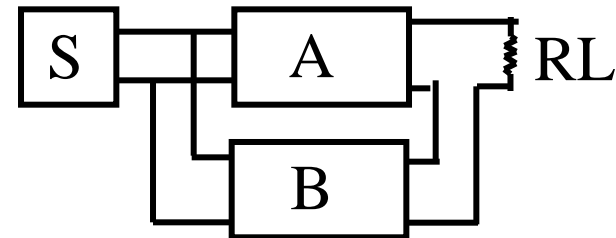
Current-Shunt Feedback  
(use  $g$  parameters)



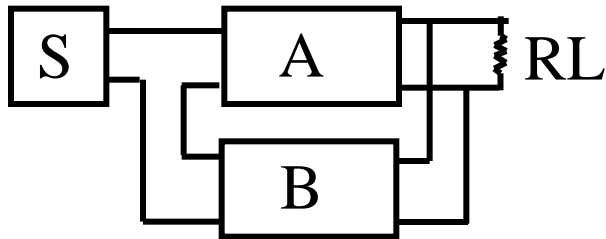Voltage-Series Feedback  
(use  $h$  parameters)




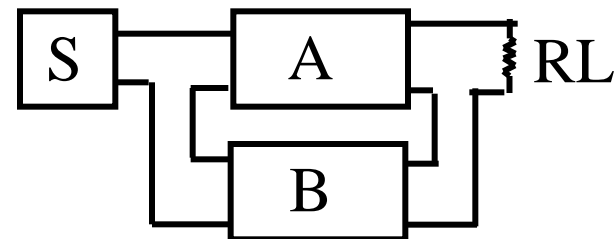Current-Series Feedback  
(use  $z$  parameters)



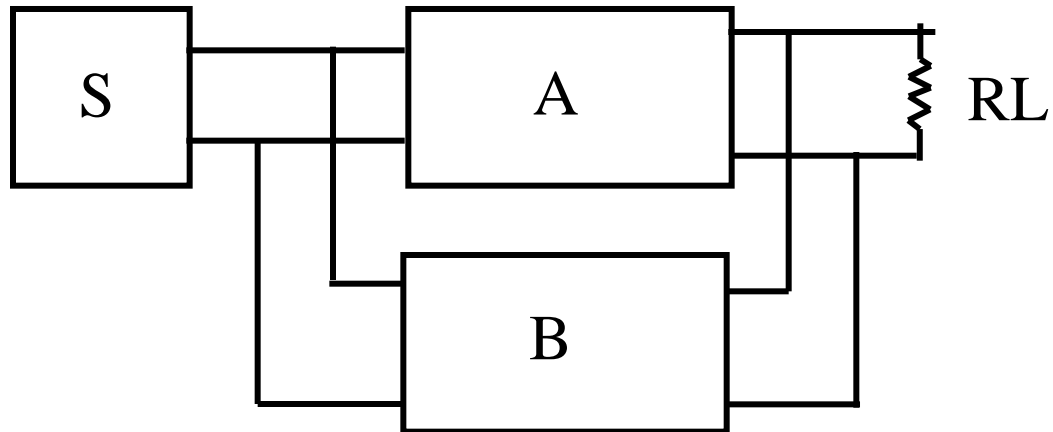
## VOLTAGE-SHUNT FEEDBACK

Since **voltage – shunt** feedback implies parallel connections for the sampling and mixing networks. We will select, y-parameter two port models and a Norton model for the source. The resulting equivalent circuit can be greatly simplified by combining parallel current sources and parallel conductances.



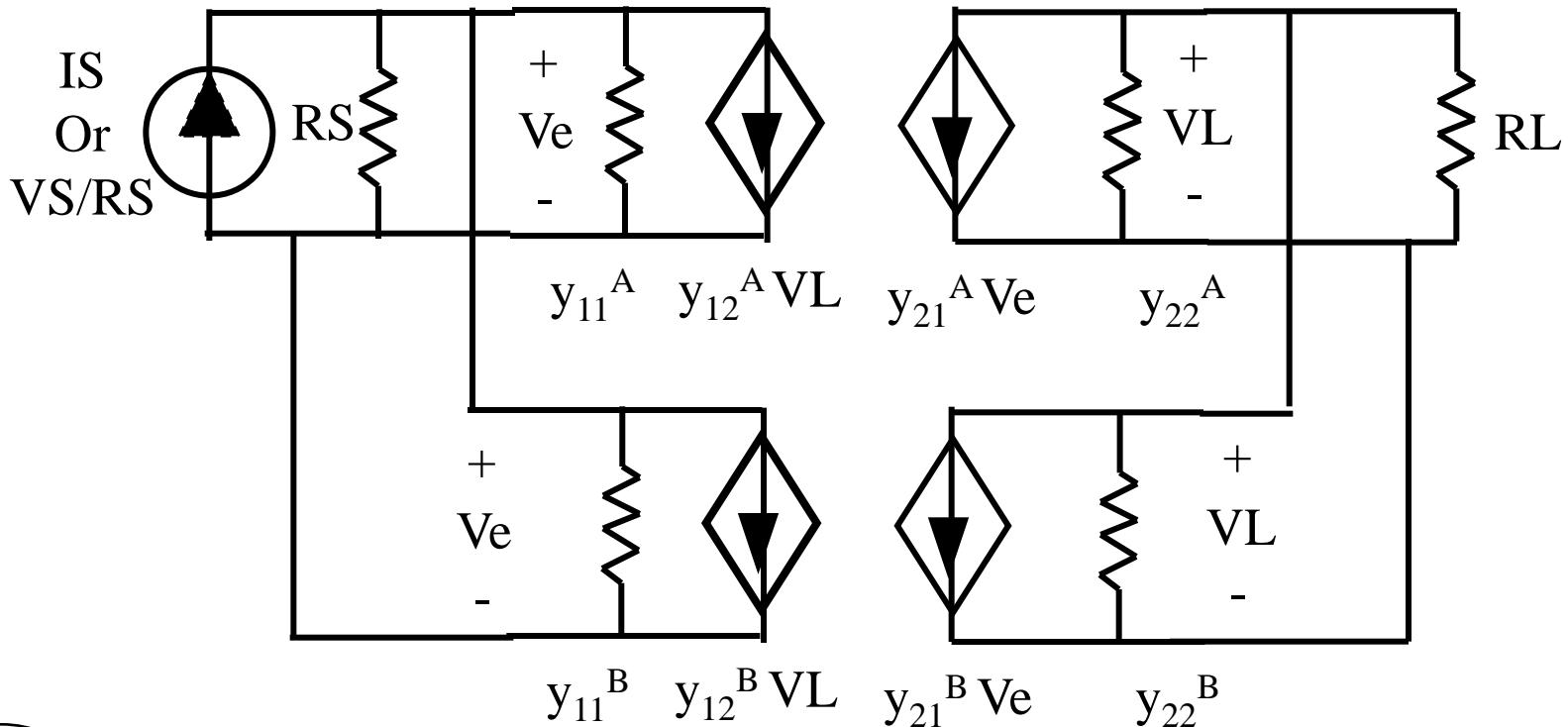
# VOLTAGE-SHUNT FEEDBACK

Select y-parameters and Norton equivalent circuits for voltage-shunt feedback:


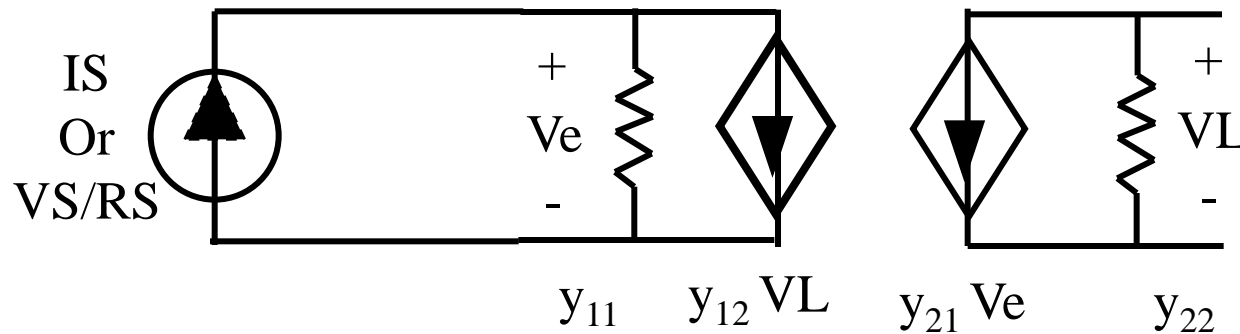
## SIMPLIFIED VOLTAGE-SHUNT FEEDBACK

From the previous page we combine current sources in parallel and conductances in parallel. (the equivalent circuit is simplified)




$$y_{11} = y_{11}^A + y_{11}^B + 1/R_s$$

$$y_{22} = y_{22}^A + y_{22}^B + 1/R_L$$

$$y_{12} = y_{12}^A + y_{12}^B$$

$$y_{21} = y_{21}^A + y_{21}^B$$

## ANALYSIS OF VOLTAGE-SHUNT FEEDBACK

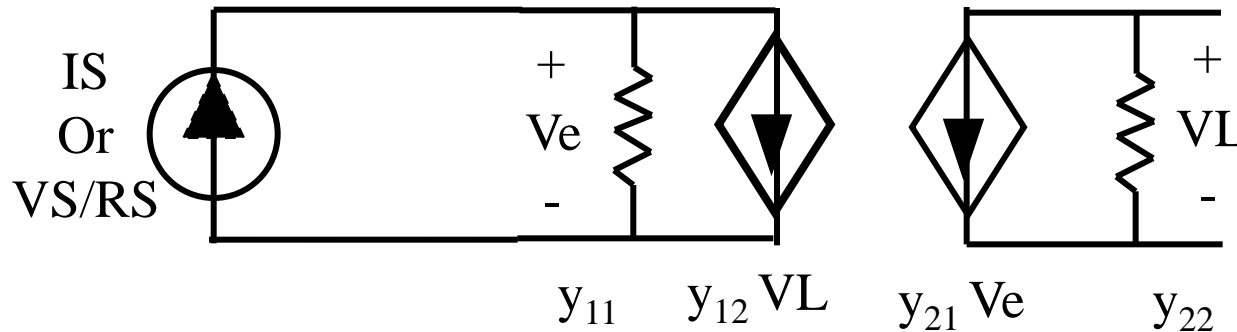

KCL gives

$$I_S = y_{11} V_e + y_{12} V_L$$

$$0 = y_{21} V_e + y_{22} V_L \text{ this eqn gives } V_e = -y_{22} V_L / y_{21}$$

$$I_S = y_{11} (-y_{22} V_L / y_{21}) + y_{12} V_L = [-y_{11} y_{22} / y_{21} + y_{12}] V_L$$

$$V_L / I_S = \frac{1}{[y_{12} - y_{11} y_{22} / y_{21}]}$$

$$V_L / I_S = \frac{\frac{-y_{21}}{y_{11} y_{22}}}{1 + \frac{-y_{12} y_{21}}{y_{11} y_{22}}}$$

$$\Rightarrow A_f = \frac{A}{1 + AB}$$

## *ANALYSIS OF VOLTAGE-SHUNT FEEDBACK*

$A_{Rf} = VL/IS$  is the gain with feedback : Notice that the gain with feedback,  $A_f$ , for voltage-shunt feedback has units of ohms ( $\Omega$ ).  $A_f$  is not a voltage gain, it is not a current gain, it is a transresistance.

Suppose we wanted a voltage gain instead of transresistance. Recall that  $IS$  came from the Norton equivalent of the source.

Thus  $VS = IS RS$   $A_{Rf} = VL/IS$

$$A_{Vf} = VL/VS = (VL/IS) (1/RS) = A_{Rf} (1/RS)$$

$$A_{If} = IL/VS = (VL/IS) (1/RL) = A_{Rf} (1/RL)$$

## *ANALYSIS OF VOLTAGE-SHUNT FEEDBACK*

$A_R = \frac{-y_{21}}{y_{11}y_{22}}$  is the gain of the feedback amplifier with the feedback disabled.  $A_R$  is not the gain of the feedback amplifier with the feedback disconnected.

$$A_{Rf} = \frac{\frac{-y_{21}}{y_{11}y_{22}}}{1 + \frac{-y_{12}y_{21}}{y_{11}y_{22}}} \bigg|_{y_{12} = 0} = \frac{-y_{21}}{y_{11}y_{22}}$$

## ANALYSIS OF VOLTAGE-SHUNT FEEDBACK

$B = y_{12}$ : this quantity is very important for estimating the gain of the amplifier with feedback

$$A_{Rf} \sim \frac{1}{B} = \frac{1}{y_{12}}$$

This approximation is good as  $y_{21}$  goes to infinity

$$A_{Rf} = \frac{\frac{-y_{21}}{y_{11}y_{22}}}{1 + \frac{-y_{12}y_{21}}{y_{11}y_{22}}}$$


Exact gain

$$T = -BA = \frac{y_{12}y_{21}}{y_{11}y_{22}} \quad \text{is the loop gain } T$$



## ANALYSIS OF VOLTAGE-SHUNT FEEDBACK

Input Admittance,  $Y_{If} = IS/Ve$

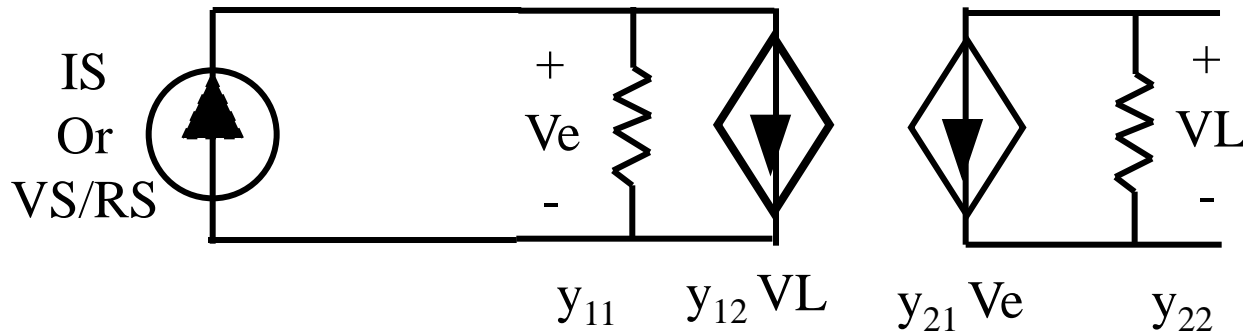

$$I_S = y_{11} V_e + y_{12} V_L$$


$$0 = y_{21} V_e + y_{22} V_L \quad \longrightarrow \quad V_L = -y_{21}/y_{22} V_e$$

$$I_S = y_{11} V_e + y_{12} \left[ -y_{21}/y_{22} V_e \right] = y_{11} V_e \left[ 1 - \frac{y_{12}y_{21}}{y_{11}y_{22}} \right]$$

$$Y_{If} = I_S/V_e = y_{11} \left[ 1 - \frac{y_{12}y_{21}}{y_{11}y_{22}} \right] = y_{11} \left[ 1 - T \right]$$

# ANALYSIS OF VOLTAGE-SHUNT FEEDBACK

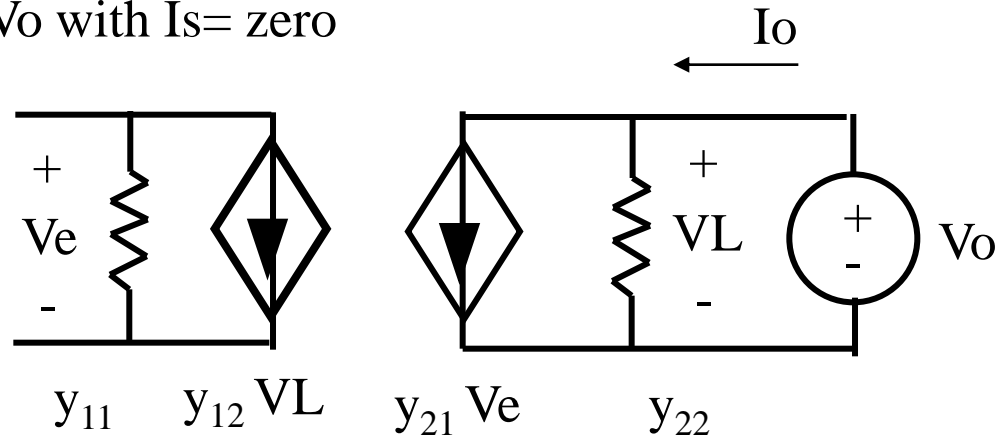**Output Admittance,  $Y_{Of} = I_o/V_o$  with  $I_s = \text{zero}$**




$$\begin{aligned} 0 &= y_{11} V_e + y_{12} V_o \\ I_o &= y_{21} V_e + y_{22} V_o \end{aligned} \quad \rightarrow \quad V_e = -y_{12}/y_{11} V_o$$

$$I_o = y_{21} \left[ -y_{12}/y_{11} V_o \right] + y_{22} V_o = y_{22} V_o \left[ 1 - \frac{y_{12}y_{21}}{y_{11}y_{22}} \right]$$

$$Y_{Of} = I_o/V_o = y_{22} \left[ 1 - \frac{y_{12}y_{21}}{y_{11}y_{22}} \right] = y_{22} \left[ 1 - T \right]$$

# EXAMPLE VOLTAGE-SHUNT FEEDBACK



Example:

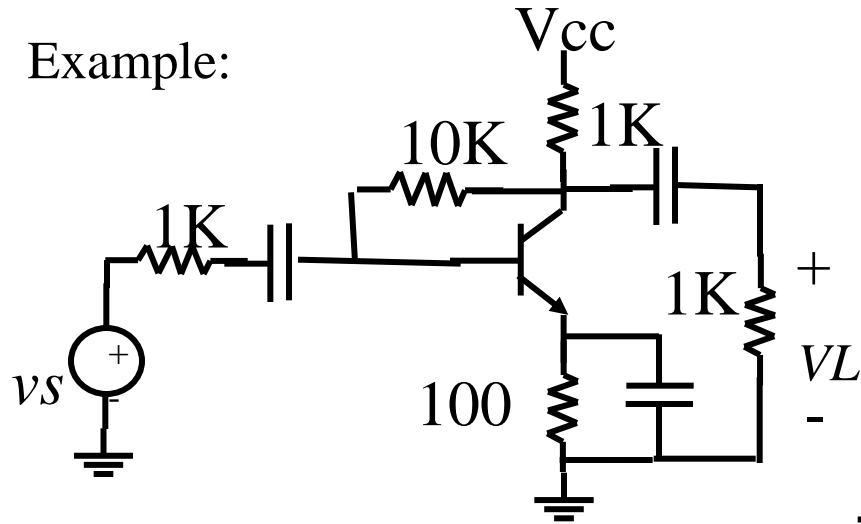

Assume DC analysis is good  
 $\beta = 100$ ,  $V_A = \text{infinite}$ ,  $r_{\pi} = 1K$

ac eq. ckt

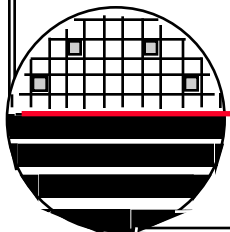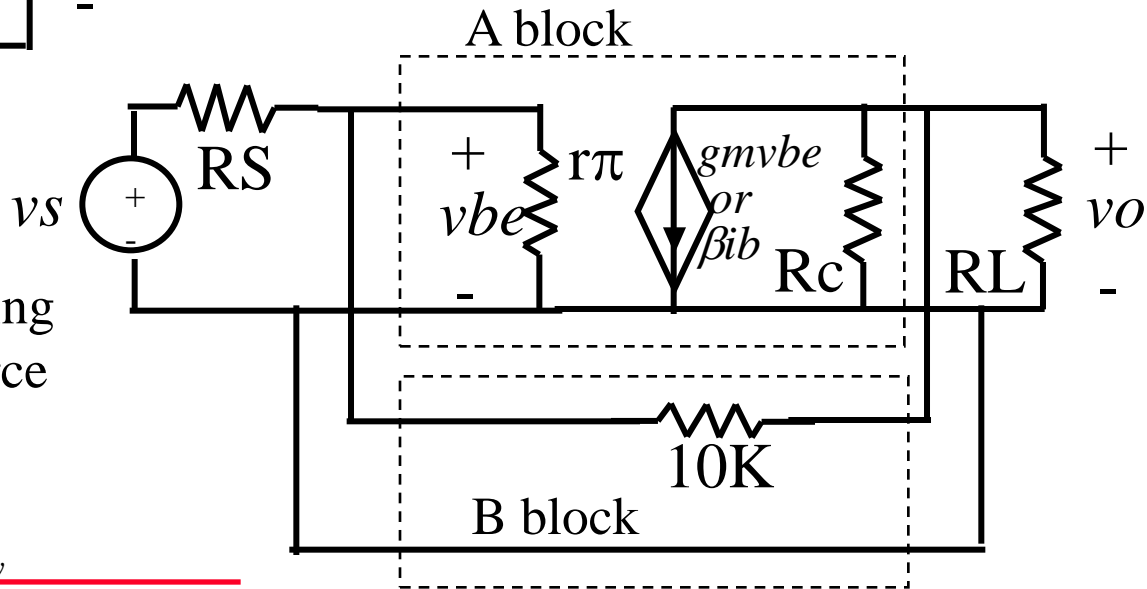1. Identify A block, B block mixing network, sampling network, source and load.






# EXAMPLE VOLTAGE-SHUNT FEEDBACK

2. Find two port parameters for A block and B block.

$$I_1 = y_{11} V_1 + y_{12} V_2$$

$$I_2 = y_{21} V_1 + y_{22} V_2$$

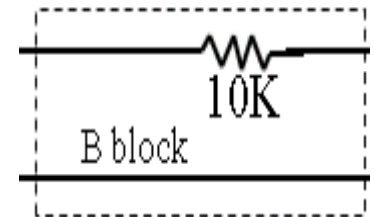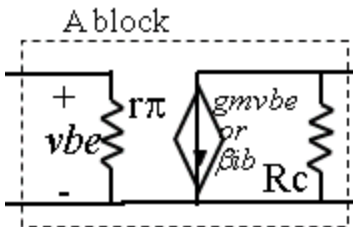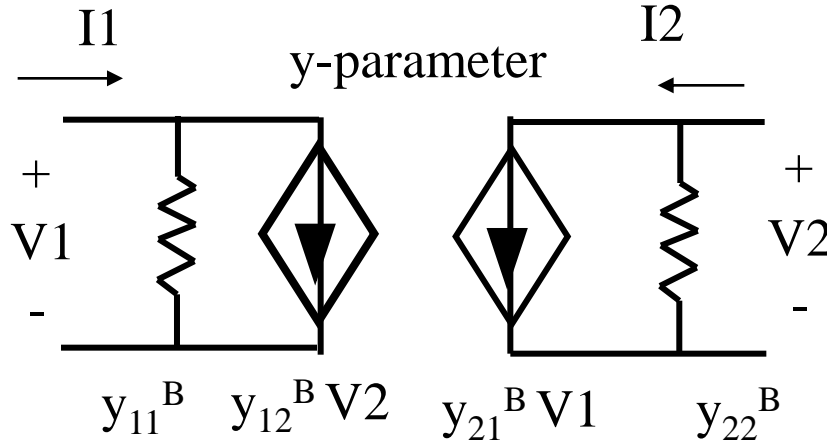

$$y_{11}^A = 1/1K = 1E-3$$

$$y_{12}^A = 0 \text{ (almost always)}$$

$$y_{21}^A = gm = \beta / r\pi = 0.1$$

$$y_{22}^A = 1/1K = 1E-3$$

$$y_{11}^B = 1/10K = 1E-4$$

$$y_{12}^B = -1/10K = -1E-4$$

$$y_{21}^B = -1/10K = -1E-4$$

$$y_{22}^B = 1/10K = 1E-4$$

**EXAMPLE VOLTAGE-SHUNT FEEDBACK**

3. Find the combined parameters

$$\begin{aligned}
 y_{11} &= y_{11}^A + y_{11}^B + 1/RS &= 1e-3 + 1e-4 + 1e-3 &= 2.1e-3 \\
 y_{12} &= y_{12}^A + y_{12}^B &= 0 + -1e-4 &= -1e-4 \\
 y_{21} &= y_{21}^A + y_{21}^B &= 0.1 - 1e-4 &= 0.0999 = 0.1 \\
 y_{22} &= y_{22}^A + y_{22}^B + 1/RL &= 1e-3 + 1e-4 + 1e-3 &= 2.1e-3
 \end{aligned}$$

4. Compute quantities of interest

4.1 Gain with feedback (transresistance)

$$A_{Rf} = \frac{\frac{-y_{21}}{y_{11}y_{22}}}{1 + \frac{-y_{12}y_{21}}{y_{11}y_{22}}} = \frac{\frac{-0.1}{(2.1e-3)(2.1e-3)}}{1 + \frac{-0.1(-1e-4)}{(2.1e-3)(2.1e-3)}} = -6940 \text{ ohms}$$

4.2 Voltage gain with feedback

$$A_{Vf} = A_{Rf} (1/RS) = -6940 (1/1000) = -6.94$$

***EXAMPLE VOLTAGE-SHUNT FEEDBACK***

## 4.3 Current Gain with Feedback

$$A_{If} = A_{Rf} (1/RL) = -6940 (1/1000) = -6.94$$

## 4.4 Approximate Gain

$$A_{Rf} \sim = 1/y_{12} = -1/1e-4 = -10000 \text{ ohms}$$

$$A_{Vf} \sim = -10000 (1/RS) = -10$$

$$A_{If} \sim = -10000 (1/RL) = -10$$

$$4.5 \text{ Loop gain} = T = \frac{y_{12}y_{21}}{y_{11}y_{22}} = (-1e-4)(0.1)/(2.1e-3)(2.1e-3) = -2.27$$

## EXAMPLE VOLTAGE-SHUNT FEEDBACK


4.6 Input admittance  $Y_{if} = y_{11} (1 - T) = y_{11} \left( 1 - \frac{y_{12}y_{21}}{y_{11}y_{22}} \right)$

$$Y_{if} = (2.1e-3)(1 - -2.27) = 6.86 \text{ mS}$$

Input impedance  $Z_{if} = 1/Y_{if} = 146 \text{ ohms}$

Note: this  $Z_{if} = 146 \text{ ohms}$  is equal to the  $1\text{Kohm } R_S$  in parallel with  $Z_{in}'$  the amplifier input impedance.

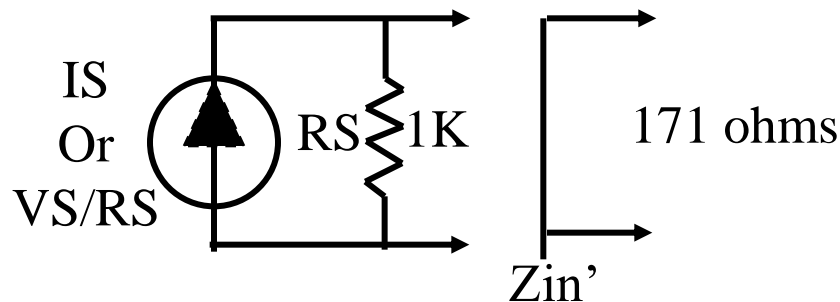So  $1000 // Z_{in}' = 146$  therefore we can find  $Z_{in}' = 171 \text{ ohms}$




***EXAMPLE VOLTAGE-SHUNT FEEDBACK***

4.7 Output Impedance  $Z_{of} = 1/Y_{of}$

$$Y_{of} = y_{22} (1-T) = y_{22} (1 - -2.27) = 6.86 \text{ mS}$$

$$Z_{of} = 1 / Y_{of} = 146 \text{ ohms}$$

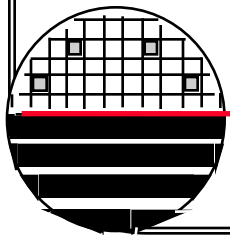
Note: this 146 includes the 1000 ohm RL  
so  $Z_{o'}$  (without RL) is = 171 ohms






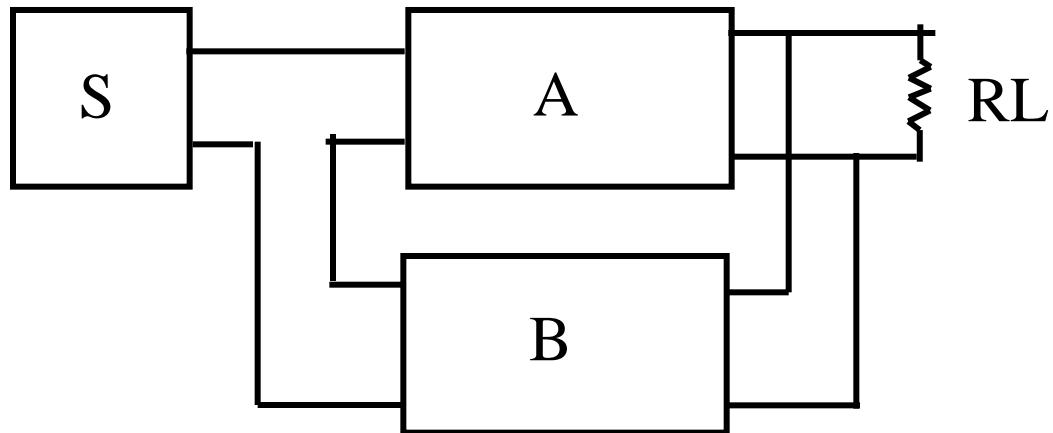
## *VOLTAGE SERIES FEEDBACK*

Since **voltage – series** feedback implies parallel connection at the load and series connection at the source, we will select, h-parameter two port models and a Thevenin model for the source. The resulting equivalent circuit can be greatly simplified by combining appropriate components




**VOLTAGE SERIES FEEDBACK**

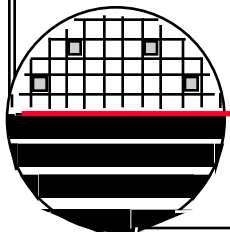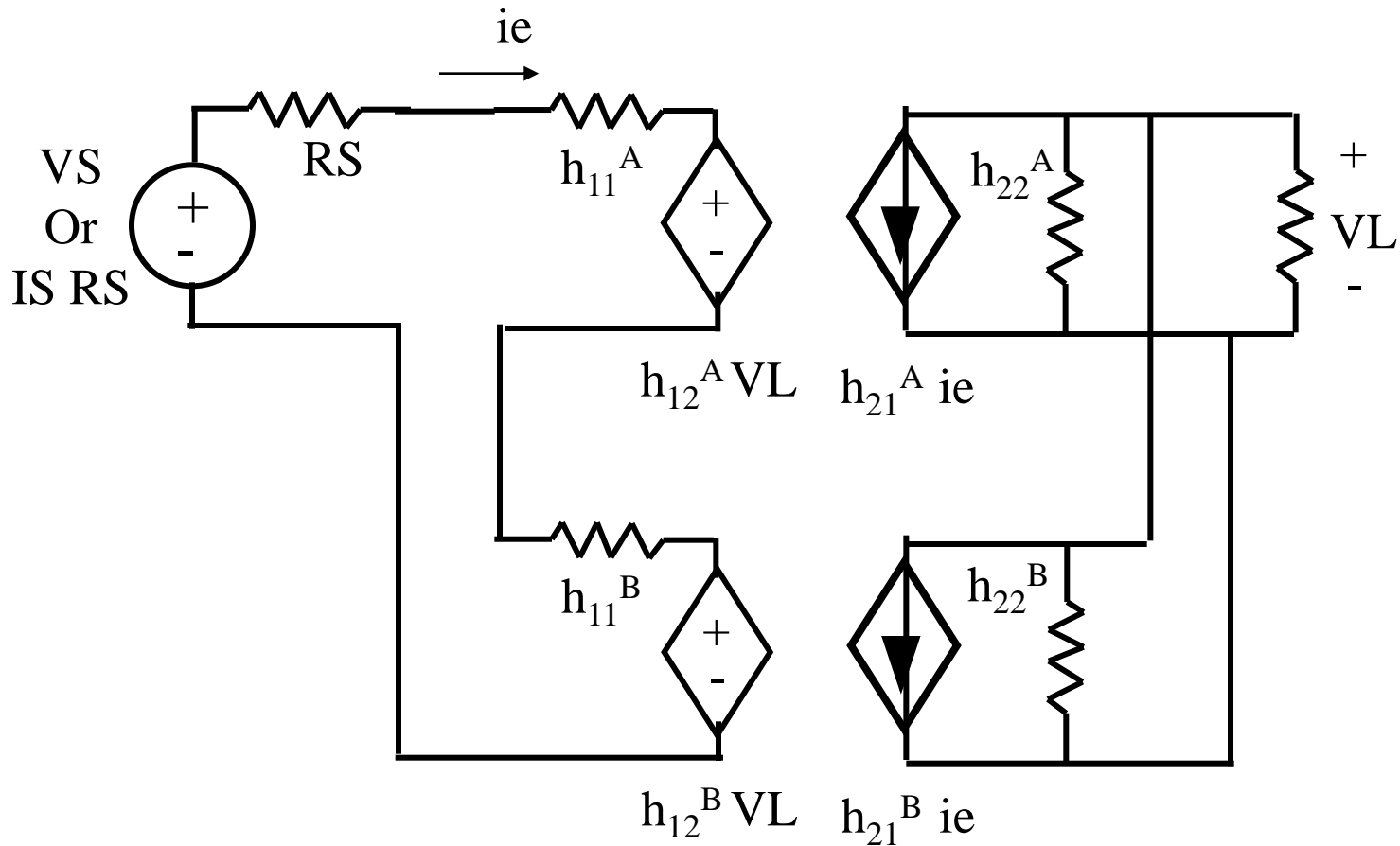
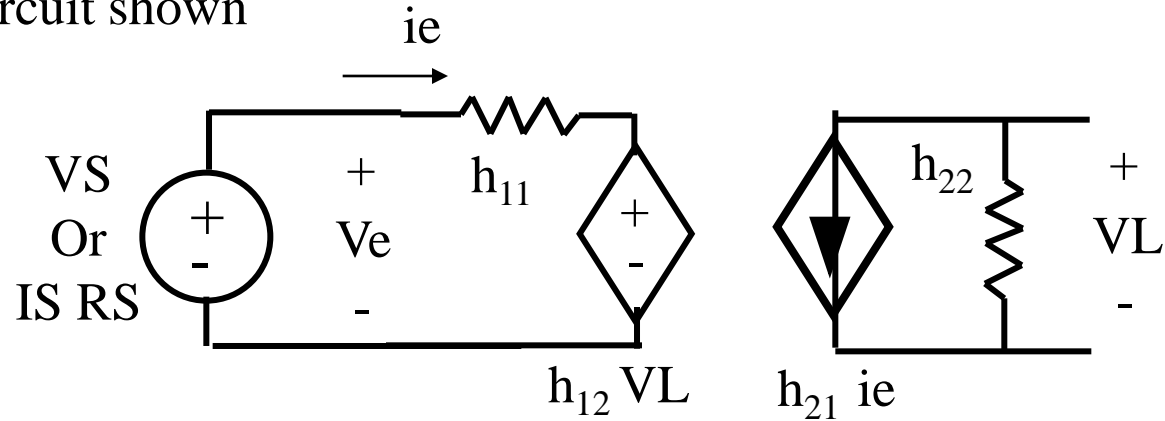
## SIMPLIFIED VOLTAGE-SERIES FEEDBACK

From the previous page we combine appropriate components to get the equivalent circuit shown




$$h_{11} = h_{11}^A + h_{11}^B + R_S$$

$$h_{22} = h_{22}^A + h_{22}^B + 1/R_L$$

$$h_{12} = h_{12}^A + h_{12}^B$$

$$h_{21} = h_{21}^A + h_{21}^B$$

# ANALYSIS OF VOLTAGE-SERIES FEEDBACK

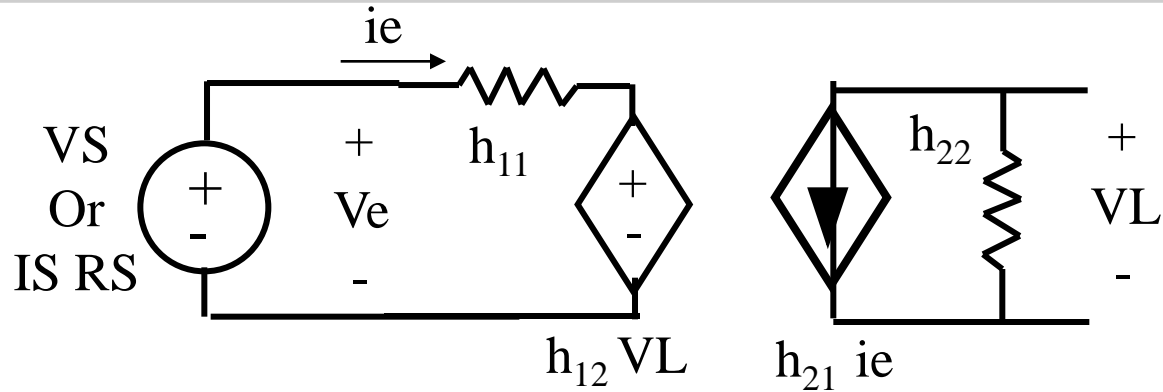

KVL gives

$$V_S = h_{11} i_e + h_{12} V_L$$


KCL gives

$$0 = h_{21} i_e + h_{22} V_L \text{ this eqn gives } i_e = -h_{22} V_L / h_{21}$$


$$V_S = h_{11} (-h_{22} V_L / h_{21}) + h_{12} V_L = [-h_{11} h_{22} / h_{21} + h_{12}] V_L$$

$$V_L / V_S = \frac{1}{[h_{12} - h_{11} h_{22} / h_{21}]}$$
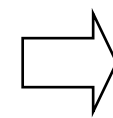
$$V_L / V_S = \frac{-h_{21}}{h_{11} h_{22}} \frac{1}{1 + \frac{-h_{12} h_{21}}{h_{11} h_{22}}}$$



$$A_f = \frac{A}{1 + AB}$$

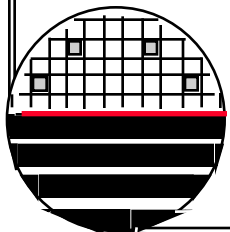

## VOLTAGE SERIES FEEDBACK

**Gain with Feedback**

$$A_{Vf} = \frac{-h_{21}}{h_{11}h_{22}} \frac{1}{1 + \frac{-h_{12}h_{21}}{h_{11}h_{22}}}$$

This is a voltage gain  
(other gains can be found)

**Gain with Feedback Disabled**

$$A_V = \frac{-h_{21}}{h_{11}h_{22}}$$

**Approximate Gain**  $B \approx \frac{1}{h_{12}}$


**Loop Gain**  $T = \frac{h_{12}h_{21}}{h_{11}h_{22}}$

**Input Impedance**  $Z_{If} = h_{11} (1-T)$

**Output Admittance**  $Y_{of} = h_{22} (1-T)$


**EXAMPLE VOLTAGE-SERIES FEEDBACK**

Example:

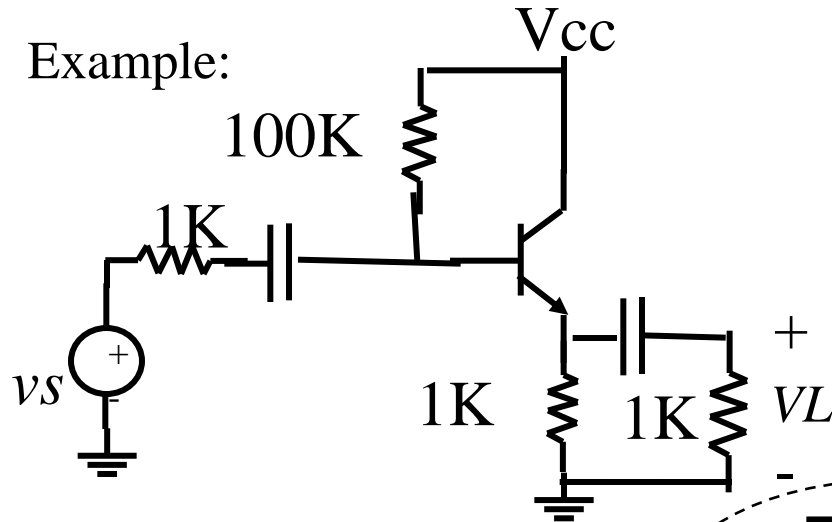


Assume DC analysis is good  
 $\beta = 100$ ,  $V_A = \text{infinite}$ ,  $r_{\pi} = 1K$

ac eq. ckt

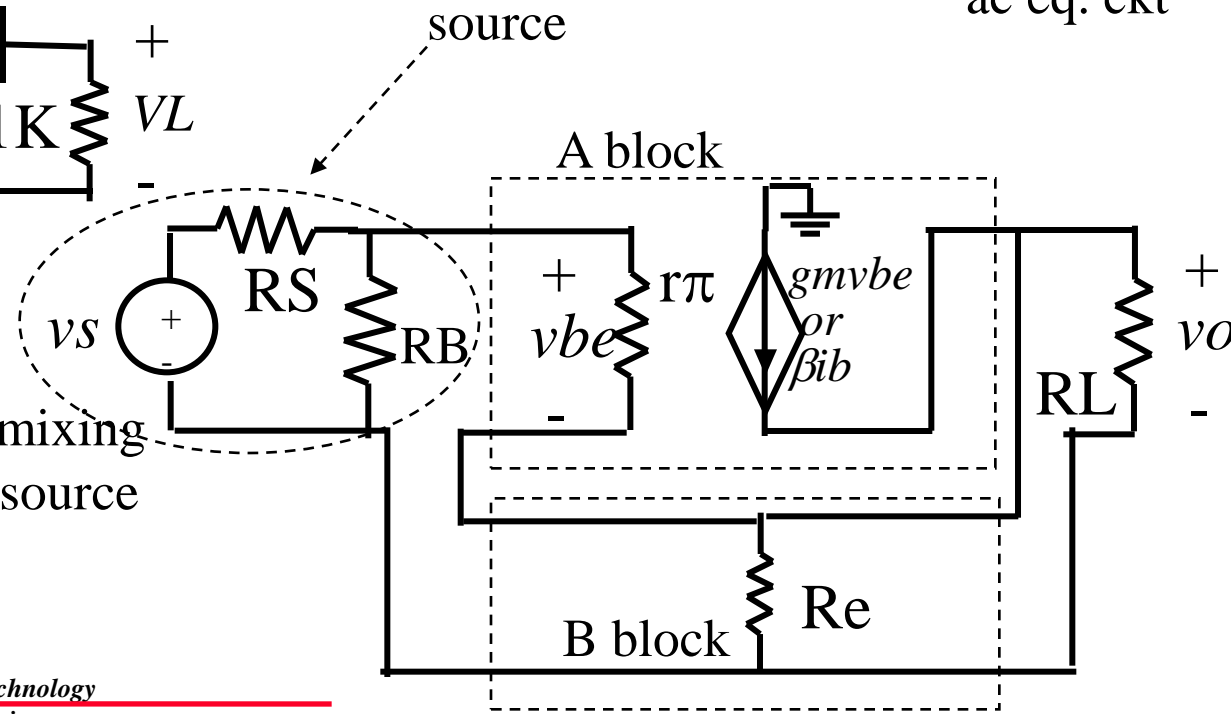


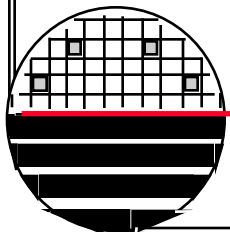1. Identify A block, B block mixing network, sampling network, source and load.



## EXAMPLE VOLTAGE-SERIES FEEDBACK

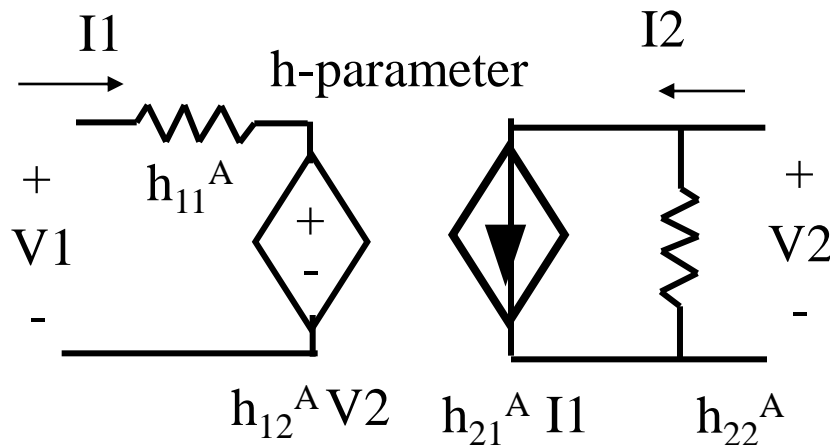2. Find two port parameters for A block and B block.



$$V_1 = h_{11} I_1 + h_{12} V_2$$

$$I_2 = h_{21} I_1 + h_{22} V_2$$

$$h_{11}^A = r_{\pi} = 1000$$

$$h_{12}^A = 0$$

$$h_{21}^A = \beta = -100$$

$$h_{22}^A = 1/r_o = 0$$

$$h_{11}^B = 0$$

$$h_{12}^B = 1$$

$$h_{21}^B = -1$$

$$h_{22}^B = 1/R_e = 1E-3$$

## EXAMPLE VOLTAGE-SERIES FEEDBACK

3. Find the combined parameters

$$\begin{aligned}
 h_{11} &= h_{11}^A + h_{11}^B + RS//RB = 1000 + 0 + 1000 && = 2000 \\
 h_{12} &= h_{12}^A + h_{12}^B && = 0 + 1 && = 1 \\
 h_{21} &= h_{21}^A + h_{21}^B && = -100 - 1 && = -101 \\
 h_{22} &= h_{22}^A + h_{22}^B + 1/RL && = 0 + 1e-3 + 1e-3 && = 2e-3
 \end{aligned}$$

4. Compute quantities of interest

4.1 Gain with feedback (Voltage Gain)

$$A_{Vf} = \frac{\frac{-h_{21}}{h_{11}h_{22}}}{1 + \frac{-h_{12}h_{21}}{h_{11}h_{22}}} = \frac{\frac{101}{(2000)(2e-3)}}{1 + \frac{(101)(1)}{(2000)(2e-3)}} = 0.962$$




## *EXAMPLE VOLTAGE-SERIES FEEDBACK*
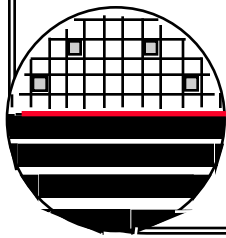
### 4.2 Approximate Voltage Gain

$$A_{vf} \sim = 1/h_{12} = 1$$

$$4.3 \text{ Loop gain} = T = \frac{h_{12}h_{21}}{h_{11}h_{22}} = (-101)(1)/(2000)(2e-3) = -25.3$$




## EXAMPLE VOLTAGE-SERIES FEEDBACK

4.4 Input impedance  $Z_{if} = h_{11} (1 - T) = h_{11} \left( 1 - \frac{h_{12}h_{21}}{h_{11}h_{22}} \right)$

$$Z_{if} = (2000)(1 - -25.3) = 52.6\text{Kohm}$$

Note: this  $Z_{if} = 52.6\text{K ohms}$  is equal to the  $1\text{Kohm } RS//RB$  in series with  $Z_{in}'$  the amplifier input impedance.

So  $Z_{in}' = 51.6\text{K ohms}$

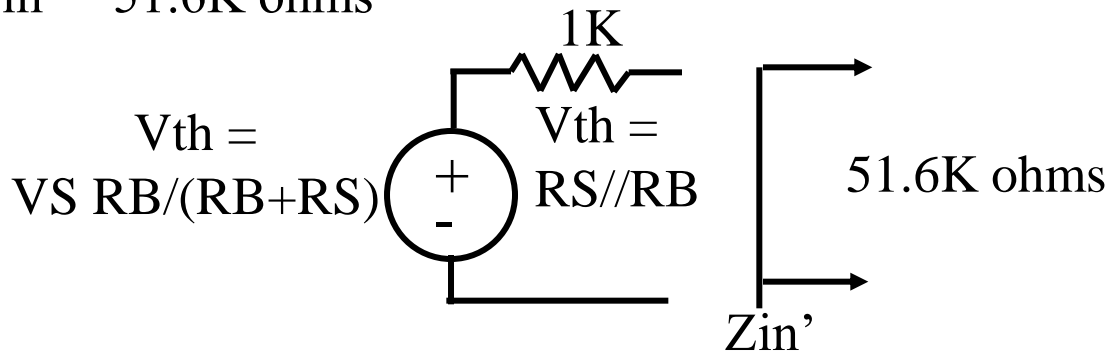

## *EXAMPLE VOLTAGE-SERIES FEEDBACK*

4.5 Output Impedance  $Z_{of} = 1/Y_{of}$


$$Y_{of} = h_{22} (1-T) = 2E-3 (1 - -25.3) = 50.6 \text{ mS}$$

$$Z_{of} = 1 / Y_{of} = 19.8 \text{ ohms}$$

Note: this 19.8 includes the 1000 ohm RL  
so  $Z_{o'}$  (without RL) is = 20.1 ohms
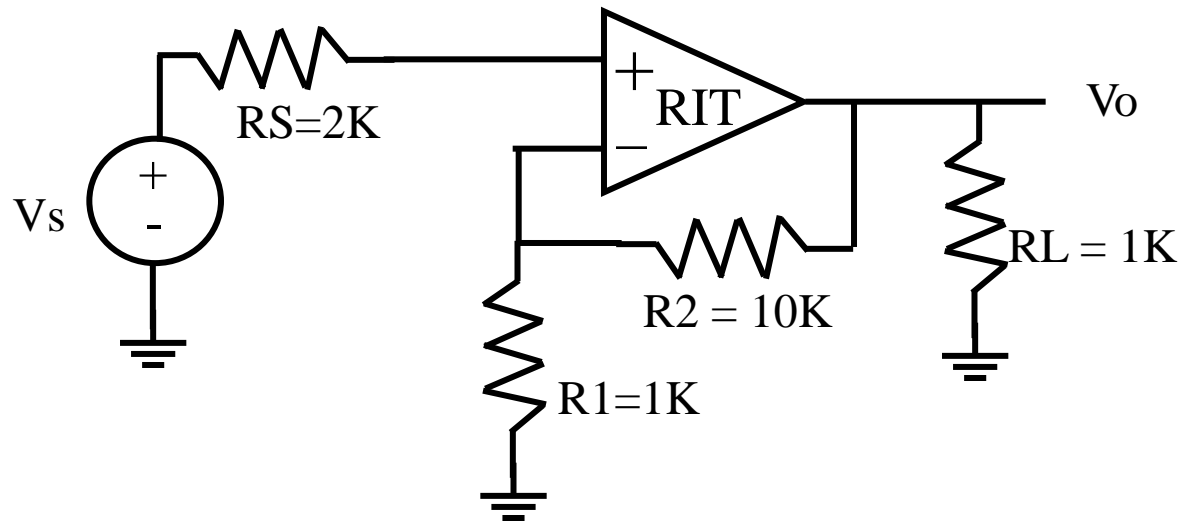
## EXAMPLE RIT OP AMP


Lets use feedback to get the exact voltage gain, approximate voltage gain, input impedance and output impedance for the circuit below. The Op Amp is the one you built in lab with a differential amplifier, level shift stage and output stage. The overall voltage gain was 600 V/V and the differential input resistance was  $\sim 2\text{K}$  ohms. The output resistance was  $\sim 200$  ohms.



Identify the feedback and make sure it is negative feedback.

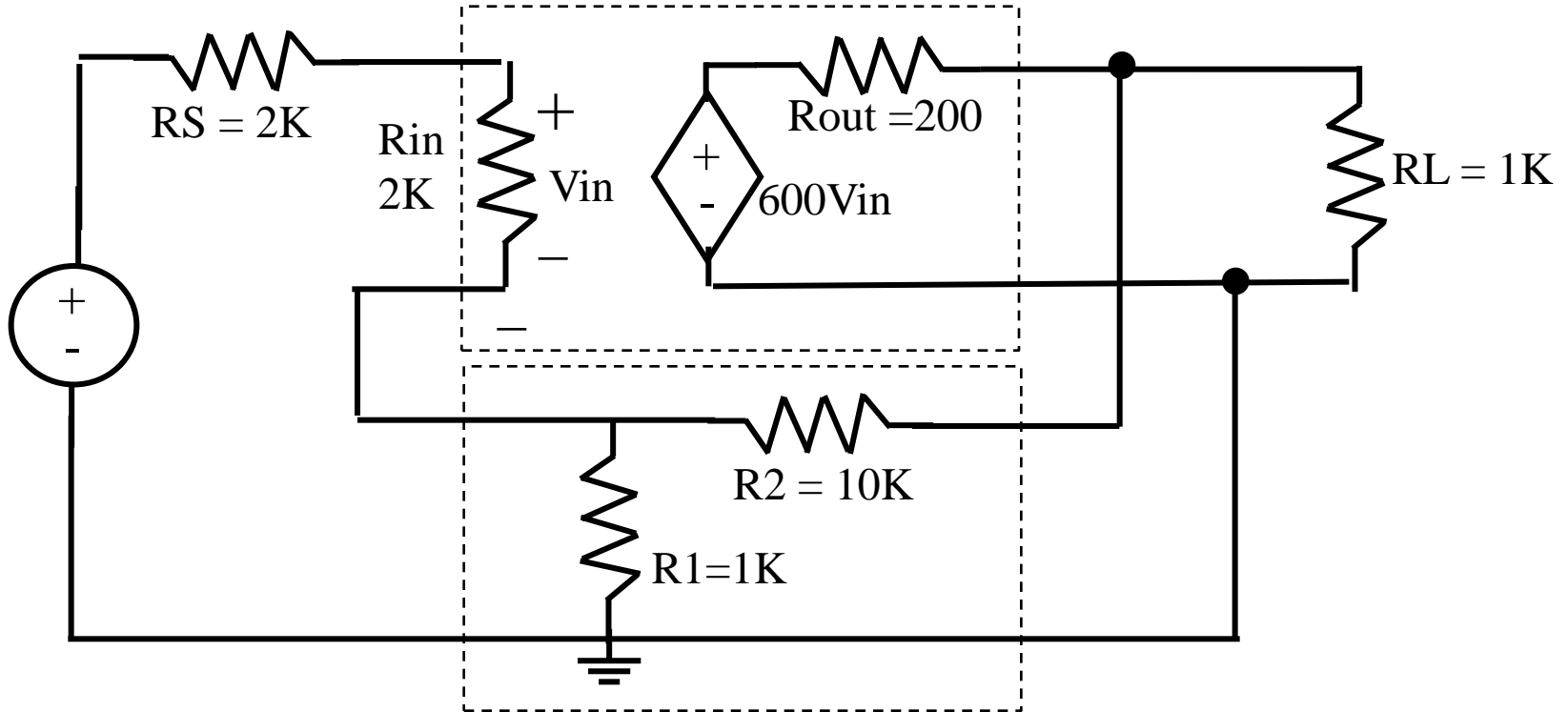**EXAMPLE RIT OP AMP**

The small signal ac equivalent circuit of the feedback amplifier on the previous page is:





Voltage – Series  
h - parameters

# EXAMPLE VOLTAGE-SERIES FEEDBACK

Find two port parameters for A block and B block.



$$V1 = h_{11} I1 + h_{12} V2$$

$$I2 = h_{21} I1 + h_{22} V2$$

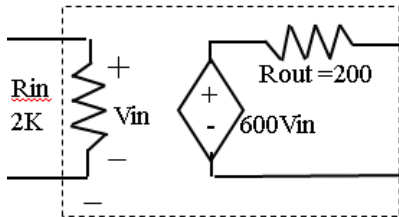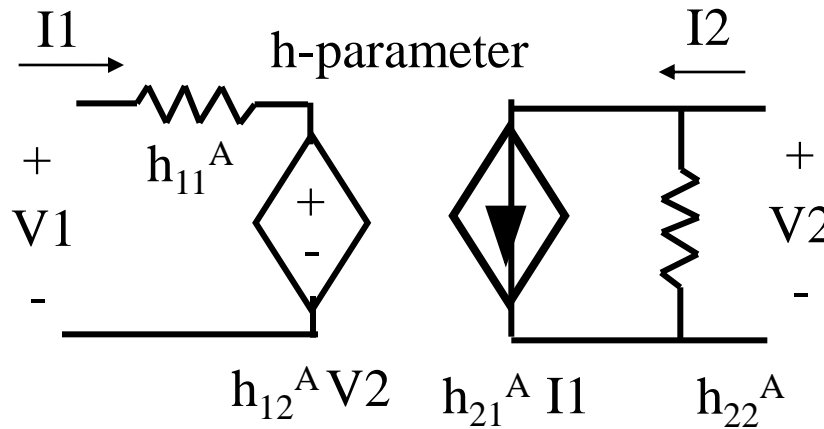

$$\begin{aligned}
 h_{11}^A &= 2K \\
 h_{12}^A &= 0 \\
 h_{21}^A &= -6000 \\
 h_{22}^A &= 1/200 = 5E-3
 \end{aligned}$$
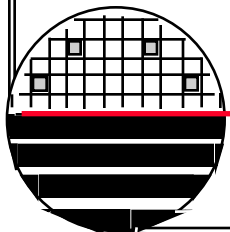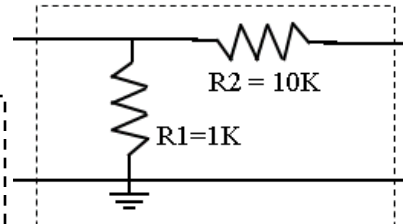
$$\begin{aligned}
 h_{11}^B &= 1K // 10K = 909 \\
 h_{12}^B &= 1/11 = 0.0909 \\
 h_{21}^B &= -0.0909 \\
 h_{22}^B &= 1/11K = 9.09E-5
 \end{aligned}$$



**EXAMPLE VOLTAGE-SERIES FEEDBACK**

Find the combined parameters

$$\begin{aligned}
 h_{11} &= h_{11}^A + h_{11}^B + R_S &= 2000 + 909 + 2000 &= 4909 \\
 h_{12} &= h_{12}^A + h_{12}^B &= 0 + 0.0909 &= 0.0909 \\
 h_{21} &= h_{21}^A + h_{21}^B &= -6000 &= -6000 \\
 h_{22} &= h_{22}^A + h_{22}^B + 1/R_L &= 1/200 + 1/11K + 1/1K &= 6.091E-3
 \end{aligned}$$

Compute quantities of interest

1. Exact Gain with feedback (Voltage Gain)

$$A_{Vf} = \frac{\frac{-h_{21}}{h_{11}h_{22}}}{1 + \frac{-h_{12}h_{21}}{h_{11}h_{22}}} = \frac{\frac{- -6000}{(4909)(6.091e-3)}}{1 + \frac{(- -6000)(0.0909)}{(4909)(6.09e-3)}} = 10.4$$

## EXAMPLE VOLTAGE-SERIES FEEDBACK

### 2. Approximate Voltage Gain

$$A_{Vf} \sim = 1/h_{12} = 1/0.0909 = 11$$

which agrees with ideal op amp theory

### 3. Loop gain = T = $\frac{h_{12}h_{21}}{h_{11}h_{22}} = -18.2$

### 4. Input Impedance

$$Z_{if} = h_{11} \left( 1 - T \right)$$

$$= 4909 (1 - -18.2) = 94.5K$$

but includes RS

$$= 94.5K - 2K = 92.5K \text{ without RS}$$

### 5. Output Impedance

$$Y_{of} = h_{22} \left( 1 - T \right)$$

$$= 6.09E-3 (1 - -18.2) = 0.117S$$

but includes RL

$$Z_{out} = 1/0.117 = 8.53 \text{ ohms}$$

but includes RL


$$Z_{out} = Z'_{out} // RL = 8.53 \text{ ohms}$$

$$Z'_{out} = 8.61 \text{ ohm without RL}$$



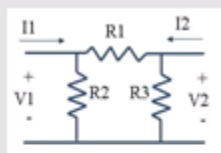
## SPREAD SHEET

Use this spreadsheet to change the values in the table below. The goal of the spreadsheet is to calculate the  $g, h, y,$  and  $z$  parameters for the amplifier network below. Enter the values for Voltage Gain  $V_{out}/V_{in}$ , Input Resistance  $R_{in}$ , and Output Resistance  $R_{out}$ .



$R1 = 10 \text{ K}\Omega$   
 $R2 = 1 \text{ K}\Omega$   
 $R3 = 1E-05 \text{ K}\Omega$   
 $R5 = 2 \text{ K}\Omega$   
 $R1 = 1 \text{ K}\Omega$

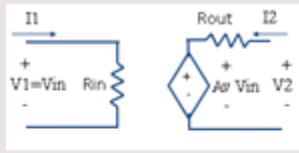
$A_v = 500 \text{ V/V}$   
 $R_{in} = 2 \text{ K}\Omega$   
 $R_{out} = 8.2 \text{ K}\Omega$




**CALCULATIONS:**

Y110 = 1.10E-03 mho	G11 = 1.00E-03 mho	H11 = 3.03E-02 ohm	Z11 = 1.00E-03 ohm
Y120 = 0.000000 1/V	G12 = -1.00E-08 1/V	H12 = 3.03E-02 V/V	Z12 = 1.00E-03 V/V
Y210 = 0.000000 1/V	G21 = -1.00E-08 V/V	H21 = -3.03E-02 1/V	Z21 = 1.00E-03 V/V
Y220 = 1.00E-04 mho	G22 = 1.00E-04 mho	H22 = 3.03E-05 ohm	Z22 = 1.10E-04 ohm

**Feedback Network Two Port Models**

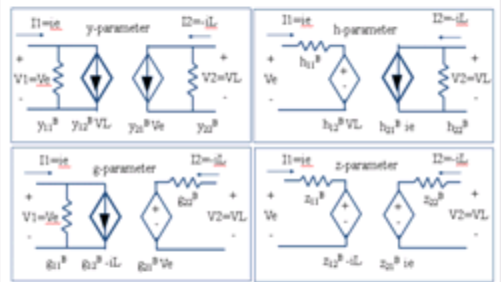

**Amplifier Network Two Port Models**

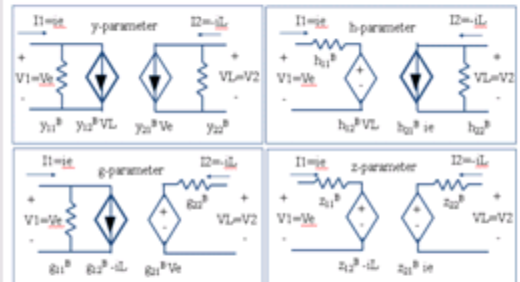

Y11 - Y11A - Y110 - 1/R5 = 2.10E-03 mho	H11 - G11A - G110 - 1/R5 = 8.00E-02 mho	H11 - H11A - H110 - R5 = 4.31E-03 ohm	Z11 - Z11A - Z110 - R5 = 5.00E-03 ohm
Y12 - Y12A - Y120 = -1.00E-08 1/V	G12 - G12A - G120 = -1.00E-08 1/V	H12 - H12A - H120 = 3.03E-02 V/V	Z12 - Z12A - Z120 = 1.00E-03 V/V
Y21 - Y21A - Y210 = -5.00E-08 1/V	G21 - G21A - G210 = 5.00E-08 V/V	H21 - H21A - H210 = 1.00E-03 1/V	Z21 - Z21A - Z210 = 1.00E-03 V/V
Y22 - Y22A - Y220 - 1/R1 = 6.10E-05 mho	G22 - G22A - G220 - R1 = 1.10E-04 mho	H22 - H22A - H220 - 1/R1 = 6.03E-05 ohm	Z22 - Z22A - Z220 - R1 = 1.22E-04 ohm

Approximate Gain With Feedback, mho	Approximate Gain With Feedback, 1/V	Approximate Gain With Feedback, V/V	Approximate Gain With Feedback, S
Approximate voltage Gain, V/V	Approximate voltage Gain, V/V	Approximate voltage Gain With Feedback, V/V	Approximate voltage Gain With Feedback, S
Exact Gain With Feedback, mho	Exact Gain With Feedback, 1/V	Exact Gain With Feedback, V/V	Exact Gain With Feedback, S
Voltage Gain With Feedback, V/V	Voltage Gain With Feedback, V/V	Voltage Gain With Feedback, V/V	Voltage Gain With Feedback, S
Loop Gain	Loop Gain	Loop Gain	Loop Gain
Input Resistance with Feedback (including R5), ohm	Input Resistance with Feedback (including R5), ohm	Input Resistance with Feedback (including R5), ohm	Input Resistance with Feedback (including R5), ohm
Input Impedance with Feedback (including R5), ohm	Input Impedance with Feedback (including R5), ohm	Input Impedance with Feedback (including R5), ohm	Input Impedance with Feedback (including R5), ohm
Output Resistance With Feedback (including R1), ohm	Output Resistance With Feedback (including R1), ohm	Output Resistance With Feedback (including R1), ohm	Output Resistance With Feedback (including R1), ohm
Output Impedance With Feedback (including R1), ohm	Output Impedance With Feedback (including R1), ohm	Output Impedance With Feedback (including R1), ohm	Output Impedance With Feedback (including R1), ohm

## SUMMARY OF FEEDBACK AMPLIFIERS

### Voltage-Shunt

Input Admittance

$$Y_{If} = y_{11} \left( 1 - T \right)$$

$$Y_{Of} = y_{22} \left( 1 - T \right)$$

Output Admittance

Loop Gain

$$T = \frac{y_{12}y_{21}}{y_{11}y_{22}}$$

$$A_{Rf} \cong \frac{1}{y_{12}}$$

~ Gain

Exact Gain

$$A_{Rf} = \frac{-y_{21}}{y_{11}y_{22}}$$

$$1 + \frac{-y_{12}y_{21}}{y_{11}y_{22}}$$

Transresistance

Voltage Gain

$$A_{Vf} = A_{Rf} (1/RS)$$

$$A_{If} = A_{Rf} (1/RL)$$

Current Gain

### Voltage-Series

Input Impedance

$$Z_{If} = h_{11} \left( 1 - T \right)$$

$$Y_{Of} = h_{22} \left( 1 - T \right)$$

Output Admittance

Loop Gain

$$T = \frac{h_{12}h_{21}}{h_{11}h_{22}}$$

$$A_{Vf} \cong \frac{1}{h_{12}}$$

~ Gain

Exact Gain

$$A_{Vf} = \frac{-h_{21}}{h_{11}h_{22}}$$

$$1 + \frac{-h_{12}h_{21}}{h_{11}h_{22}}$$

Voltage gain

Voltage Gain

$$A_{Vf} = A_{Vf}$$

$$A_{If} = A_{Vf} (RS/RL)$$

Current Gain

## SUMMARY OF FEEDBACK AMPLIFIERS

### Current-Shunt

Input Admittance

$$Y_{Of} = g_{22} (1 - T)$$

$$Z_{If} = g_{11} (1 - T)$$

Output Impedance

Loop Gain

$$T = \frac{g_{12}g_{21}}{g_{11}g_{22}}$$

$$A_{If} \approx \frac{1}{g_{12}}$$

~ Gain

Exact Gain

$$A_{If} = \frac{-g_{21}}{g_{11}g_{22}} \left( 1 + \frac{-g_{12}g_{21}}{g_{11}g_{22}} \right)$$

Current Gain

Voltage Gain

$$A_{Vf} = A_{If} (-R_L/R_S)$$

$$A_{If} = A_{If}$$

Current Gain

### Current-Series

Input Impedance

$$Z_{Of} = z_{22} (1 - T)$$

$$Z_{If} = z_{11} (1 - T)$$

Output Impedance

Loop Gain

$$T = \frac{z_{12}z_{21}}{z_{11}z_{22}}$$

$$A_{Gf} \approx \frac{1}{z_{12}}$$

~ Gain

Exact Gain

$$A_{Gf} = \frac{-z_{21}}{z_{11}z_{22}} \left( 1 + \frac{-z_{12}z_{21}}{z_{11}z_{22}} \right)$$

Transconductance

Voltage Gain


$$A_{Vf} = A_{Gf} (-R_L)$$

$$A_{If} = A_{Gf} (R_S)$$

Current Gain




## REFERENCES

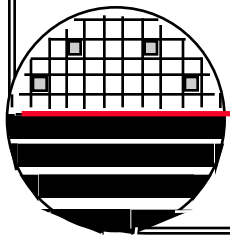1. Sedra and Smith, 5.1-5.4
2. Device Electronics for Integrated Circuits, 2nd Edition, Kamins and Muller, John Wiley and Sons, 1986.
3. The Bipolar Junction Transistor, 2nd Edition, Gerald Neudeck, Addison-Wesley, 1989.



***HOMWORK PROBLEM 1***

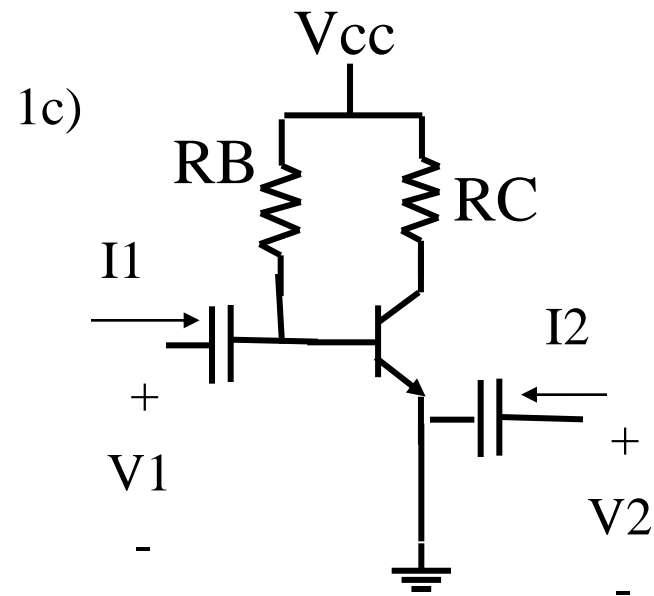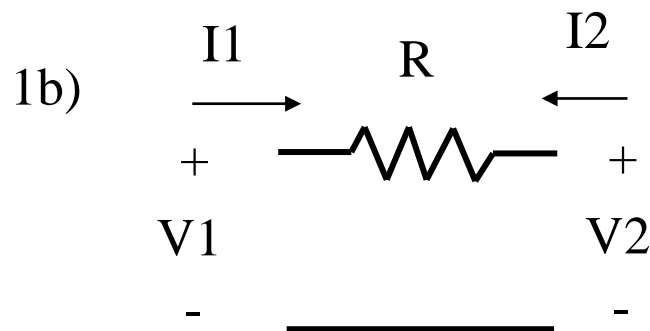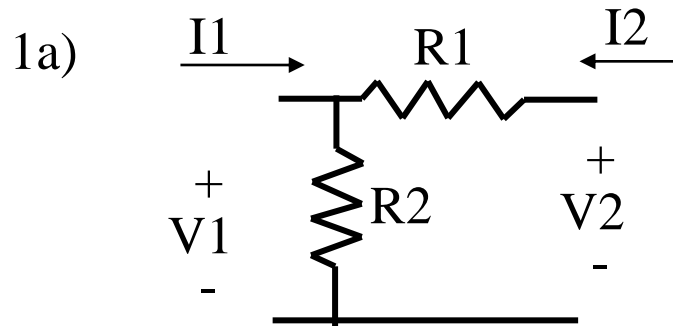1. Find all 16 two port parameters for each of the following circuits.



***HOMWORK SOLUTION FOR PROBLEM 1***

1a)

$$y_{11} = 1/(R1 // R2)$$

$$y_{12} = -1/R1$$

$$y_{21} = -1/R1$$

$$y_{22} = 1/R1$$

$$z_{11} = R2$$

$$z_{12} = R2$$

$$z_{21} = R2$$

$$z_{22} = R1 + R2$$

$$h_{11} = R1 // R2$$

$$h_{12} = R2 / (R1+R2)$$

$$h_{21} = -R2 / (R1+R2)$$

$$h_{22} = 1 / (R1+R2)$$

$$g_{11} = 1/R2$$

$$g_{12} = -1$$

$$g_{21} = 1$$

$$g_{22} = R1$$

1b)

$$y_{11} = 1/R$$

$$y_{12} = -1/R$$

$$y_{21} = -1/R$$

$$y_{22} = 1/R$$

$$z_{11} = \text{infinity}$$

$$z_{12} = \text{infinity}$$

$$z_{21} = \text{infinity}$$

$$z_{22} = \text{infinity}$$

$$h_{11} = R$$

$$h_{12} = 1$$

$$h_{21} = -1$$

$$h_{22} = 0$$

$$g_{11} = 0$$

$$g_{12} = -1$$

$$g_{21} = 1$$

$$g_{22} = R$$

1c)

$$y_{11} = 1/(RB // r\pi)$$

$$y_{12} = 0$$

$$y_{21} = g_m$$

$$y_{22} = 1/RC$$

$$z_{11} = RB // r\pi$$

$$z_{12} = 0$$

$$z_{21} = -\beta RC$$

$$z_{22} = RC$$

$$h_{11} = (RB // r\pi)$$

$$h_{12} = 0$$

$$h_{21} = \beta$$


$$h_{22} = 1/RC$$

$$g_{11} = 1/(RB // r\pi)$$

$$g_{12} = 0$$

$$g_{21} = -g_m RC$$

$$g_{22} = RC$$

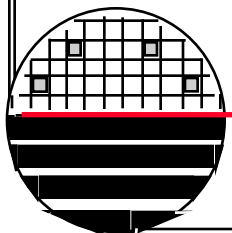

## HOMEWORK PROBLEM 2 AND SOLUTION

2 a) Find  $\int_A^{Af}$  If A changes by 20% how much does Af change.


b) Redesign the feedback amplifier in a) so that  $\int_A^{Af}$  is reduced by a factor of 100.

**Solution:**

$$2 a) \int_A^{Af} = \frac{1}{1 + AB} = 1/101 = .0099$$


If A changes by 20% then Af changes by  $20\% \times 0.0099 = 0.198\% \sim 0.2\%$

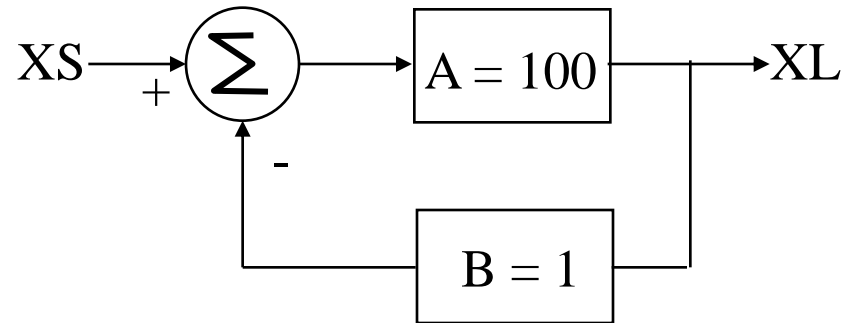b) If we want the sensitivity to be 1/10001 instead of 1/101 then we increase the gain of the amplifier A to 10,000 giving  $Af = A/(1+AB) = 1$  (same as before) and sensitivity =  $1/(1+AB) = 0.0001$  thus a 20% change in A is 0.002% change in gain with feedback



# HOMEWORK PROBLEM 3 AND SOLUTION

3.

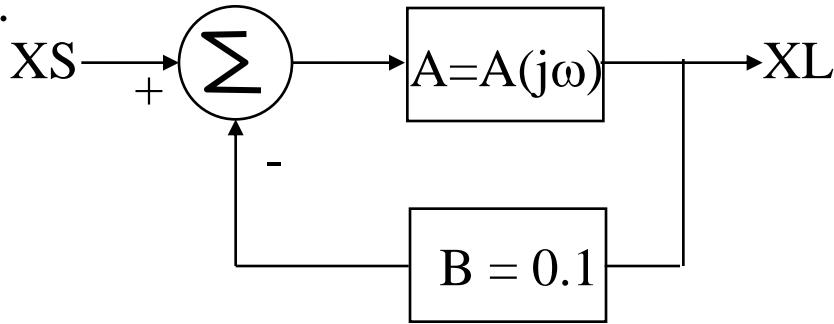


$$A(j\omega) = \frac{1000}{1 + j f/f_1}$$

Let  $f_1 = 1000$  hz

Draw a Bode plot of the amplitude part of the gain function for  $A(j\omega)$  and  $A_f(j\omega)$

**Solution:**

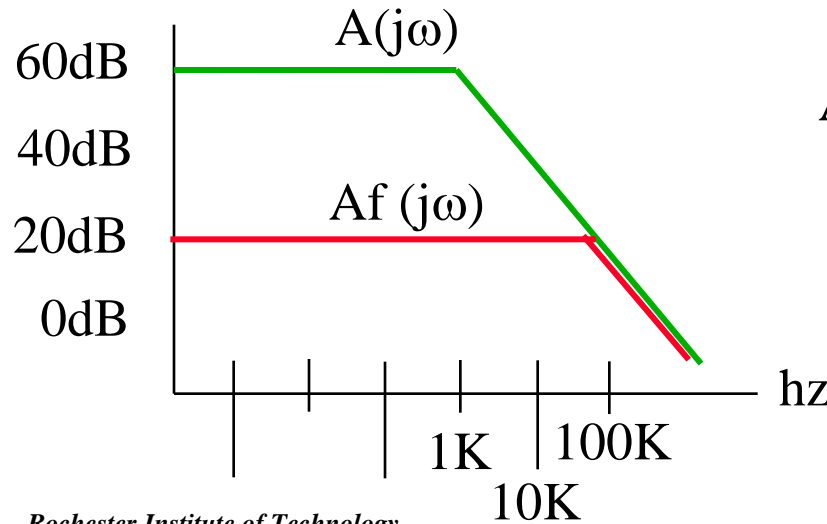

$$A_f = \frac{A}{1+AB} = \frac{\frac{1000}{1+jf/1000}}{1 + \frac{100}{1+jf/1000}}$$



$$= \frac{1000}{1+jf/1000 + 100}$$

$$= \frac{1000}{101} \frac{1}{1+jf/101000}$$







***HOMWORK PROBLEM 4***

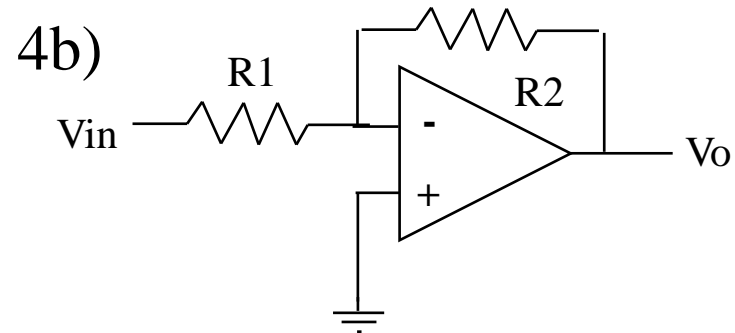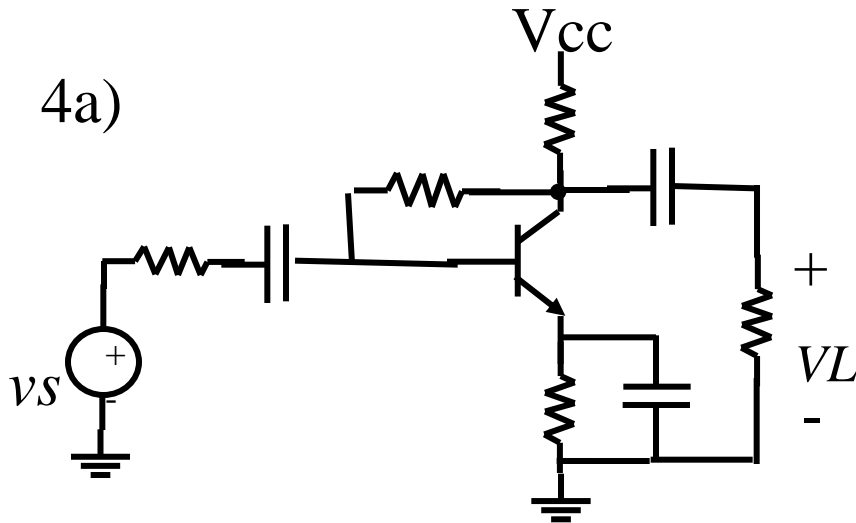4) Refer to the feedback amplifiers shown below. For each identify the type of feedback and determine if the feedback is negative or positive.




***HOMWORK PROBLEM 4 (CONTINUED)***

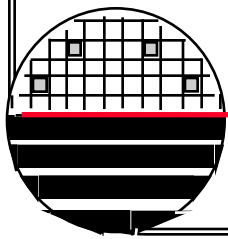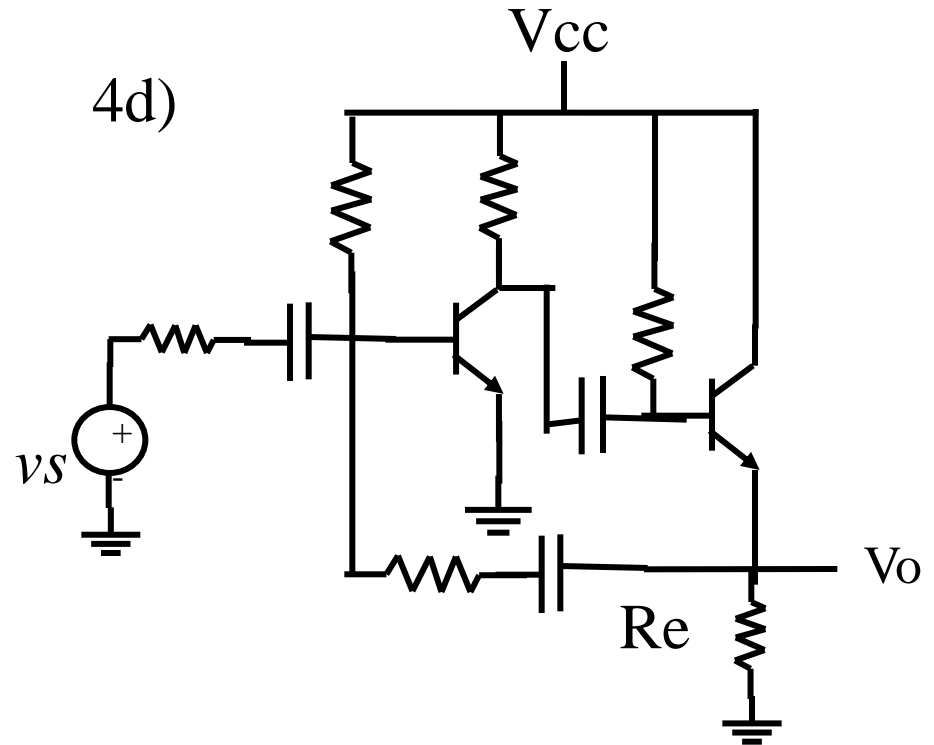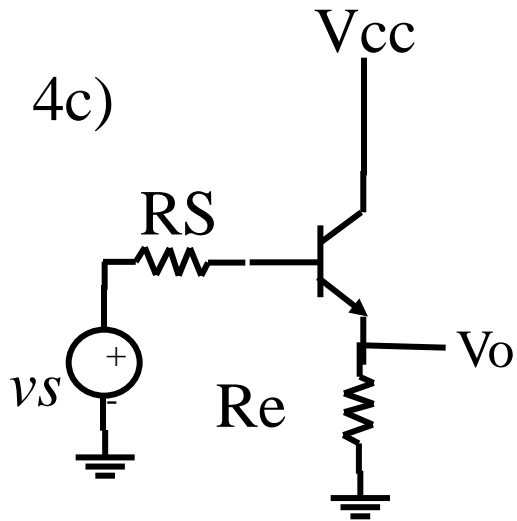

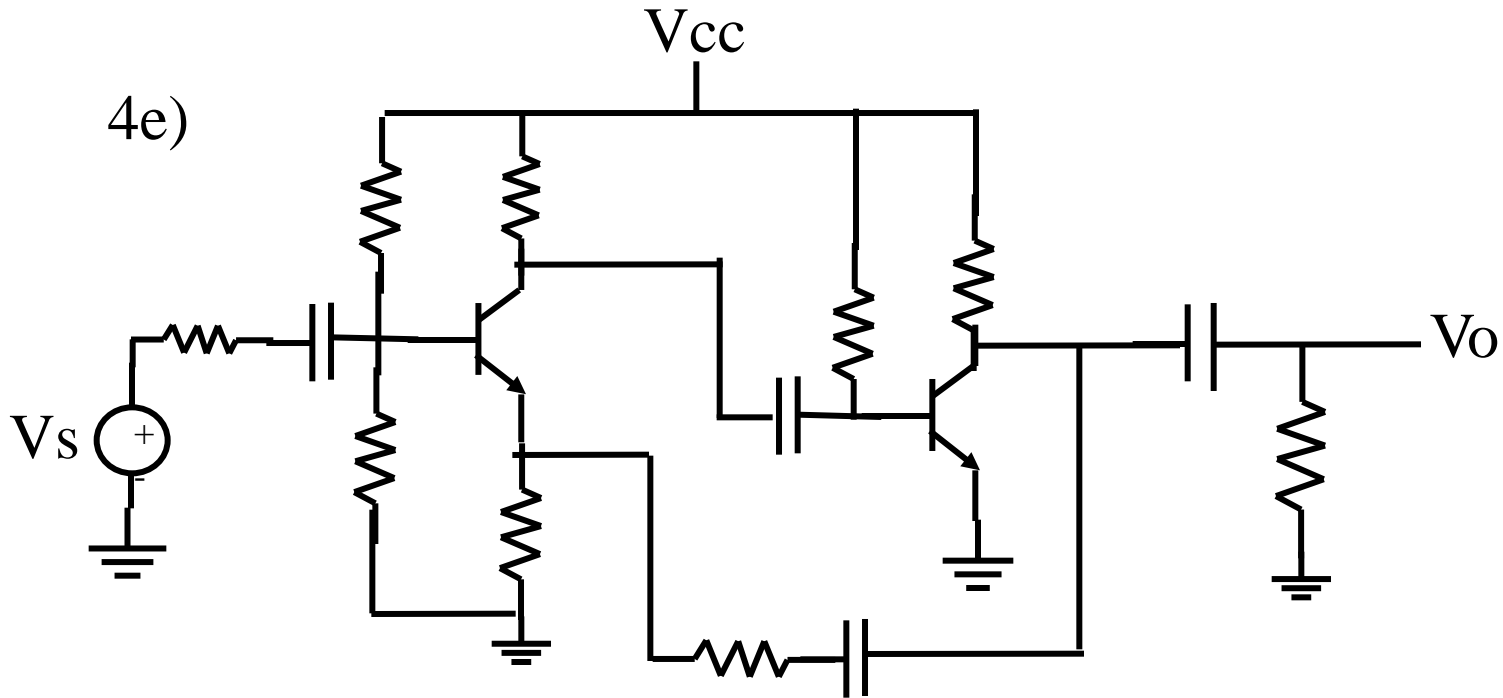***HOMWORK PROBLEM 4 (CONTINUED)***

## *HOMWORK PROBLEM 4 SOLUTION*

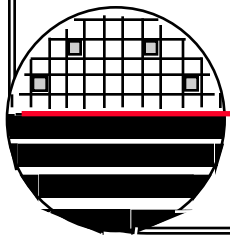4. All are negative feedback
  - a. Voltage Shunt
  - b. Voltage Shunt
  - c. Voltage Series
  - d. Voltage Shunt
  - e. Voltage Series




***HOMWORK PROBLEM 5***

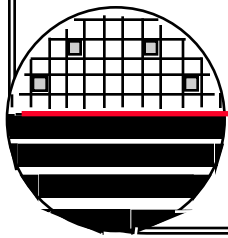5) For each of the circuits shown in problems 7, 8, and 9, estimate the gain with feedback.  $A_{xf} \approx 1/B$  and  $B = X_{12}$ , where  $X_{12}$  is the appropriate combined two port parameters.

Identify the type of gain, transconductance, transresistance, current or voltage.

Convert  $A_{xf}$  to voltage gain with feedback,  $A_{vf}$ .



***HOMWORK PROBLEM 5 SOLUTION***

5a) for the amplifier in problem 6 we have voltage shunt feedback which uses y parameter two port equivalent circuits for the analysis.

$$y_{12} = y_{12}^A + y_{12}^B = 0 - 1/10K$$

$$A_{Rf} \approx 1/y_{12} = -10K \text{ ohms}$$

$$A_{Vf} = A_{Rf} 1/RS = -10K/600 = -16.7$$

5b) for the amplifier in problem 7 we have current shunt feedback which uses g parameter two port equivalent circuits for the analysis.

$$g_{12} = g_{12}^A + g_{12}^B = 0 - 200/(200+10k) = -0.0196$$


$$A_{If} \approx 1/g_{12} = -1/0.0196 = -51$$

$$A_{Vf} = A_{If} (-RL)/RS = -51 (-2K/1K) = 102$$

5c) for the amplifier in problem 8 we have voltage series feedback which uses h parameter two port equivalent circuits for the analysis.

$$h_{12} = h_{12}^A + h_{12}^B = 0 + 100/(100+10k) = 0.0099$$

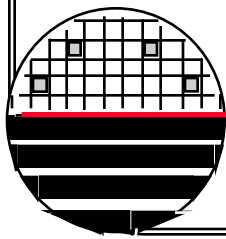
$$A_{Vf} \approx 1/h_{12} = 1/0.0099 = -101$$



**HOMWORK PROBLEM 6**

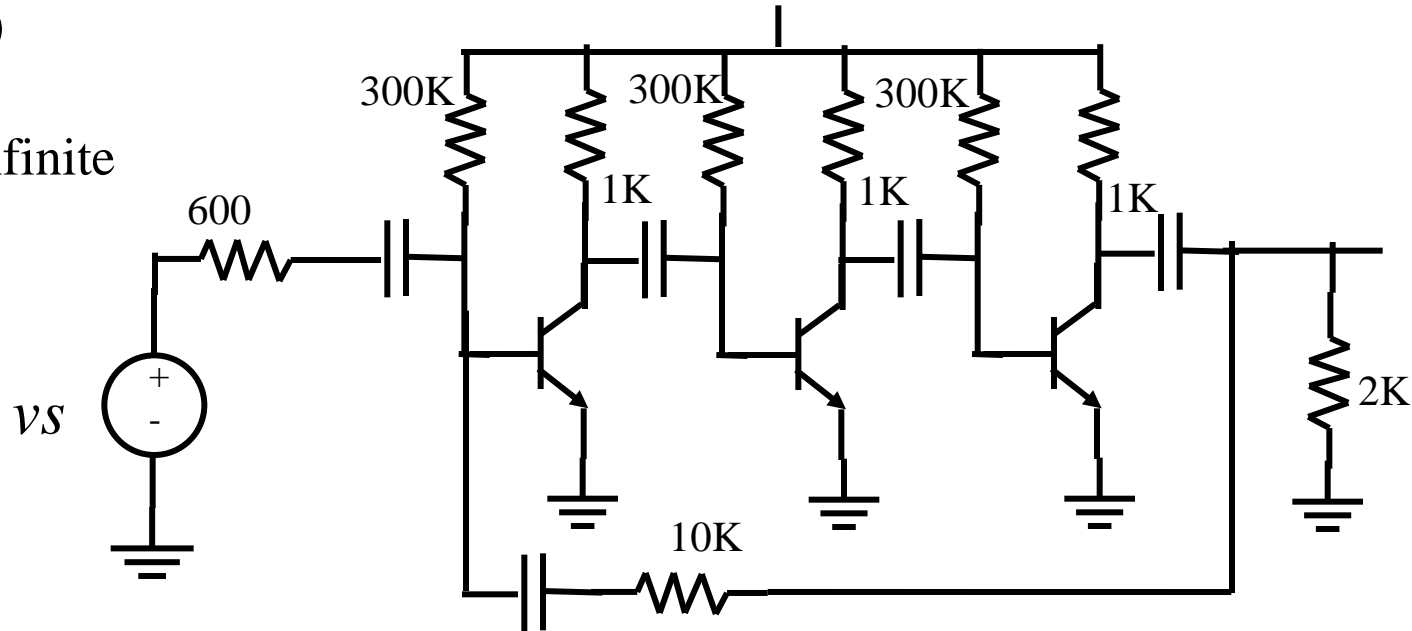
6) Find the exact gain with feedback for each of the circuit shown below.

$\beta = 100$   
 $r\pi = 1k$   
 $V_A = \text{infinite}$




$g_m = I_c/V_T = \beta/r\pi = 100/1K = 100mS$

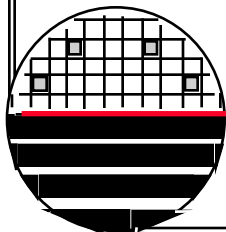Find the two port parameters for the A and B networks and compute  $A_{Vf}$  (exactly)



**HOMWORK PROBLEM 6 SOLUTION**

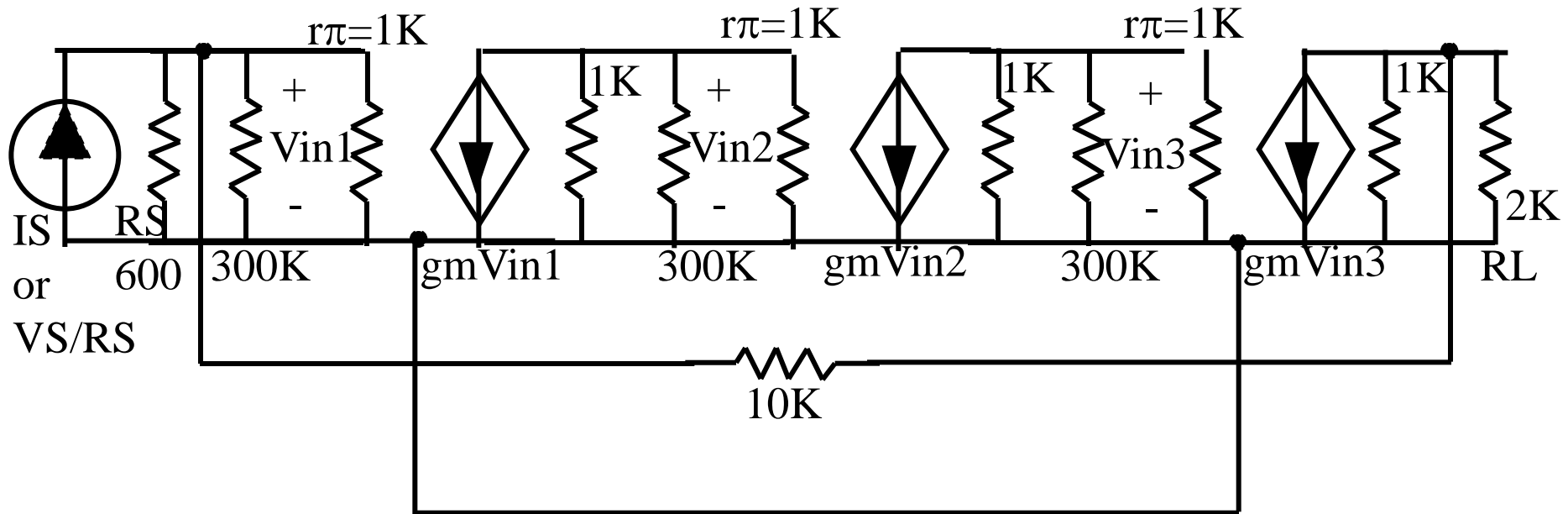

$$y_{11A} = 1/(300K // 1K) = 0.001003 \quad y_{12A} = 0 \quad y_{22A} = 1/1K = 0.001$$

$$y_{21A} = -gm_3(-gm_2(1K // 300K // 1K))(-gm_1(1K // 300K // 1K)) = -250$$

$$y_{11B} = 1/10K = 0.0001 \quad y_{12B} = -1/10K \quad y_{21B} = -1/10K \quad y_{22A} = 1/10K$$



## *HOMWORK PROBLEM 6 SOLUTION*

Exact Gain

$$A_{Rf} = \frac{\frac{-y_{21}}{y_{11}y_{22}}}{1 + \frac{-y_{12}y_{21}}{y_{11}y_{22}}}$$

Transresistance

$$A_{rf} = \frac{250/((.00277)(.0016))}{1 + (-0.0001)(250)/((.00277)(.0016))} = -9998 \text{ ohms}$$

Note:  $A_{rf} \sim 1/y_{12} = -10000 \text{ ohms}$

$$A_{vf} = A_{rf} \cdot 1/R_S = -9998/600 = -16.7$$

$$y_{11} = y_{11A} + y_{11B} + 1/R_S = 0.001 + 0.0001 + 0.00167 = 0.00277$$



$$y_{12} = y_{12A} + y_{12B} = -0.0001 - 0 = -0.0001$$

$$y_{21} = y_{21A} + y_{21B} = -0.0001 - 250 = -250$$

$$y_{22} = y_{22A} + y_{22B} + 1/R_L = 0.0001 + 0.001 + 0.0005 = 0.0016$$


***HOMWORK PROBLEM 7***

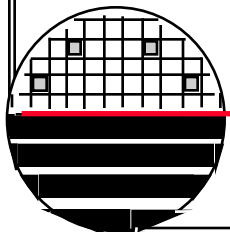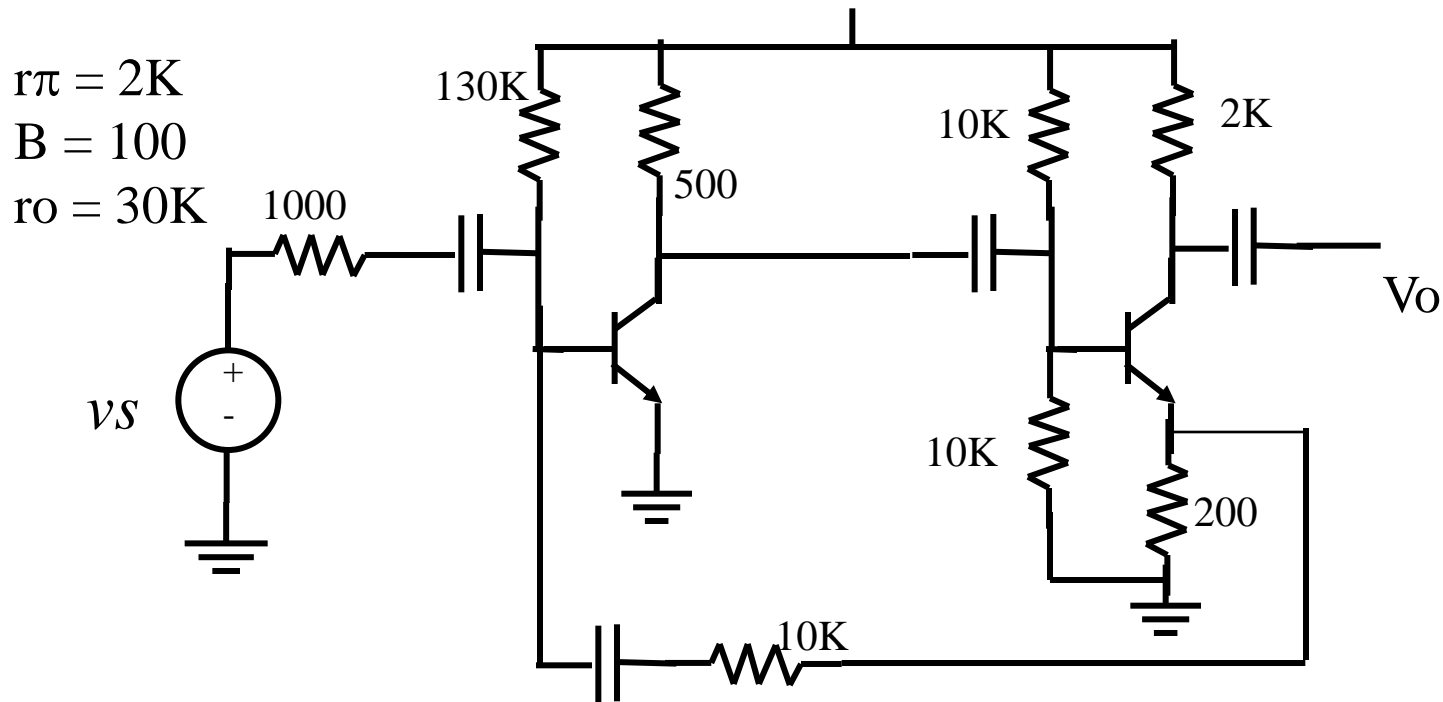7) Find the exact gain with feedback for the circuit shown below.


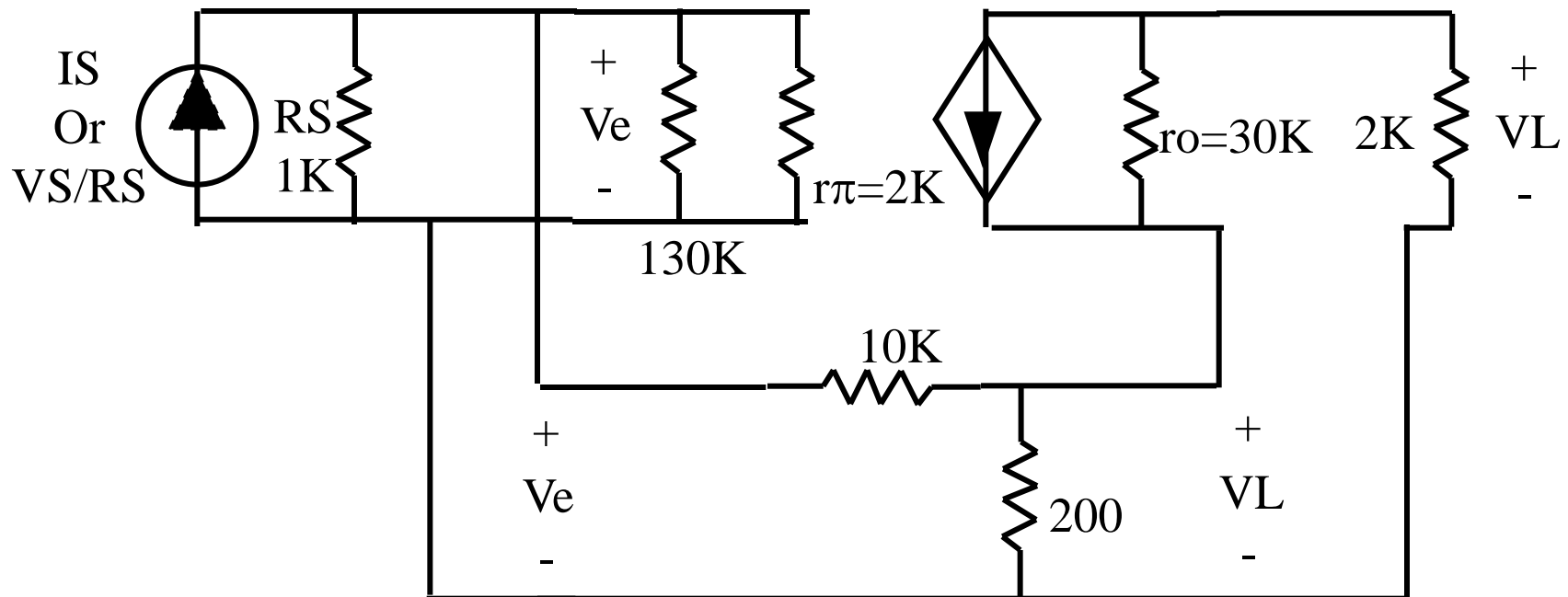
## HOMEWORK PROBLEM 7 SOLUTION

7 cont.) Find the exact gain with feedback for the circuit shown below. The ac equivalent circuit below is useful in separating the B block of the feedback amplifier.



***HOMWORK PROBLEM 7 SOLUTION***

7 cont.)

$$g_{11A}=0.5e-3$$

$$g_{12A}=0$$

$$g_{21A}=13.7E-3(30K)=3020$$

$$g_{22A}=30K$$

$$g_{11B}=0.098e-3$$

$$g_{12B}=-0.0196$$

$$g_{21B}=0.0196$$

$$g_{22B}=193$$

$$1/RS = 1E-3$$

$$RL=2K$$

$$g_{11}=g_{11A}+g_{11B}+1/RS = 1.598E-3$$

$$g_{12} = g_{12A} + g_{12B} = -0.0196$$

$$g_{21} = g_{21A} + g_{21B} = 3120$$

$$g_{22} = g_{22A} + g_{22B} + RL = 32.19K$$

Exact Gain (current gain)


$$A_{If} = \frac{\frac{-g_{21}}{g_{11}g_{22}}}{1 + \frac{-g_{12}g_{21}}{g_{11}g_{22}}} = -27.3$$

$$\text{Note: } A_{if} \sim 1/g_{12} = -51$$


$$A_{vf} = A_{if} (-RL)/RS = -27.3 (-2K/1K) = 54.6$$

***HOMWORK PROBLEM 8***

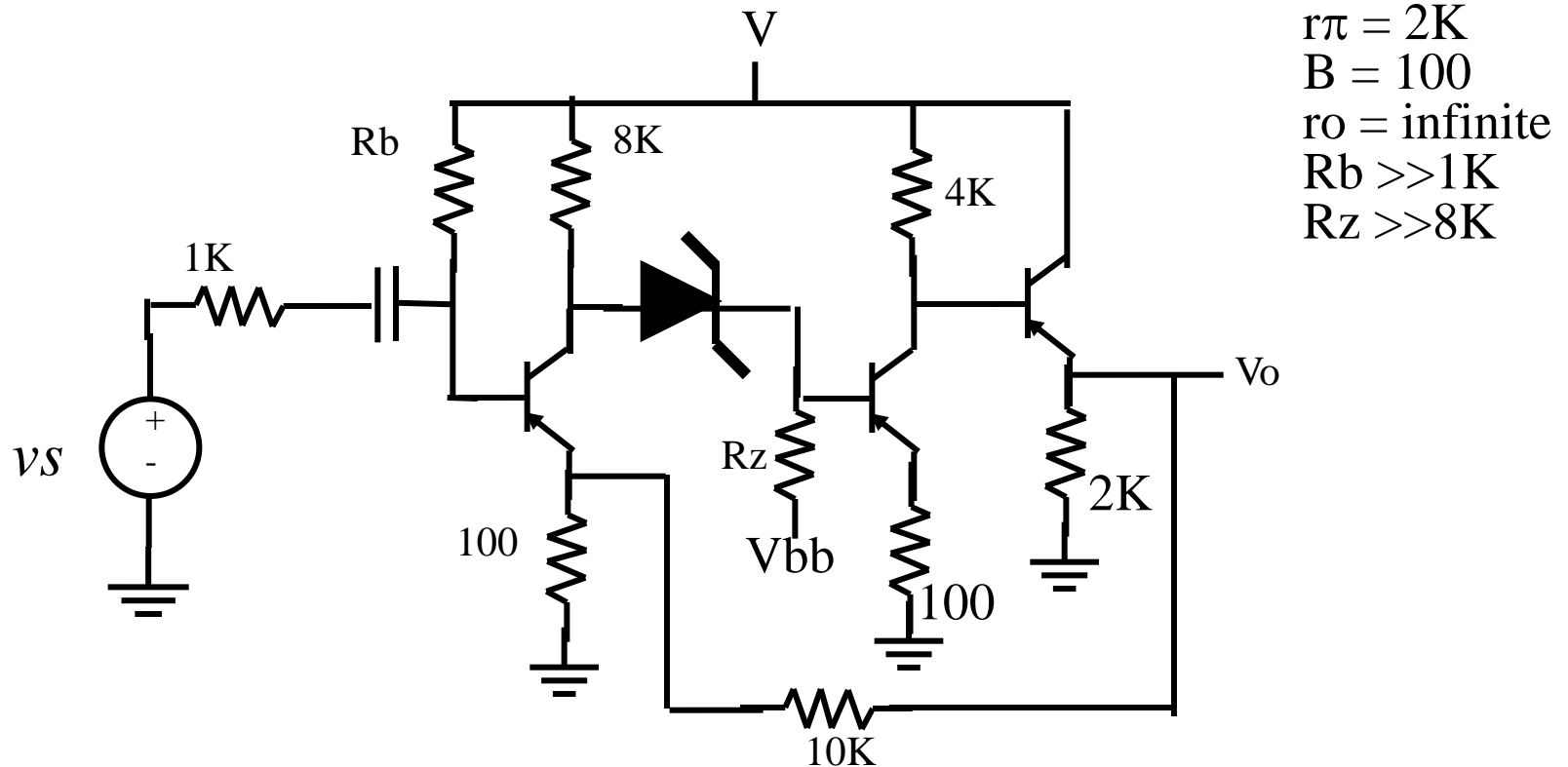8) Find the exact gain with feedback for the circuit shown below.




## HOMEWORK PROBLEM 8 SOLUTION

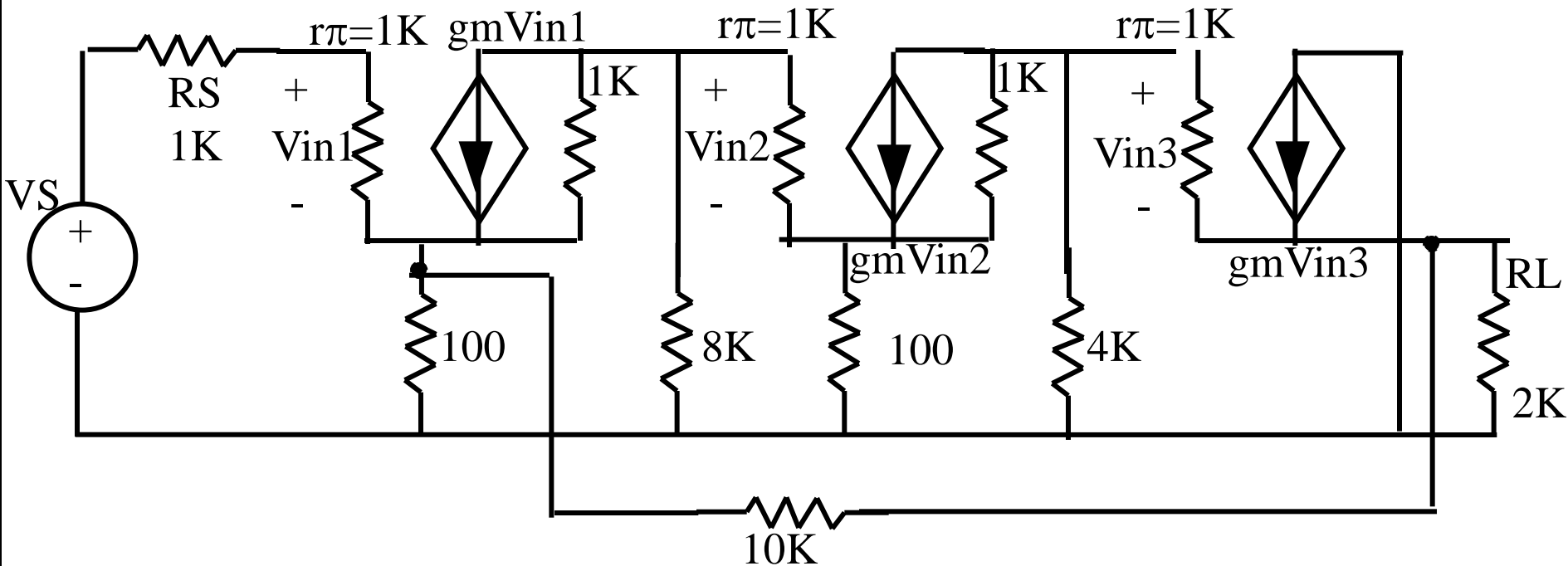

Note: the “A” block and “B” block are not completely separate, with proper mixing and sampling networks. The following equivalent circuit can be used

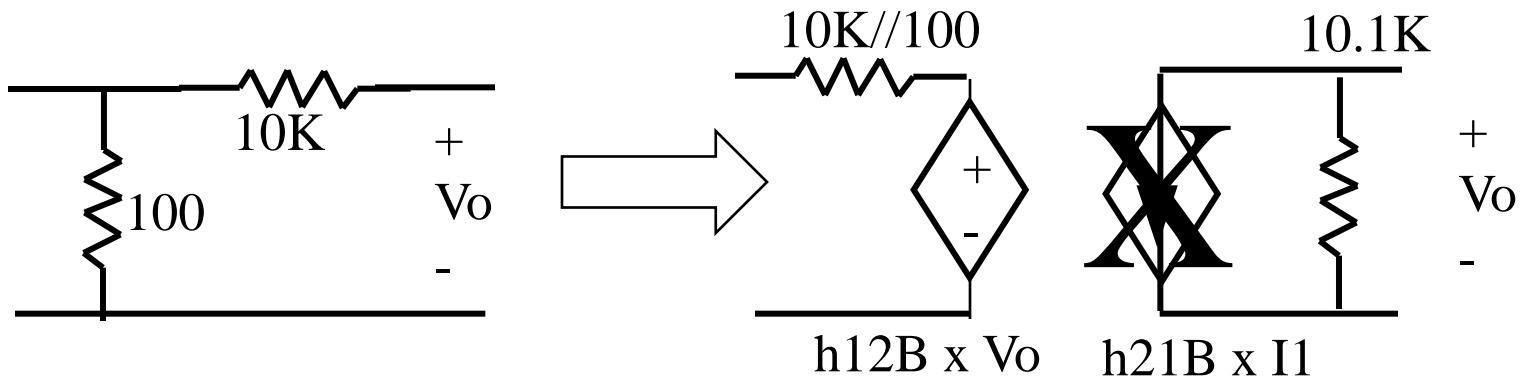**HOMWORK PROBLEM 8 SOLUTION**

First consider the 10K and 100 ohm as the “B” block




We can not just take the 100 ohm out of the emitter of the first transistor because the transistor will not work correctly in the “A” block,

Note:  $h_{21A} \gg h_{21B}$  so neglect  $h_{21B}$
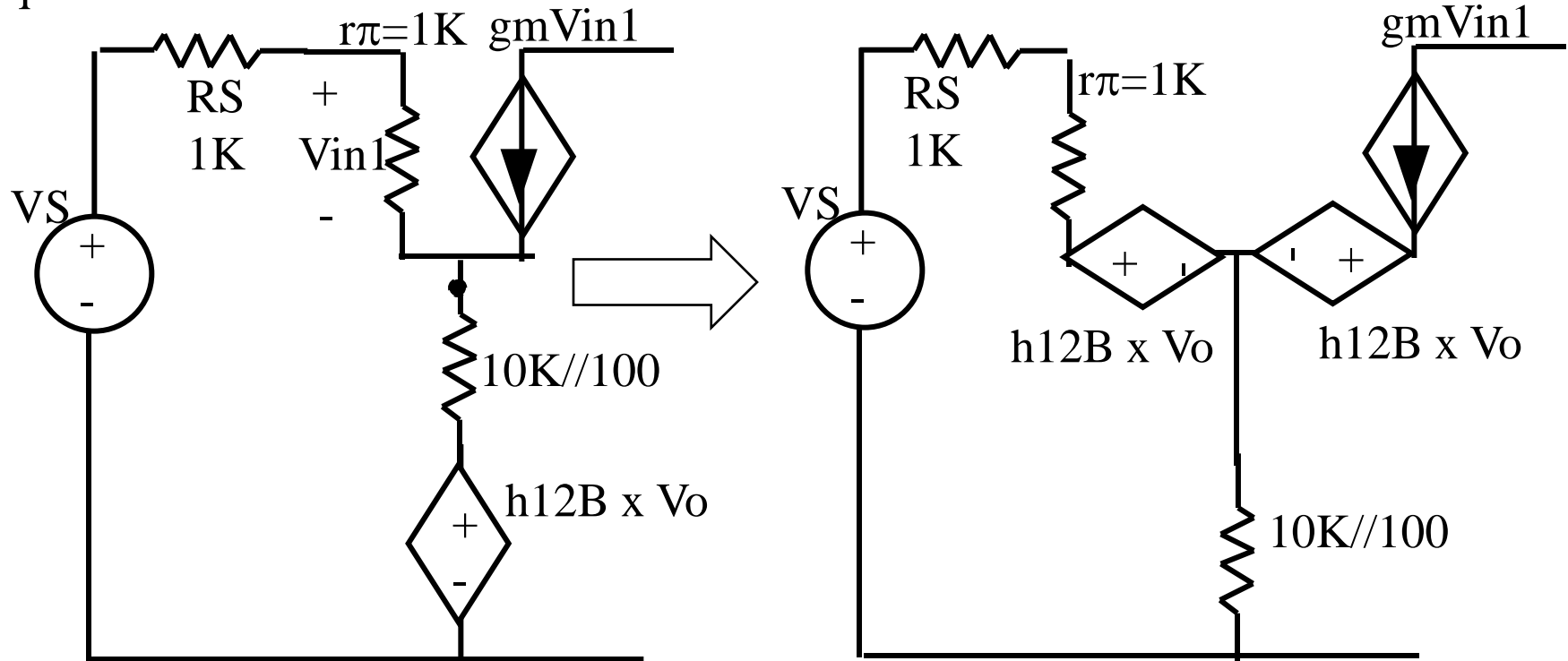
## HOMEWORK PROBLEM 8 SOLUTION

In the emitter of the first transistor put the left hand part of the “B” block 2 port equivalent circuit




Note: the right  $h_{12}V_o$  is in series with a current source and can be eliminated.

Note: left  $h_{12}V_o$  is in a series loop to left of the two X's (next page) and can be moved anywhere in that loop.



**HOMWORK PROBLEM 8 SOLUTION**

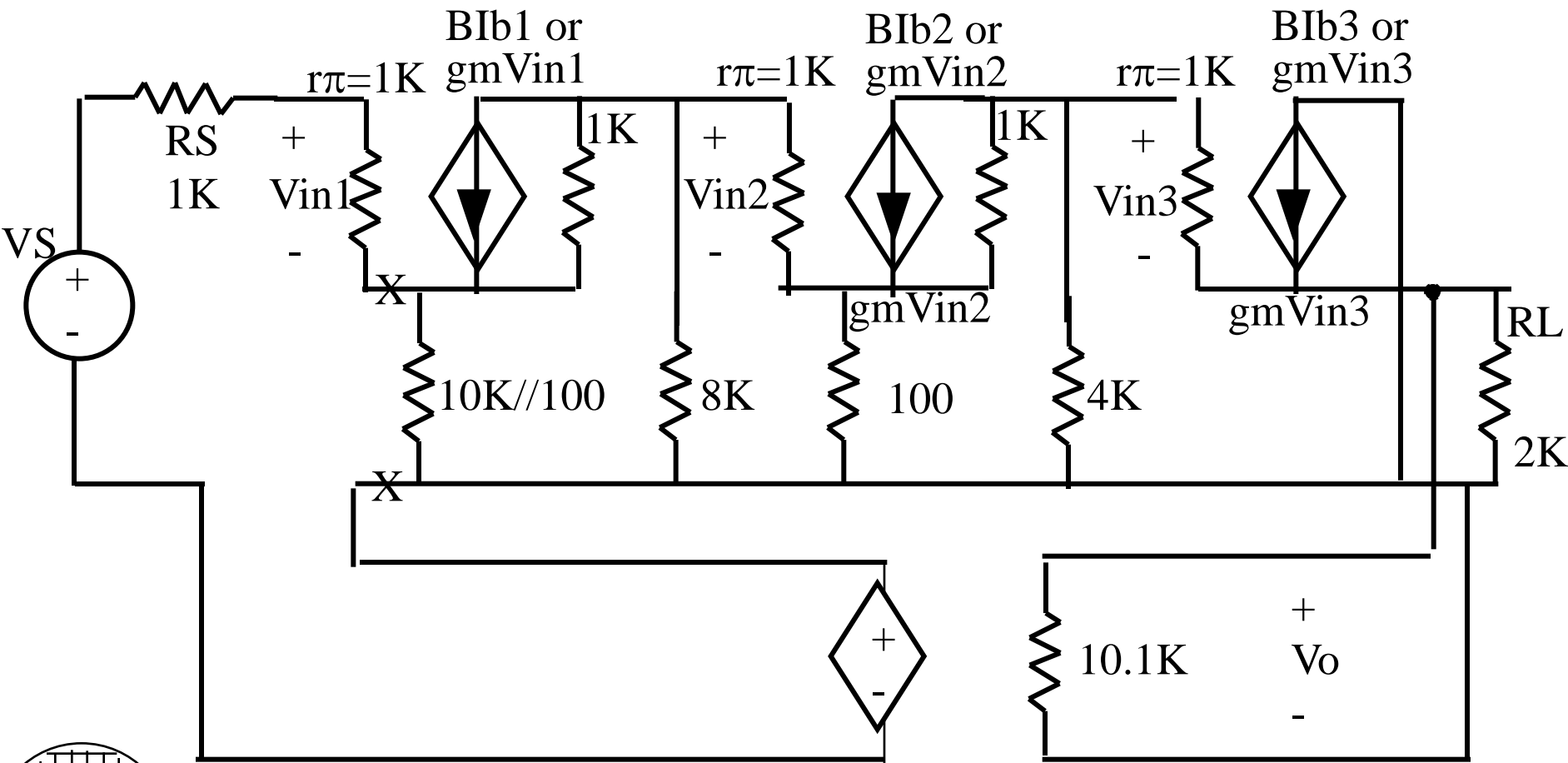

## *HOMWORK PROBLEM 8 SOLUTION*

Finally we have an ac equivalent circuit where the “A” block and “B” block are separate and proper mixing and sampling networks exist.

$$h_{11A} = r_{\pi} + (B+1)10K//100 = 12K$$

$$h_{12A} = 0$$

$$h_{22A} = 1/(2K//(r_{\pi}+4K)/(B+1)) = 0.0173$$

$$h_{21A} = 268000$$

$$h_{21A} = I_2/I_1 \text{ with } V_2 = 0$$

$$I_2 = -(B+1)I_{b3} \text{ so } I_2/I_{b3} = -(B+1) = -101$$

$$I_{b3} = -BI_{b2} (4K/(4K+r_p)) \text{ so } I_{b3}/I_{b2} = -66.7$$

$$I_{b2} = BI_{b1} (8K/(8K+(r_p+(B+1)100))) \text{ so } I_{b2}/I_{b1} = -39.8$$

$$h_{12A} = I_2/I_1 = I_2/I_{b3} \times I_{b3}/I_{b2} \times I_{b2}/I_{b1} = 268000$$

***HOMWORK PROBLEM 8 SOLUTION***

$h_{11B} = 0$  ,already included

$R_S = 1K$

$h_{12B} = 100/(100+10K) = 0.0099$

$h_{21B}$  = neglected compared to  $h_{21}$  of “A” block

$h_{22B} = 1/(10K+100) = 1/10.1K$

$R_L$  = infinite, included in “A” block

$$h_{11} = h_{11A} + h_{11B} = 13K$$


$$h_{12} = h_{12A} + h_{12B} = 0 + 0.0099$$

$$h_{21} = h_{21A} + h_{21B} = -268000$$

$$h_{22} = h_{22A} + h_{22B} = 0.0174$$

Exact Gain

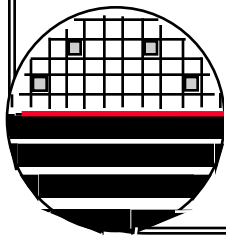
$$A_{v_f} = \frac{\frac{-h_{21}}{h_{11}h_{22}}}{1 + \frac{-h_{12}h_{21}}{h_{11}h_{22}}} = \frac{-\frac{268000}{(13K)(0.0099)}}{1 + \frac{-268000(0.0099)}{(13K)(0.0099)}} = 93$$



**OLD EXAM QUESTION**

Pro 2.


Beta = 150

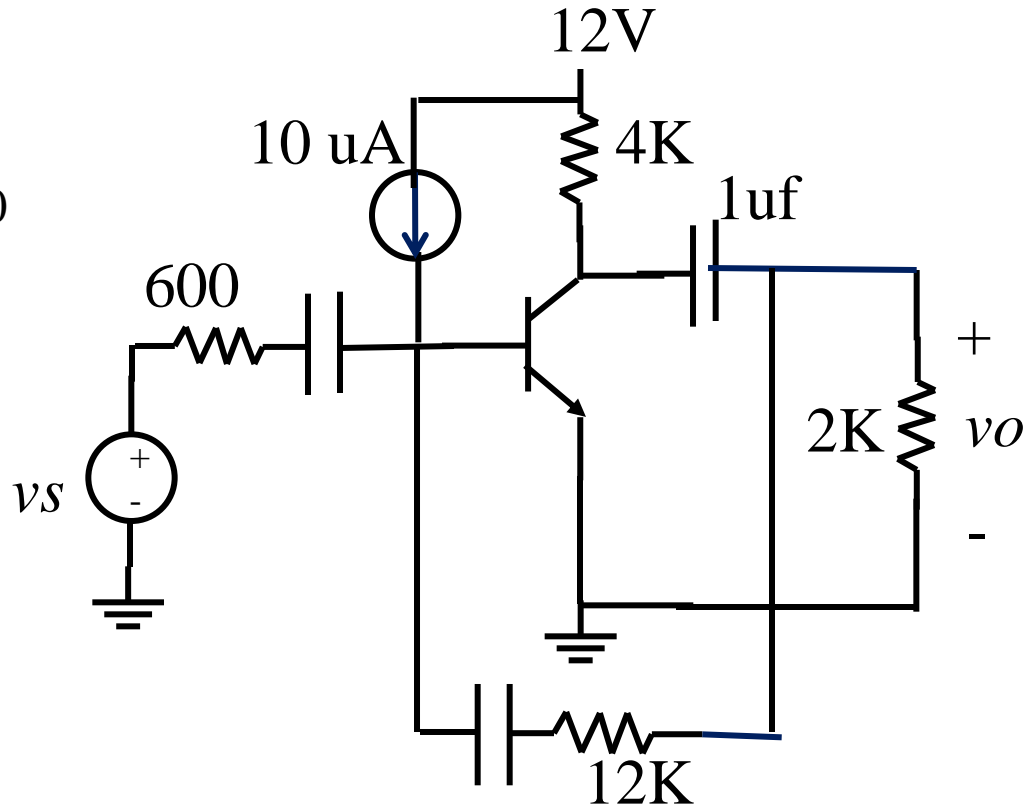

Find Exact Gain With Feedback, Approximate Gain with Feedback, Voltage Gain, Current Gain, Input Resistance

## OLD EXAM QUESTION

Pro 2.

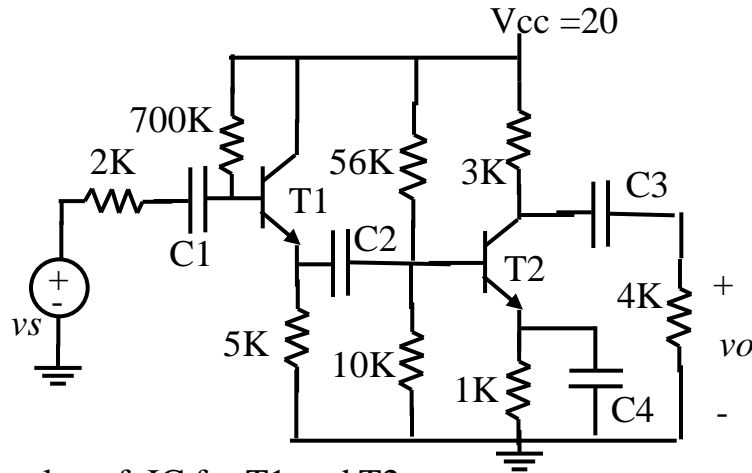

Assume  $\beta = 150$   
 $V_A = 100$

Calculate dc value of  $I_C$  for T1 and T2

Calculate  $g_m$ ,  $r_\pi$  and  $r_o$  for T1 and T2

Calculate the voltage gain  $v_o/v_s$

Pro 3.

For the circuit in problem 2 use a single resistor to provide voltage shunt feedback to stabilize the gain with feedback at  $\sim 40$  V/V. What value of feedback resistor should be used and show how you would connect it by adding it to the schematic of problem 2.