

**ROCHESTER INSTITUTE OF TECHNOLOGY  
MICROELECTRONIC ENGINEERING**

# Power Conditioning Electronics

**Dr. Lynn Fuller**

Webpage: <http://people.rit.edu/lffeee>

Microelectronic Engineering

Rochester Institute of Technology

82 Lomb Memorial Drive


Rochester, NY 14623-5604

Tel (585) 475-2035

Fax (585) 475-5041

Email: [Lynn.Fuller@rit.edu](mailto:Lynn.Fuller@rit.edu)

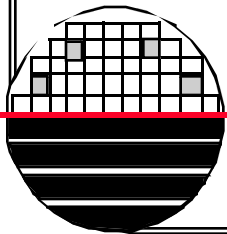Department webpage: <http://www.microe.rit.edu>



*OUTLINE*

Introduction


Power Conditioning

Voltage Regulators

Analog Switches

Two Phase Clocks


Voltage Inverters, Doublers, Tripler's

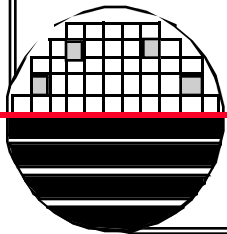
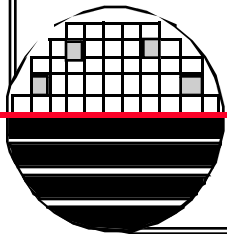
### *INTRODUCTION*


The design of microsystems involves the integration of MEMS, on chip custom integrated circuits, off chip electronics, such as power supply chips, microcontrollers and communication components. The integration is often done at the printed circuit board (PCB) level.

This document will look at the power management electronics used in these systems.




*MICROSYSTEM*

Multi-Sensor MEMs Chip

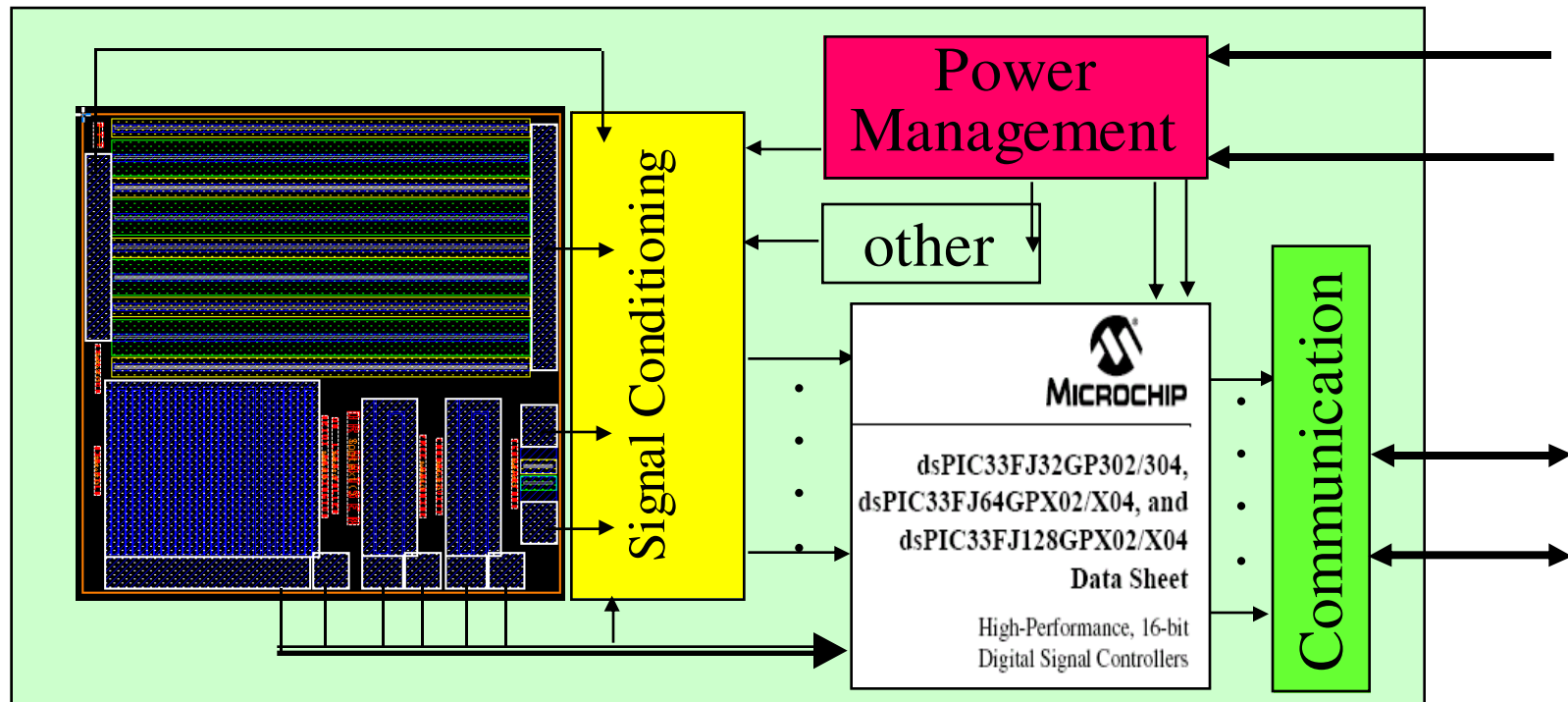



Micro Controller

Signal Conditioning  
Electronics

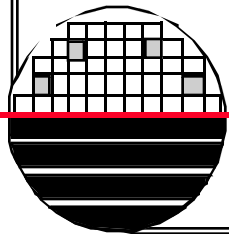


**POWER CONDITIONING EXAMPLE**

Unregulated  
9 to 24 volts DC

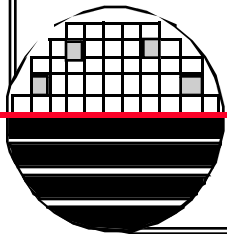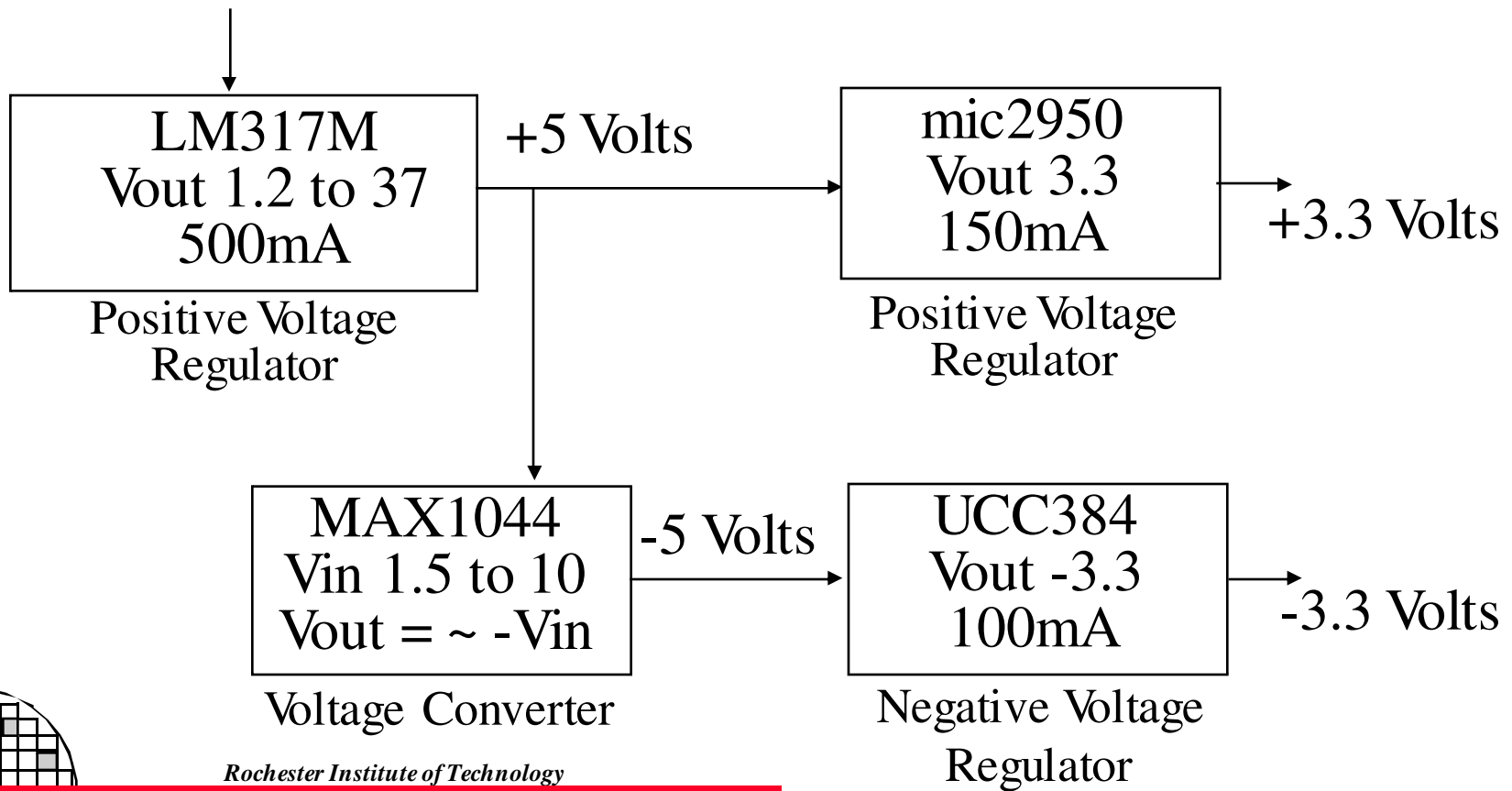


**BASIC VOLTAGE REGULATOR**

Voltage Regulator

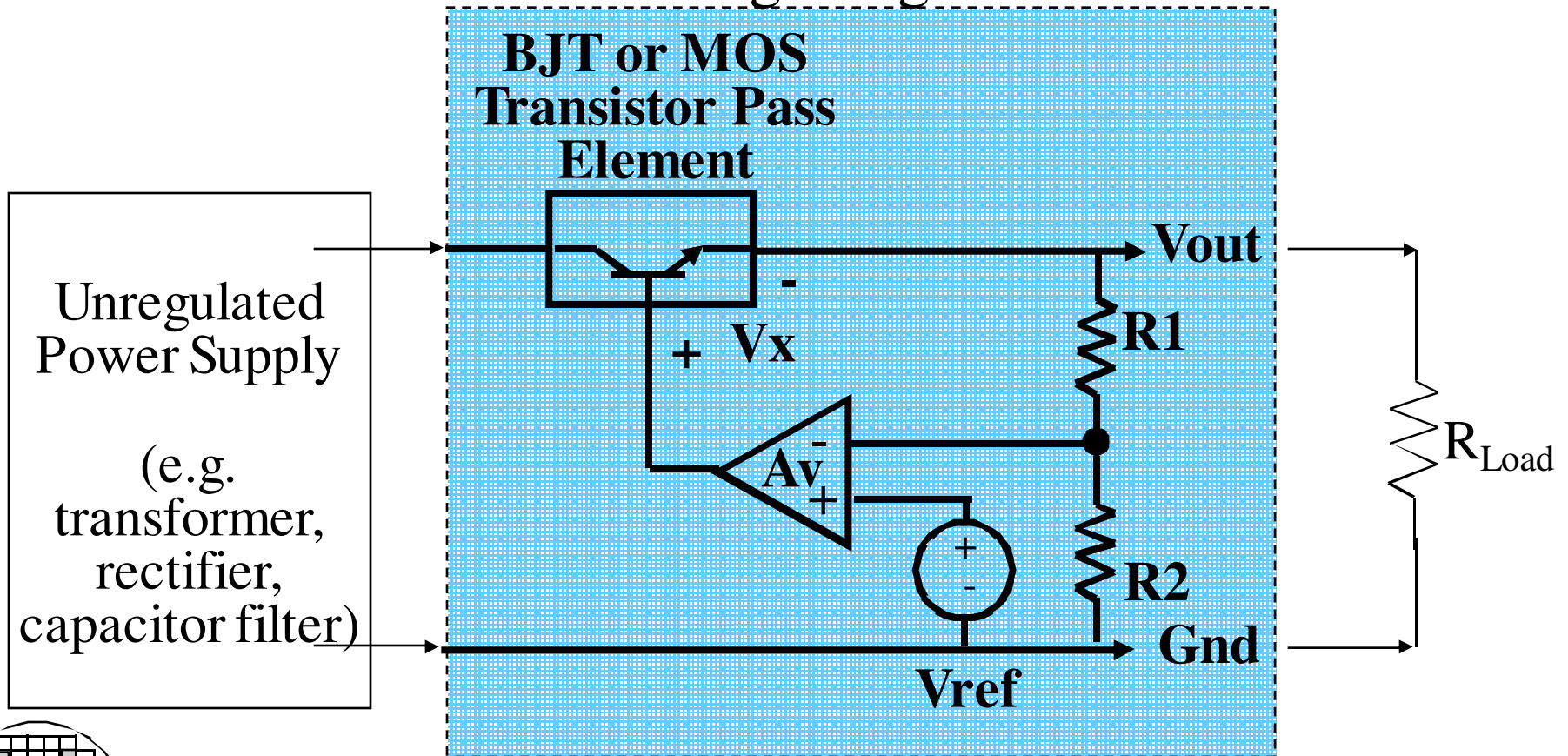


$$V_{out} = V_{ref}(1 + R_1/R_2)$$

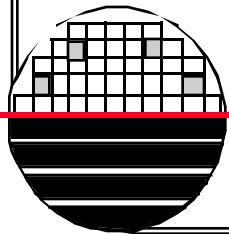


**POWER SUPPLY COMPONENTS**

Description	Digikey Part Number	Package	~Price
POS Lin Regulator Variable	LM317MBSTT3GOS CT-ND	SOT-223	\$0.72
POS Lin Regulator 3.3 Volt	576-1151-ND	8-SOIC	\$1.11
Voltage Converter CMOS SW-CAP	MAX1044CPA+-ND	8-DIP	\$2.68
Voltage Converter CMOS SW-CAP	MAX1044CSA+-ND	8-SOIC	\$3.26
NEG Lin Regulator	296-11417-5-ND	8-SOIC	\$5.60

8-DIP

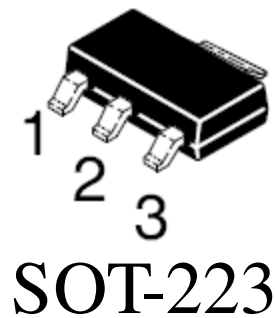


SOT-223

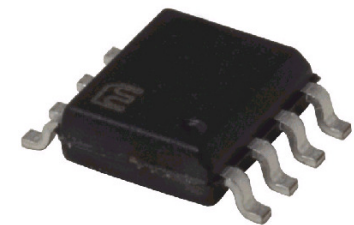


8-SOIC

**VOLTAGE REGULATOR**

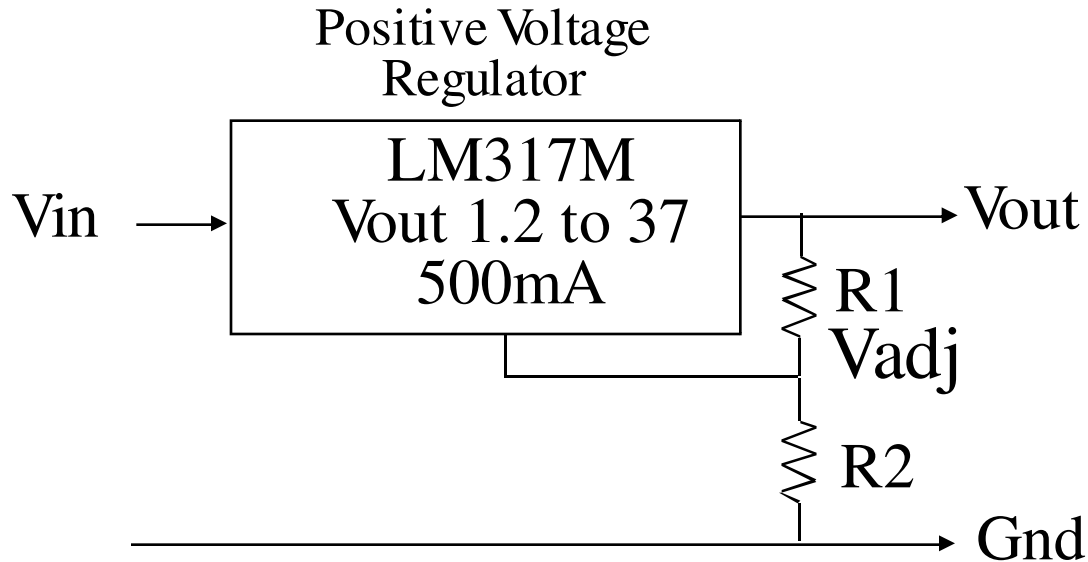

$$V_{out} = 1.25(1 + R2/R1)$$

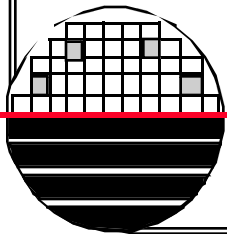
Note: see data sheets for [LM317M-D.pdf](#)  
the reference is between Vout and Vadj  
not between Vadj and ground.






**VOLTAGE REGULATOR ( $V_{ref}$  to  $V_{out}$  not to ground)**

Voltage Regulator

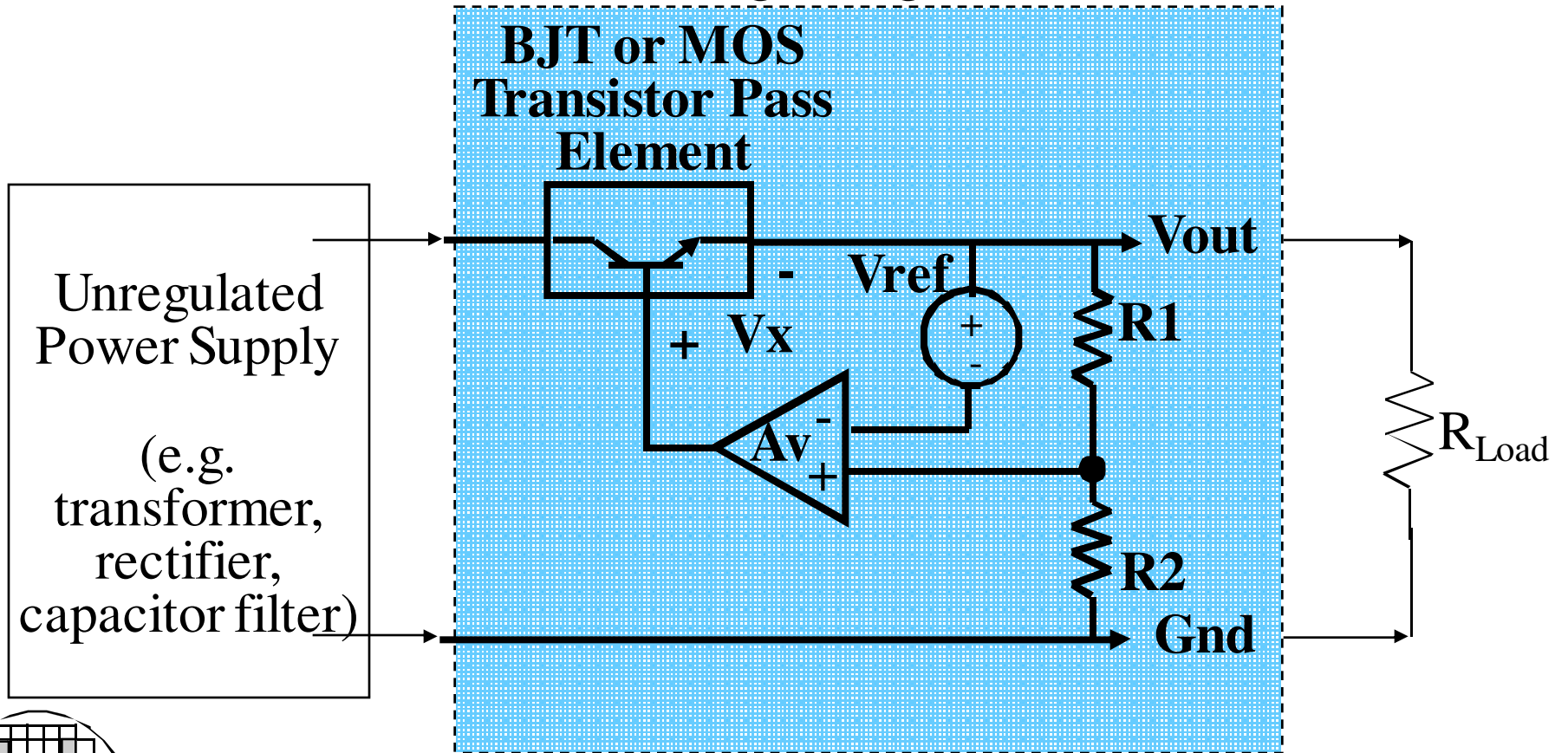

$$V_{out} = V_{ref}(1 + R_2/R_1)$$

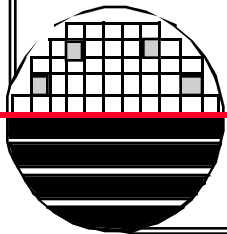



# NEGATIVE VOLTAGE REGULATOR

UCC284-5, UCC284-12, UCC284-ADJ, UCC384-5, UCC384-12, UCC384-ADJ  
 LOW-DROPOUT 0.5-A NEGATIVE LINEAR REGULATOR


SLUS234D – JANUARY 2000 – REVISED FEBRUARY 2002

functional block diagram



$$V_{out} = V_{ref}(1 + R1/R2)$$

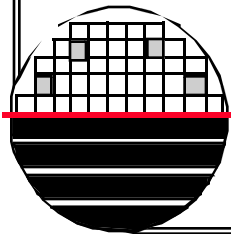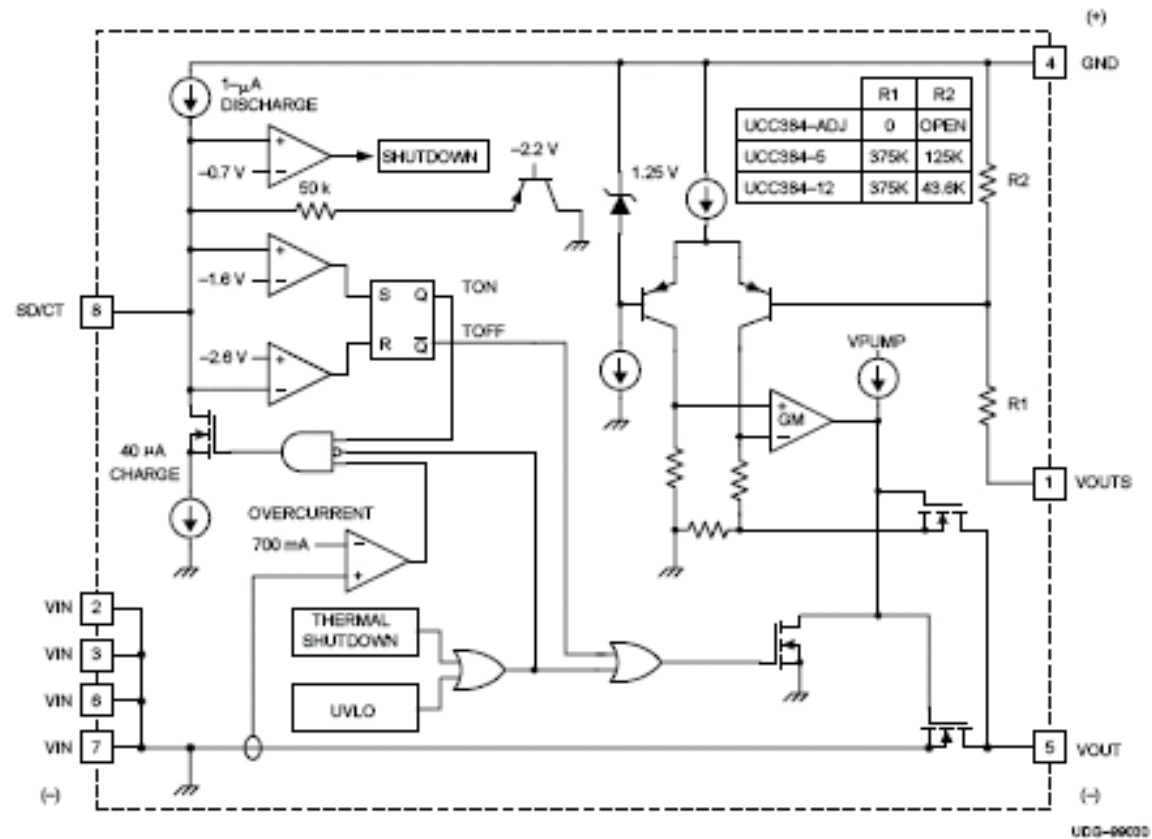



**SWITCHED CAPACITOR VOLTAGE TRIPLER**

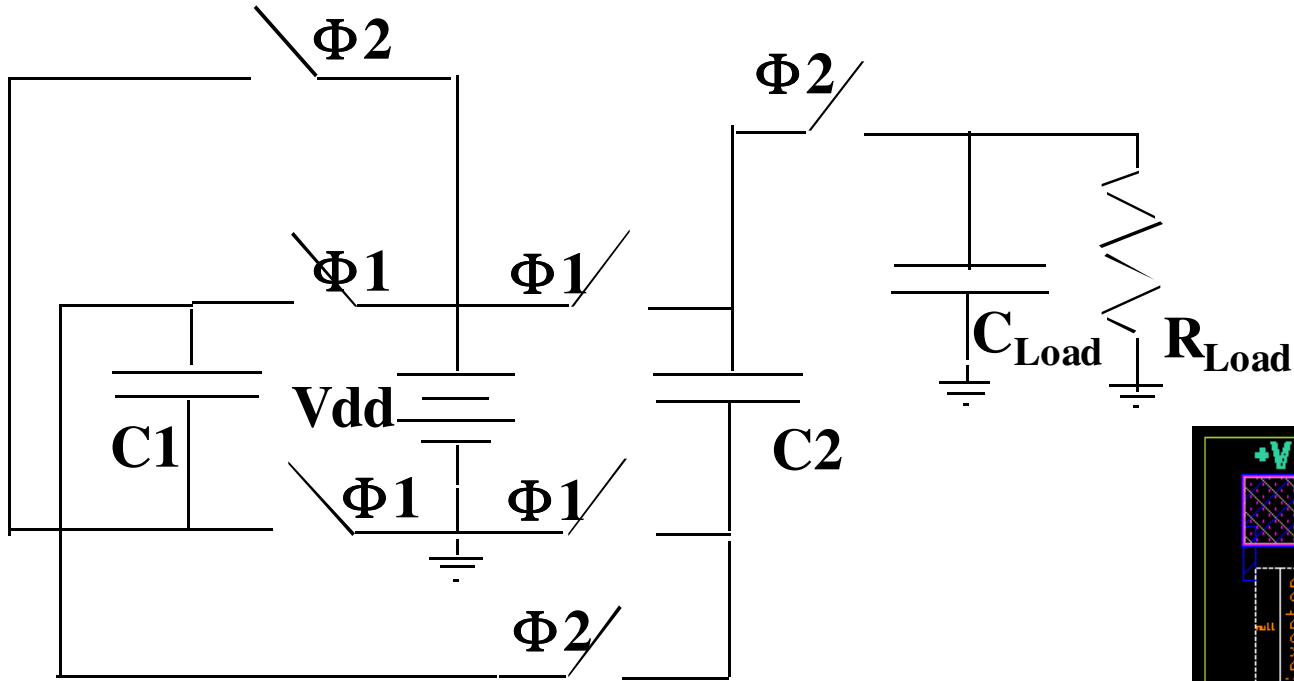


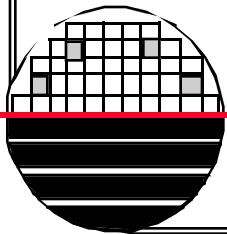
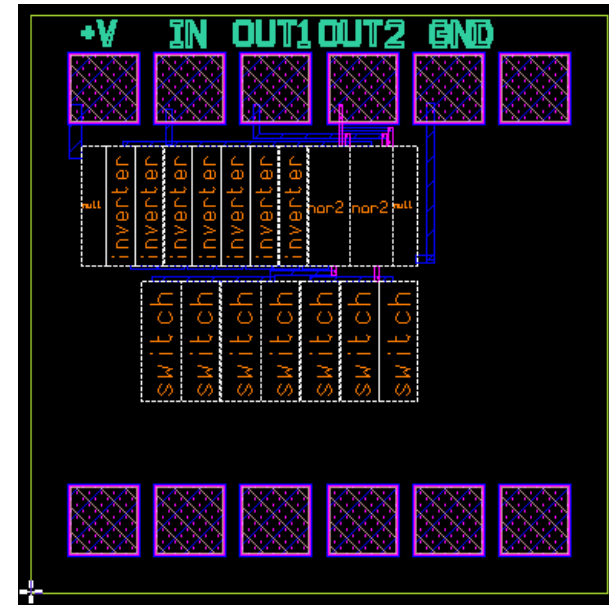
When  $\phi_1$  is high switches put  $C_1$  and  $C_2$  in parallel with  $V_{dd}$ . When  $\phi_2$  is high switches put  $C_1$ ,  $C_2$  and  $V_{dd}$  in series, tripling the voltage to the load.





**TWO PHASE NON OVERLAPPING CLOCK**

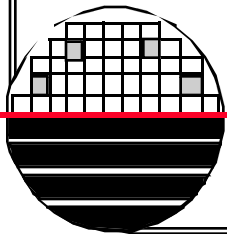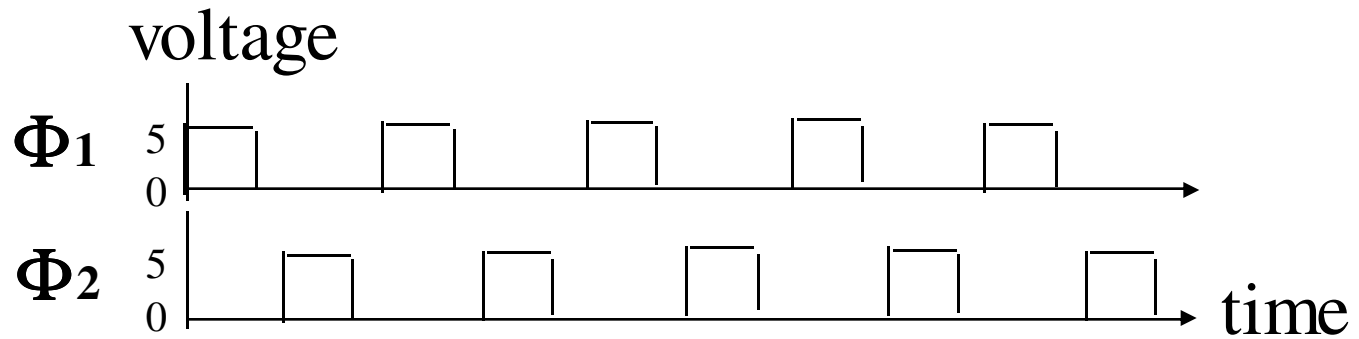

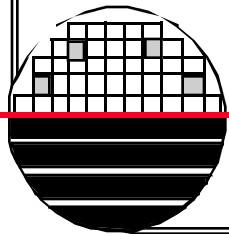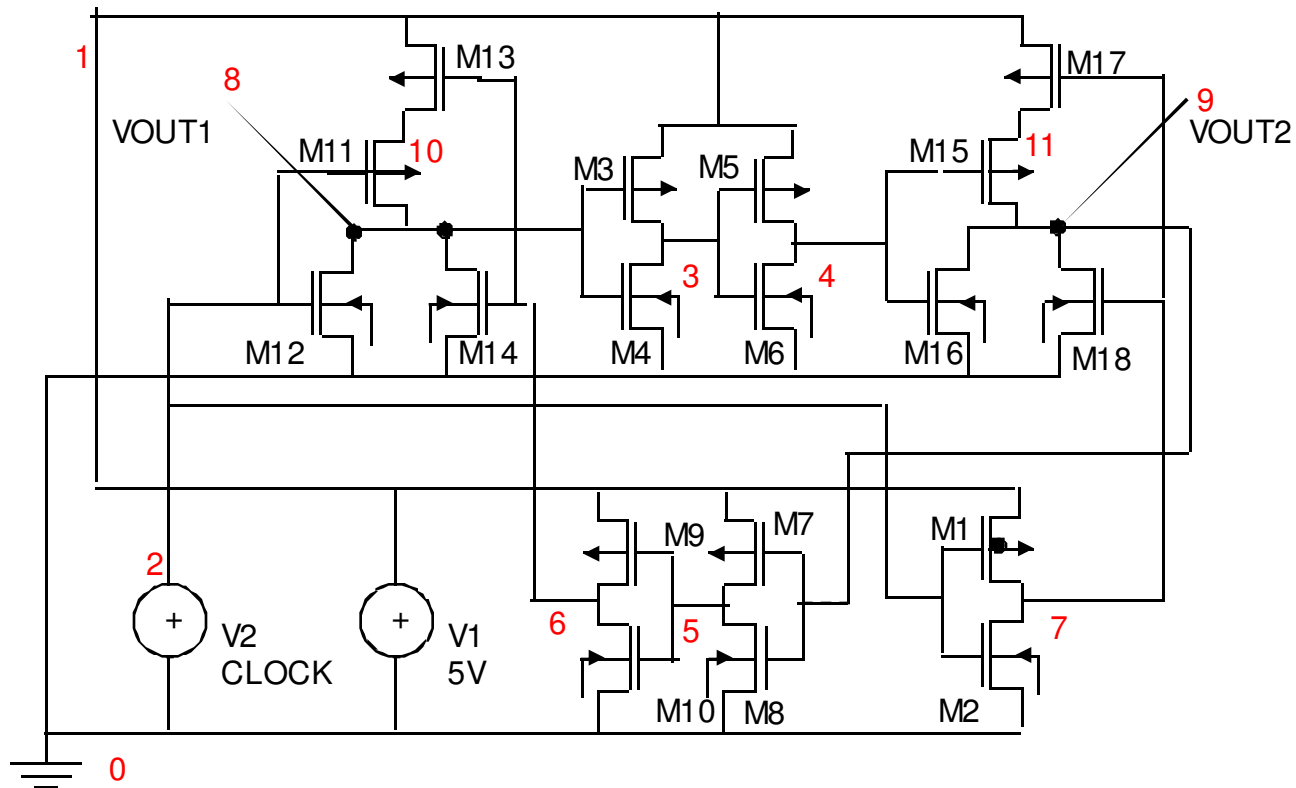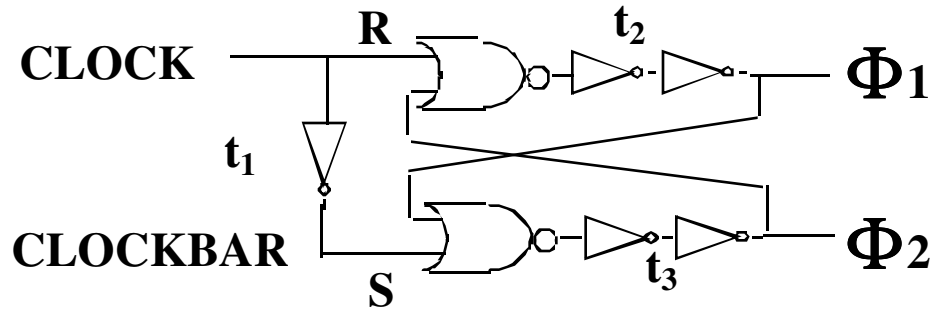**VERSION 2 OF TWO PHASE NON OVERLAPPING CLOCK**






**WINSPICE SIMULATION FOR VERSION TWO**

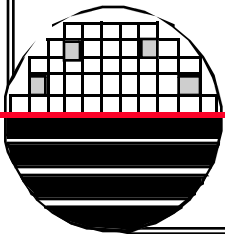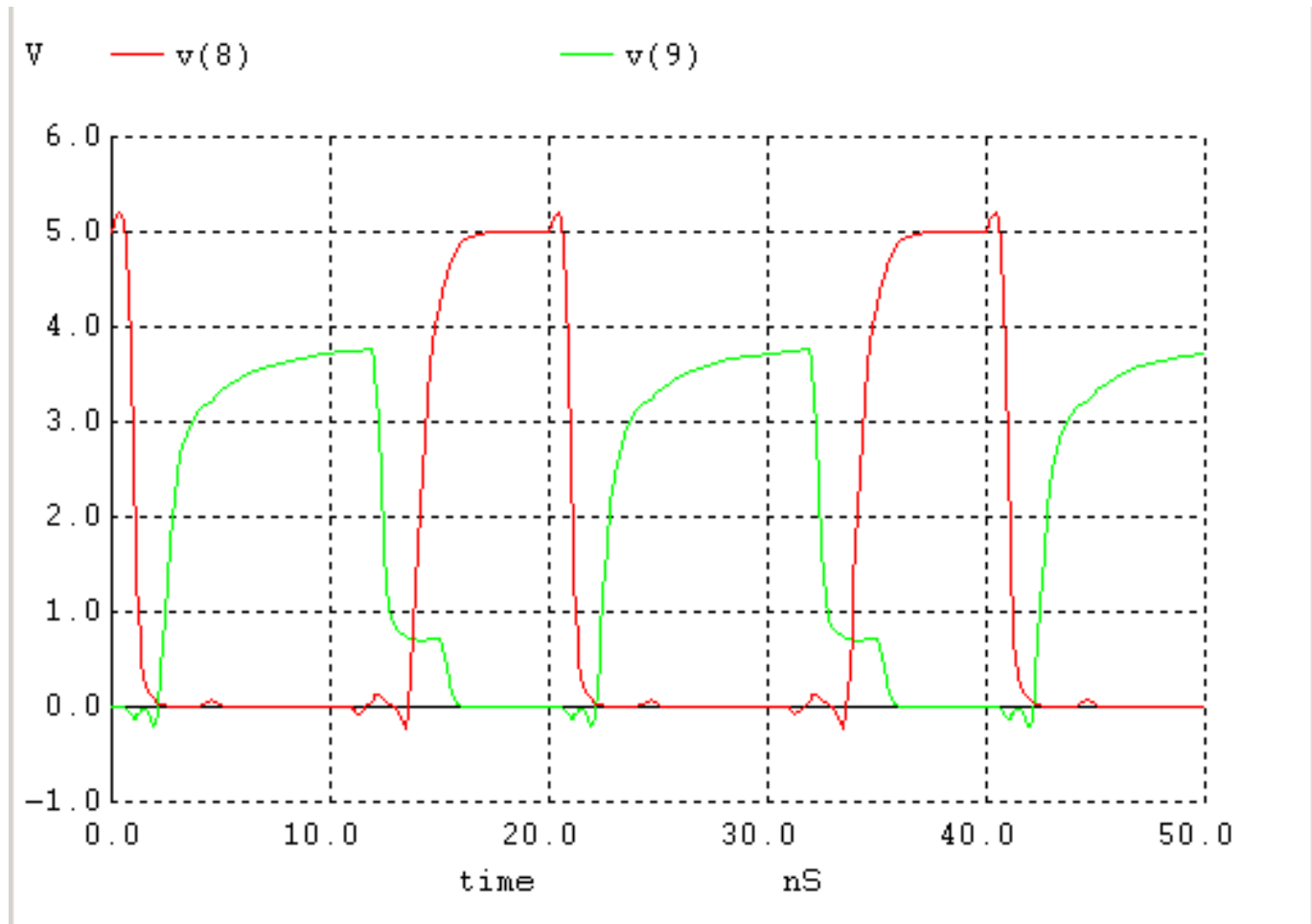


Rochester Institute of Technology  
Microelectronic Engineering

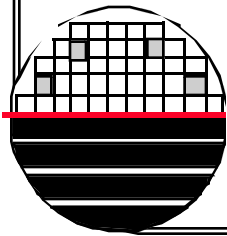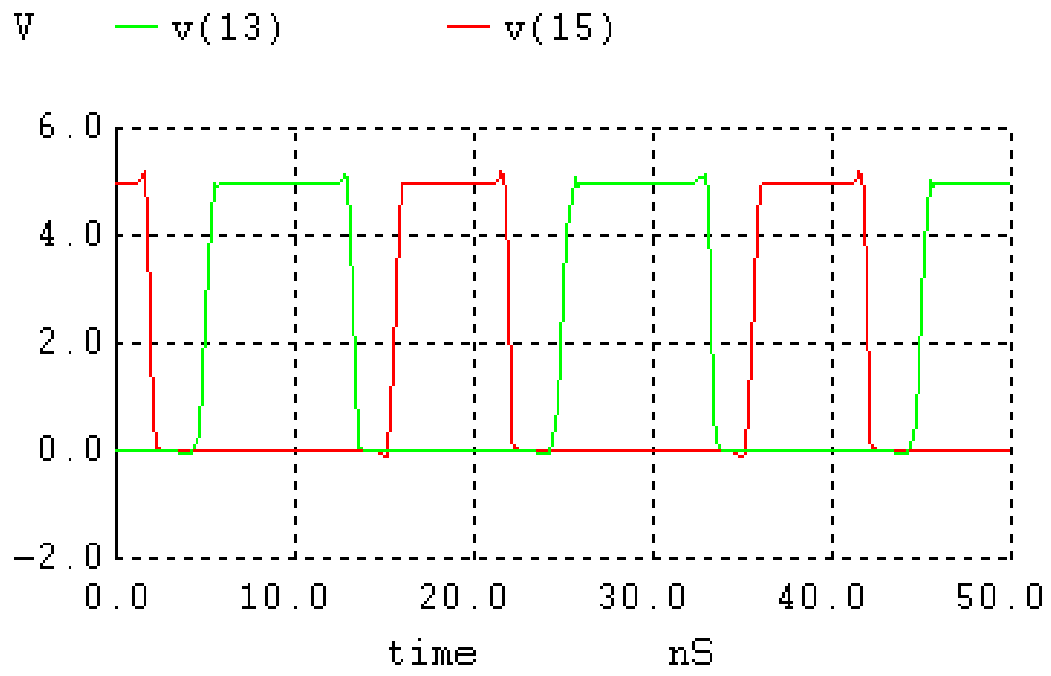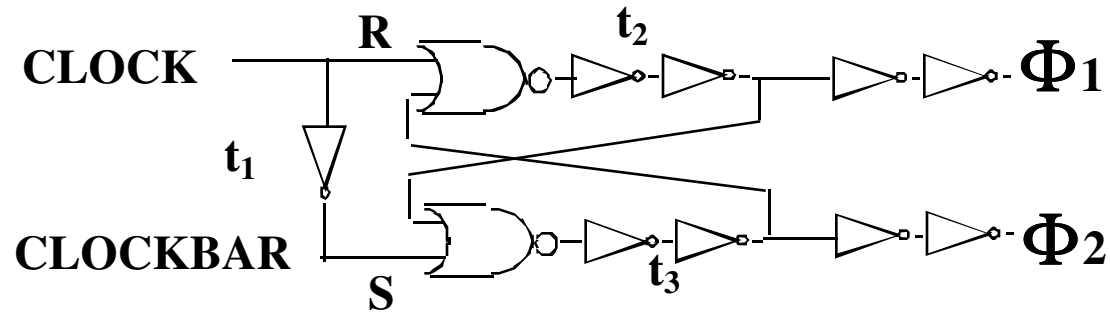**WINSPICE SIMULATION FOR VERSION TWO + BUFFERS**




LAYOUT FOR TWO PHASE CLOCK

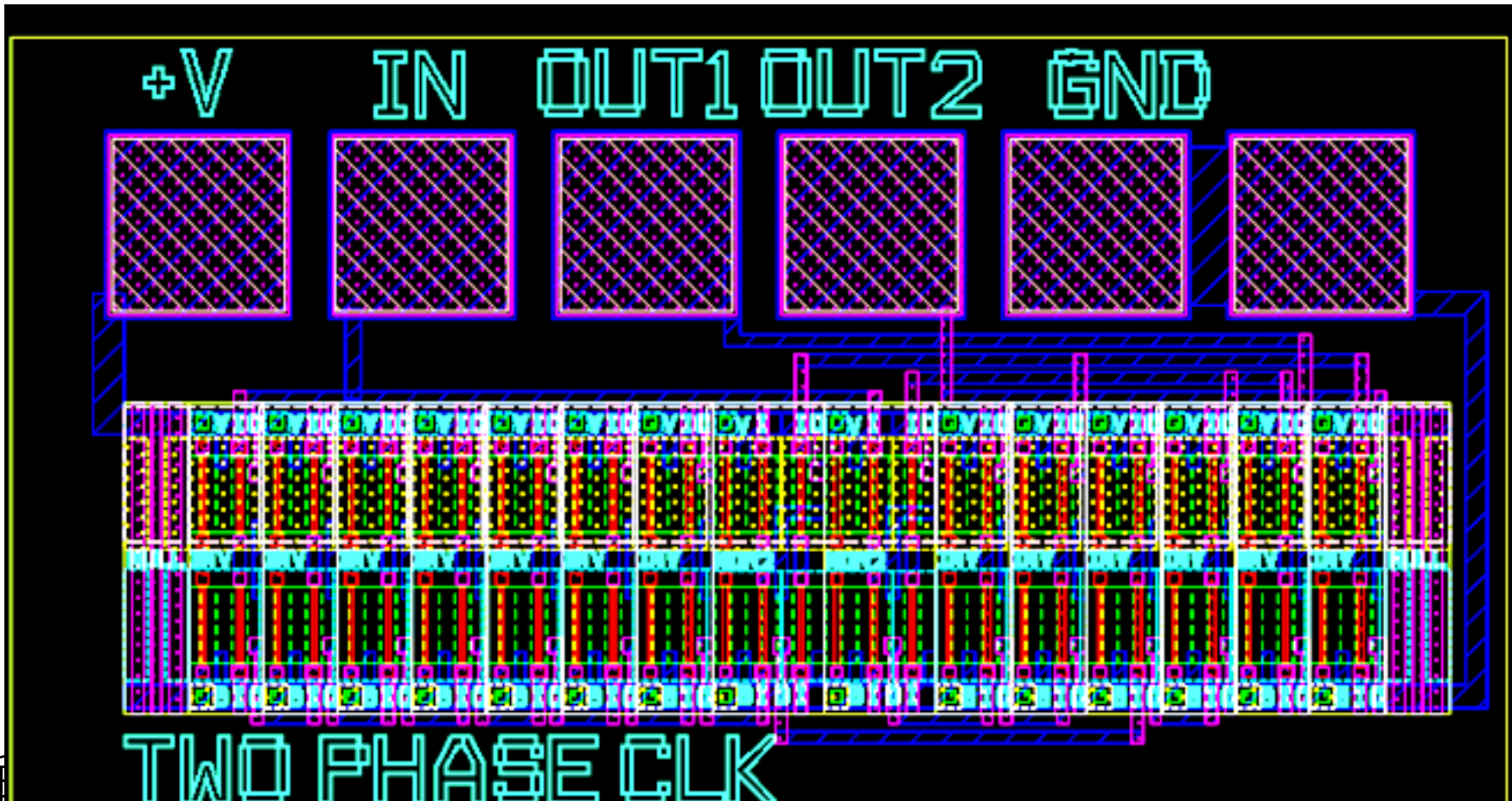


Rochester Institute of Technology  
Microelectronic Engineering






***ANALOG SWITCHES***

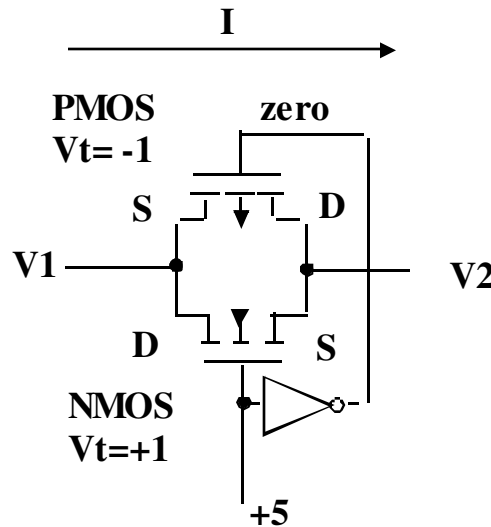

For current flowing to the right (ie  $V1 > V2$ ) the PMOS transistor will be on if  $V1$  is greater than the threshold voltage, the NMOS transistor will be on if  $V2$  is  $< 4$  volts. If we are charging up a capacitor load at node 2 to 5 volts, initially current will flow through NMOS and PMOS but once  $V2$  gets above 4 volts the NMOS will be off. If we are trying to charge up  $V2$  to  $V1 = +1$  volt the PMOS will never be on. A complementary situation occurs for current flow to the left. Single transistor switches can be used if we are sure the  $V_{gs}$  will be more than the threshold voltage for the specific circuit application. (or use larger voltages on the gates)

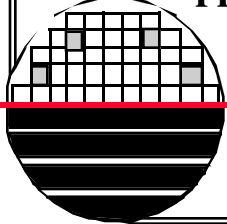

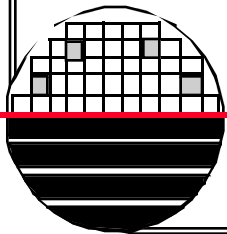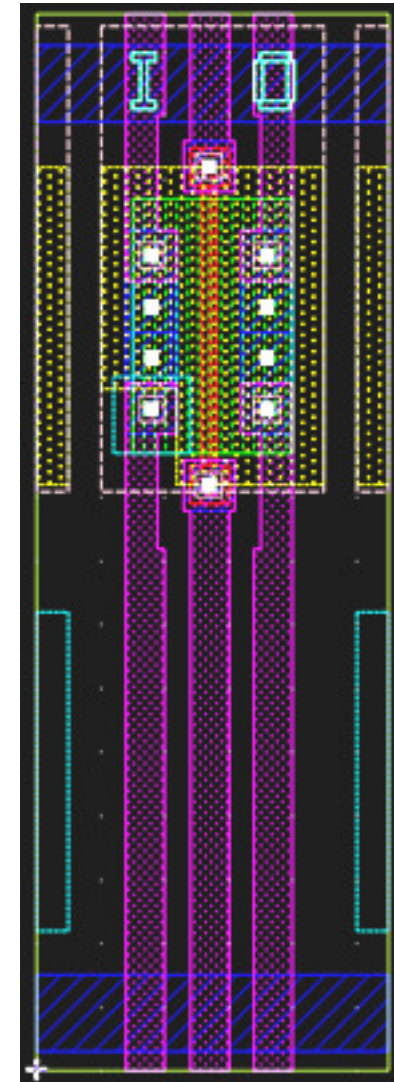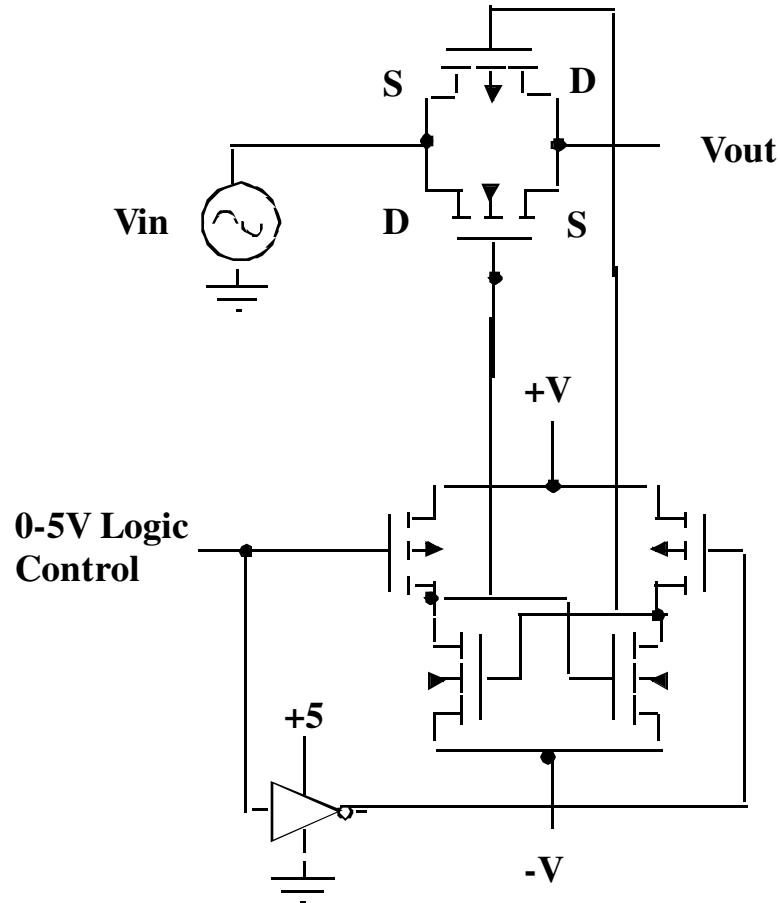
**(+V to -V) ANALOG SWITCH WITH (0 to 5 V) CONTROL**




# SWITCHED CAPACITOR VOLTAGE CONVERTER

- Portable Telephones
- Op-Amp Power Supplies
- EIA/TIA-232E and EIA/TIA-562 Power Supplies
- Data-Acquisition Systems
- Hand-Held Instruments
- Panel Meters

Typical Operating Circuit

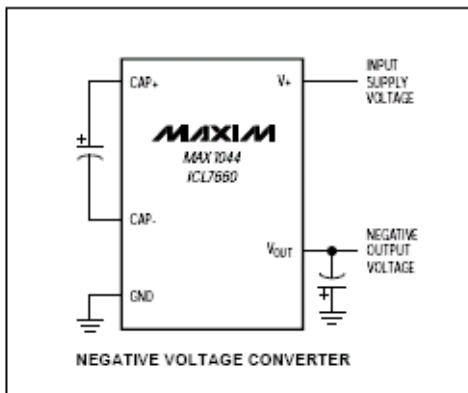


Pin Configurations

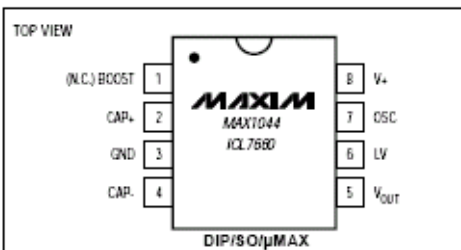

MAX1044CSA+-ND  
CMOS  
1.5 to 10 Volt Supply

Package Information

DIM	INCHES		MILLIMETERS	
	MIN	MAX	MIN	MAX
A	0.036	0.044	0.91	1.11
A1	0.004	0.008	0.10	0.20
B	0.010	0.014	0.25	0.36
C	0.005	0.007	0.13	0.18
D	0.116	0.120	2.95	3.05
E	0.116	0.120	2.95	3.05
e	0.0256		0.65	
H	0.188	0.196	4.78	5.03
L	0.016	0.026	0.41	0.66
α	0°	6°	0°	6°

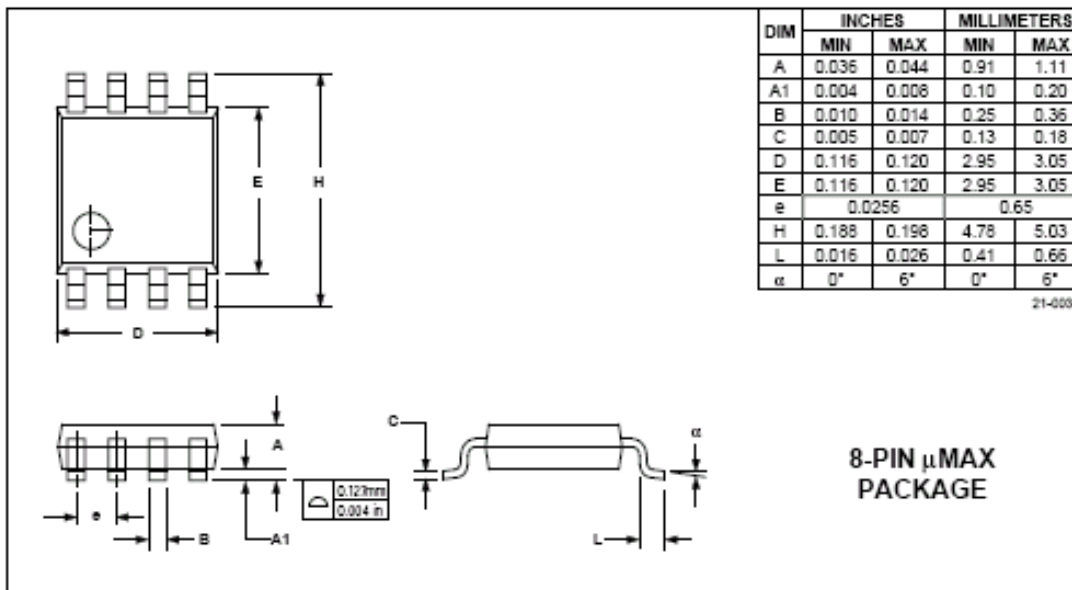


8-PIN μMAX PACKAGE

Maxim cannot assume responsibility for use of any circuitry other than circuitry entirely embodied in a Maxim product. No circuit patent licenses are implied. Maxim reserves the right to change the circuitry and specifications without notice at any time.

12 Maxim Integrated Products, 120 San Gabriel Drive, Sunnyvale, CA 94086 (408) 737-7600

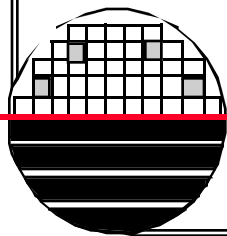© 1994 Maxim Integrated Products Printed USA MAXIM is a registered trademark of Maxim Integrated Products.



Rochester Institute of  
Microelectronic Engi

**MAX1044 VOLTAGE CONVERTER**

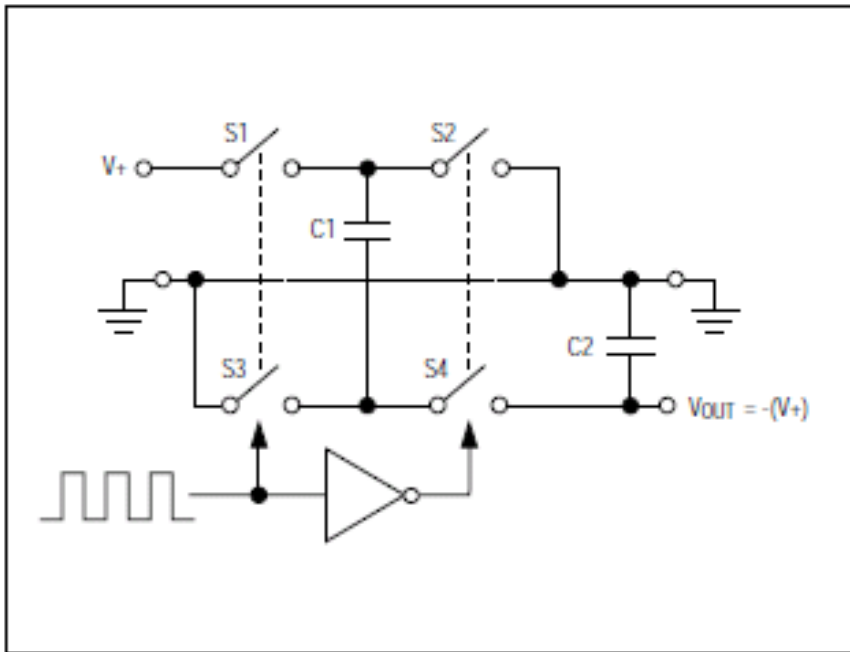


Figure 2. Ideal Voltage Inverter



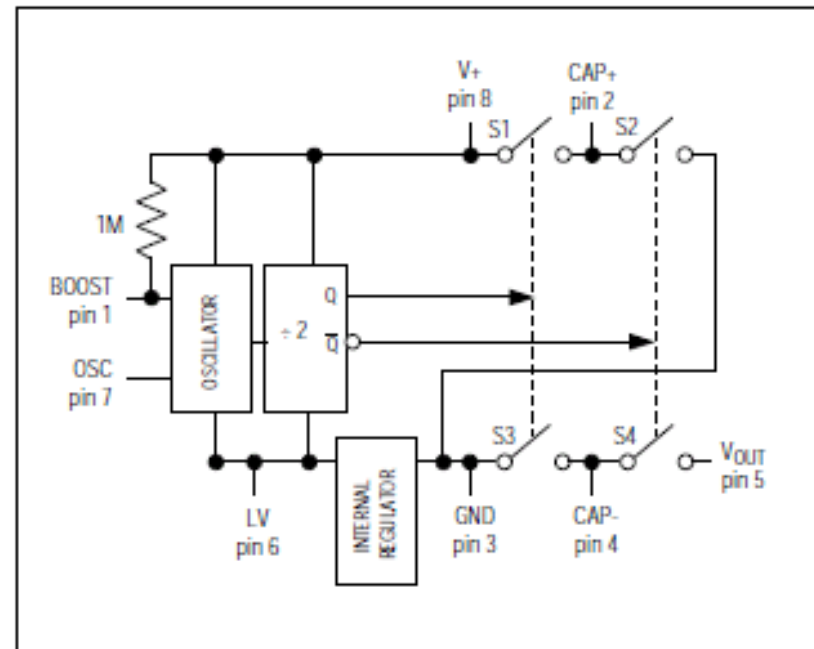


Figure 4. MAX1044 and ICL7660 Functional Diagram

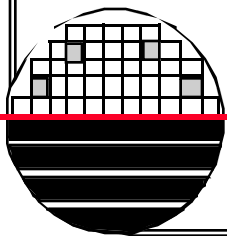

*REFERENCES*

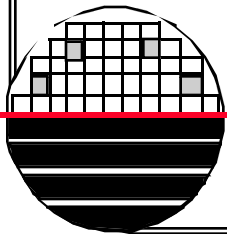1. Dr. Fullers webpage <http://people.rit.edu/lffeee>



***HOMEWORK – POWER CONDITIONING***

1. Sketch a schematic showing battery, switches and capacitors of the positive-to-negative switched capacitor voltage converter.
2. Design a 6 volt regulator using a 741 op amp and a BJT transistor.
3. Do a SPICE simulation of the two phase clock version two with buffers shown in these lecture notes.

