

ROCHESTER INSTITUTE OF TECHNOLOGY
MICROELECTRONIC ENGINEERING

SPICE Examples

Dr. Lynn Fuller

Electrical and Microelectronic Engineering

Rochester Institute of Technology

82 Lomb Memorial Drive

Rochester, NY 14623-5604


Tel (585) 475-2035

Fax (585) 475-5041

Dr. Fuller's Webpage: <http://people.rit.edu/lffeee>


Email: Lynn.Fuller@rit.edu

 Dept Webpage: <http://www.microe.rit.edu>




ADOBE PRESENTER

 This PowerPoint module has been published using Adobe Presenter. Please click on the **Notes** tab in the left panel to read the instructors comments for each slide. Manually advance the slide by clicking on the **play** arrow or pressing the **page down** key.



OUTLINE

 Introduction
Text Input Files
DC, Transient, AC Analysis
LC Filter
Inverters, NMOS, PMOS, CMOS
 Rise Time, Fall Time, Gate Delay
 Ring Oscillator
Combinatorial Logic, NOR, 4 to 1 MUX
Inverter with Hysteresis
Oscillators
2 Phase Non Overlapping Clocks
Analog Switch
Op Amps, CMOS, BJT
Waveform Generator
Operational Transconductance Amplifier (OTA)
AM Receiver
References
Homework



INTRODUCTION

SPICE (Simulation Program for Integrated Circuit Engineering) is a general-purpose circuit simulation program for non-linear DC, non-linear transient, and linear AC analysis. Circuits may contain resistors, capacitors, inductors, mutual inductors, independent voltage and current sources, four types of dependent sources, transmission lines, switches, and several semiconductor devices: including diodes, BJTs, JFETs, MESFETs, and MOSFETs. Circuits with large numbers of all types of components can be simulated.

SPICE input files and output files are simple text files (e.g. name.txt)

Input files include a TITLE, circuit description NET LIST, analysis directives (COMMANDS), and lists of other text files to include (INC) such as model libraries (LIB) and an END command.

INTRODUCTION

PSpice Lite 9.2 is one of the OrCAD family of products, from Cadence Design Systems, Inc., offering a complete suite of electronic design tools. It is free and includes limited versions of OrCAD Capture, for schematic capture, PSpice for analog circuit simulation and Pspice A/D for mixed analog and digital circuit simulation. PSpice Lite 9.2 is limited to 64 nodes, 10 transistors, two operational amplifiers and 65 primitive digital devices. See page 35 (xxxv) of the PSpice Users Guide.

LT SPICE – is a free SPICE simulator with schematic capture from Linear Technology. It is quite similar to PSpice Lite but is not limited in the number of devices or nodes. Linear Technology (LT) is one of the industry leaders in analog and digital integrated circuits. Linear Technology provides a complete set of SPICE models for LT components.

CREATING THE INPUT FILE

The input file can be generated from a schematic capture program, or just typed in a text editor such as “Notepad” or “WordPad”

*Simple Resistor Divider


```
R1 1 0 2K
```

```
R2 2 1 3K
```

```
V1 2 0 DC 5
```

```
.DC V1 0 5 .1
```


```
.END
```

 

LTSPICE USING INPUT FILE INSTEAD OF SCHEMATIC

```
Draft3.asc  
  
.include C:\SPICE\SimpleExample.txt  
.op
```

 
.op is a spice directive to do DC operating point analysis



```
SimpleExample.txt - Notepad  
File Edit Format View Help  
*DR FULLER - SIMPLE EXAMPLE TITLE  
* THE FIRST LINE IS THE TITLE  
* LINES THAT START WITH * ARE COMMENT LINES AND DO NOTHING  
* UPPER AND lower case text ARE TREATED THE SAME  
* CIRCUIT IS DESCRIBED BELOW (NET LIST)  
R1 1 0 2K ; resistor R1 between node 1 and zero has value 2000 ohms  
R2 2 1 3K  
V1 2 0 DC 5 ; voltage source V1 is a DC source of 5 volts  
*  
* REQUESTED ANALYSIS (DIRECTIVES OR COMMANDS)  
.DC V1 0 5 .1 ; find all node voltages and branch currents for V1 starti  
* incrementing by 0.1 volts ending at 5 volts|  
*  
*.INCLUDE File_name.txt ;(none for this example)  
*  
.END
```

*This is a text file located at
C:\SPICE\SimpleExample.txt*


RC DIVIDER CIRCUIT

 

Calculate VC as the voltage V1 is swept from 0 to 3 volts

Change the V1 to a 3 volt pulse function and plot VC versus time.

 Change the voltage V1 to an AC voltage source and plot VC versus frequency




DC SPICE ANALYSIS USING LTSPICE

The screenshot displays the LTSpice IV interface. The top window shows a plot of two voltage signals over time. The x-axis represents time from 0.0V to 3.0V, and the y-axis represents voltage from 0.0V to 3.0V. A blue line, labeled V(n001), shows a linear increase from 0.0V to 3.0V. A green line, labeled V(n002), shows a linear increase from 0.0V to approximately 0.9V. The bottom window shows a circuit schematic with a voltage source V1 (3V), a resistor R1 (20K), a resistor R2 (10K), and a capacitor C1 (1μF). The netlist for the circuit is displayed in the bottom right corner.

```
* C:\Program Files\LTC\LTspiceIV\Draft3.net
R2 N002 0 10K
R1 N002 N001 20K
C1 N002 0 1μ
V1 N001 0 3
.dc v1 0 3 .01
.backanno
.end
```

This net list is automatically generated from the schematic

TRANSIENT ANALYSIS USING LTSPICE

 

`.tran 0 100m 0 startup`

The circuit schematic shows a voltage source V1 connected in series with a resistor R1 (20K). This series combination is connected to a parallel network of a resistor R2 (10K) and a capacitor C1 (1µ). The circuit is powered by a pulse source V1.



`PULSE(0 3 0 2N 2N 25m 50m 2)`

Independent Voltage Source - V1

- Functions:
 - (none)
 - PULSE(V1 V2 Tdelay Trise Tfall Ton Period Ncycles)
 - SINE(Voffset Vamp Freq Td Theta Phi Ncycles)
 - EXP(V1 V2 Td1 Tau1 Td2 Tau2)
 - SFFM(Voff Vamp Fcar MDI Fsig)
 - PWL(t1 v1 t2 v2...)
 - PWL FILE:
- DC Value:
 - DC value:
 - Make this information visible on schematic:
- Small signal AC analysis(AC):
 - AC Amplitude:
 - AC Phase:
 - Make this information visible on schematic:
- Parasitic Properties:
 - Series Resistance[Ω]:
 - Parallel Capacitance[F]:
 - Make this information visible on schematic:
- Parameters:
 - Vinitial[V]:
 - Von[V]:
 - Tdelay[s]:
 - Trise[s]:
 - Tfall[s]:
 - Ton[s]:
 - Tperiod[s]:
 - Ncycles:
- Additional PwL Points:
- Make this information visible on schematic:

Right click on voltage source to get this dialog box

AC ANALYSIS USING LTSPICE

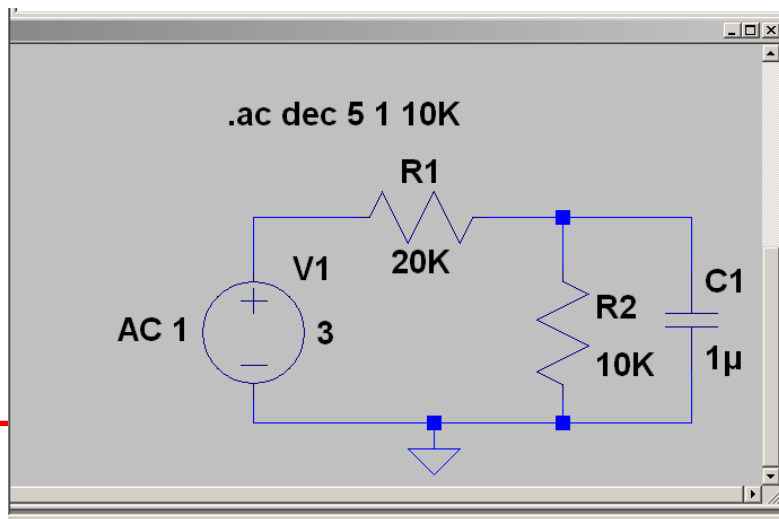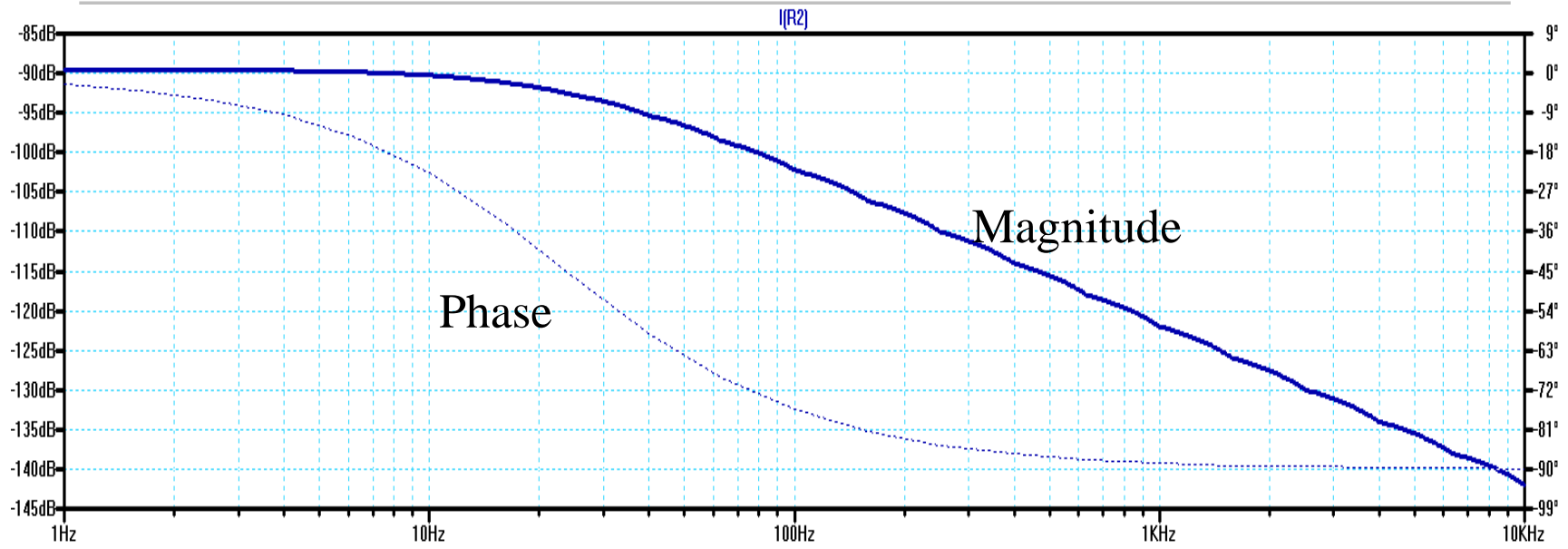

The dialog box for the Independent Voltage Source V1 is shown. It contains the following settings:

- Functions: (none)
- PULSE(V1 V2 Tdelay Trise Tfall Ton Period Ncycles)
- SINE(Voffset Vamp Freq Td Theta Phi Ncycles)
- EXP(V1 V2 Td1 Tau1 Td2 Tau2)
- SFFM(Voff Vamp Fcar MDI Fsig)
- PWL(I1 v1 I2 v2...)
- PWL FILE:

DC Value: DC value: Make this information visible on schematic:

Small signal AC analysis (AC): AC Amplitude: AC Phase: Make this information visible on schematic:



Parasitic Properties: Series Resistance[Ω]: Parallel Capacitance[F]: Make this information visible on schematic:

Additional PwL Points:


Make this information visible on schematic:

Right click on voltage source to get this dialog box

LC FILTER

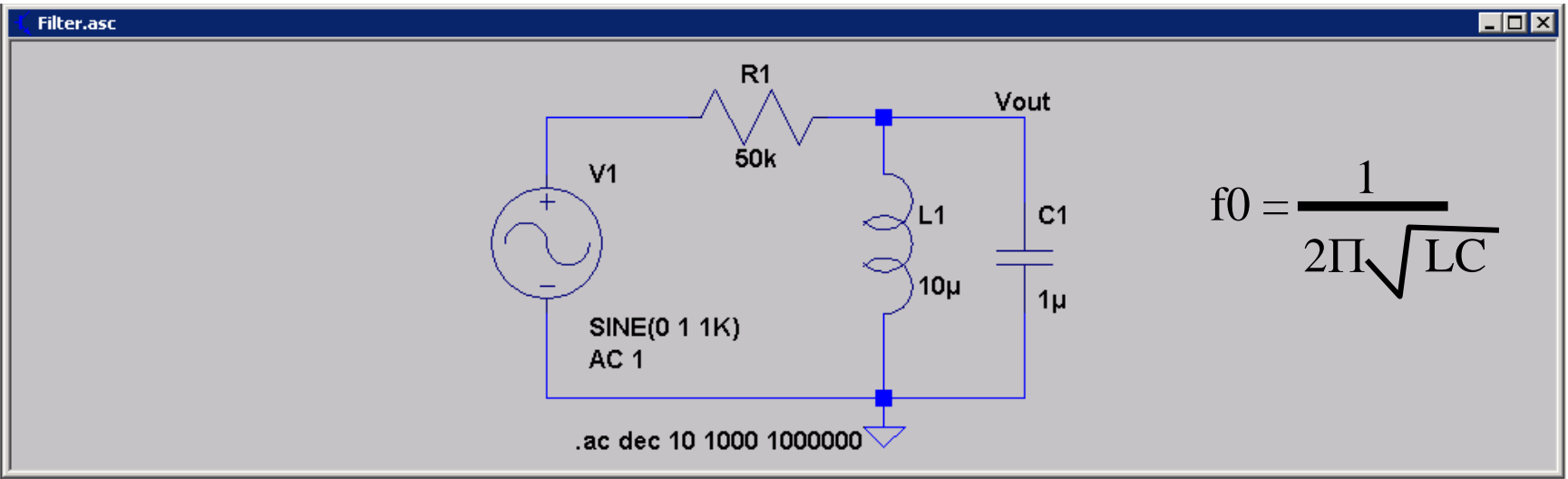 


NMOS INVERTER WITH RESISTER LOAD

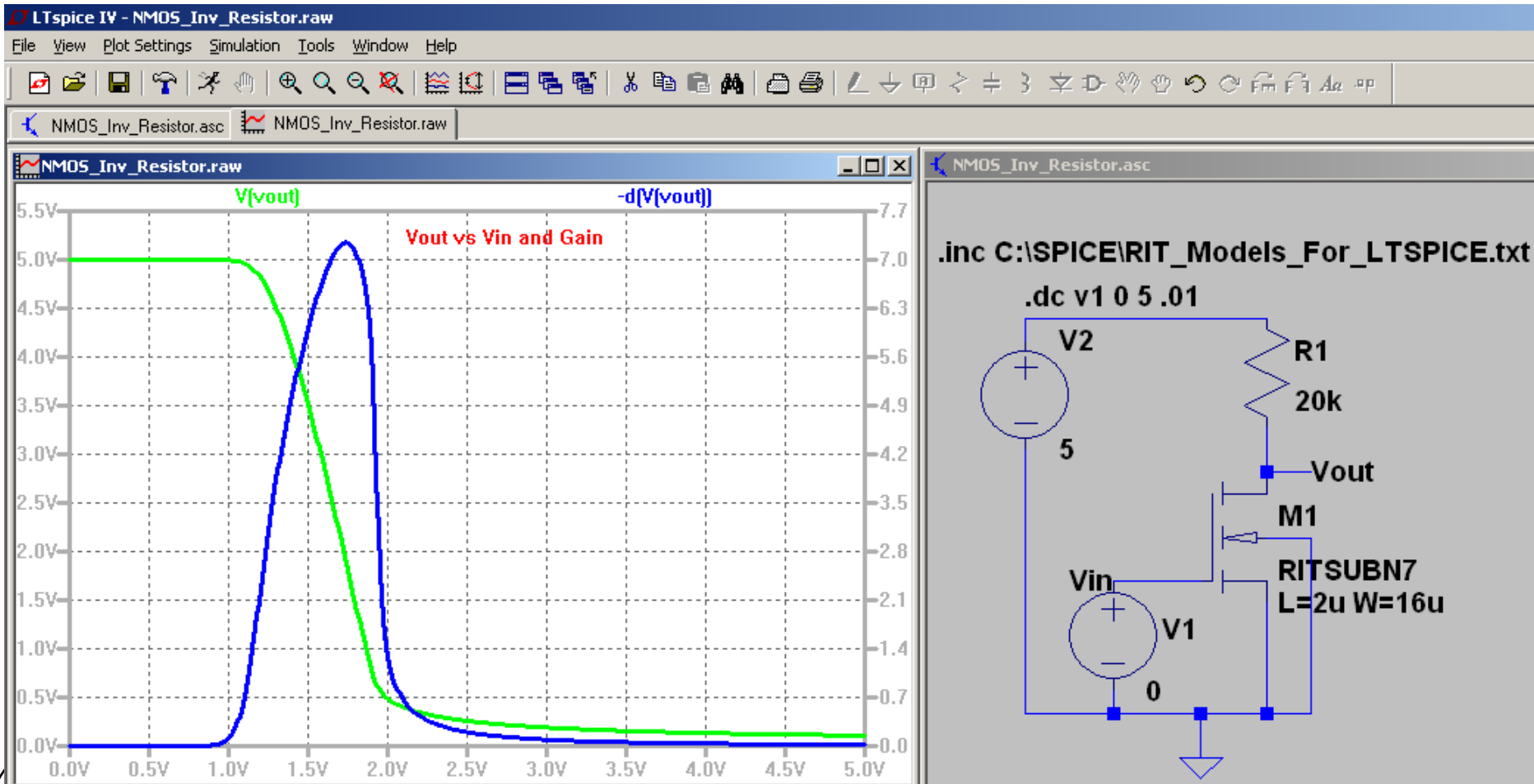


Rochester Institute of Technology
Microelectronic Engineering

NMOS INVERTER RESISTIVE LOADS

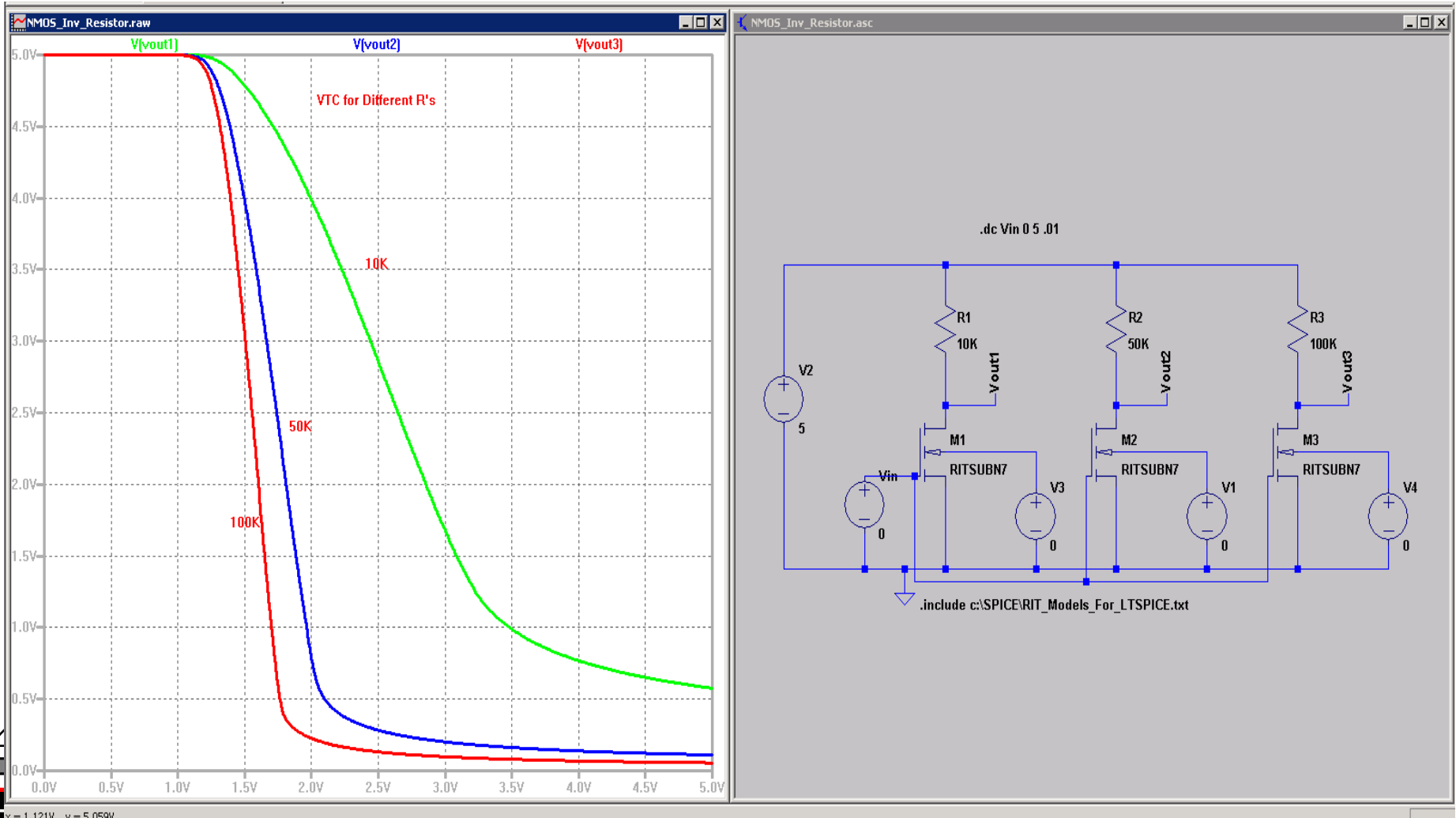

NMOS INVERTER WITH NMOS LOAD

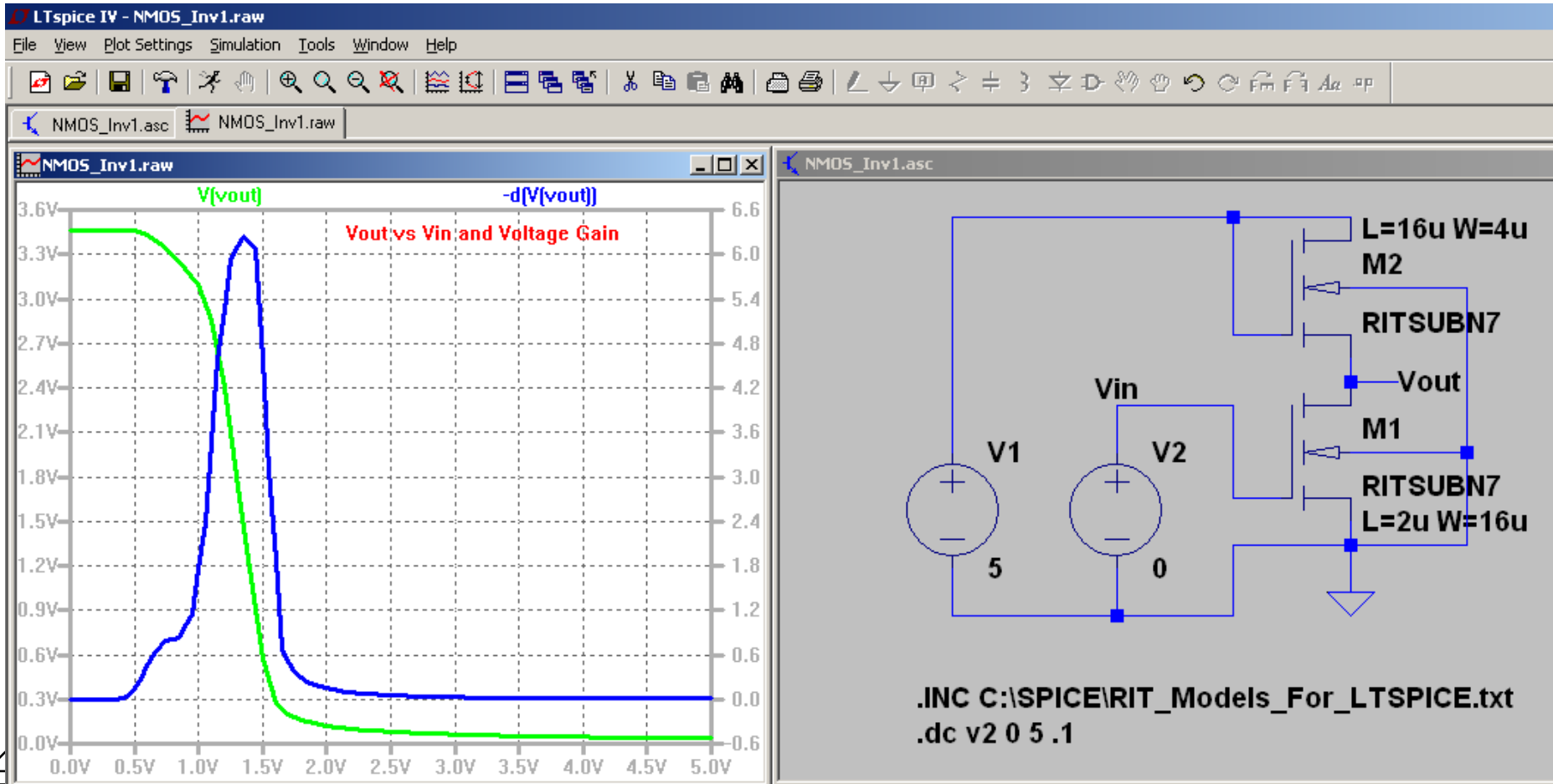

Rochester Institute of Technology
Microelectronic Engineering

PMOS INVERTER WITH PMOS LOAD

INVERTER USING RIT PMOSFET, Dr. Lynn Fuller, 2-11-2007

*LINE ABOVE IS TITLE

*

*START WIN SPICE AND ENTER LOCATION AND NAME OF INPUT FILE

*THIS FILE IS PMOS_INVERTER.TXT

*EXAMPLE: winspice> source c:/spice/PMOS_INVERTER.txt

*

*THE TRANSISTOR MODELS ARE IN THE FILE NAMED BELOW

.INCLUDE E:\SPICE\WINSPICE\RIT_MICROE_MODELS.TXT

*

*CIRCUIT DESCRIPTION

*

*VOLTAGE SOURCES

V1 1 0 DC -10

V2 2 0 DC 0

*

*TRANSISTORS

M1 7 2 0 0 RITPMOS49 L=20U W=60U

M2 1 1 7 0 RITPMOS49 L=60U W=20U

*

*REQUESTED ANALYSIS





.OP

.DC V2 0 -10 -0.1




.PLOT DC V(7)

*


.END

   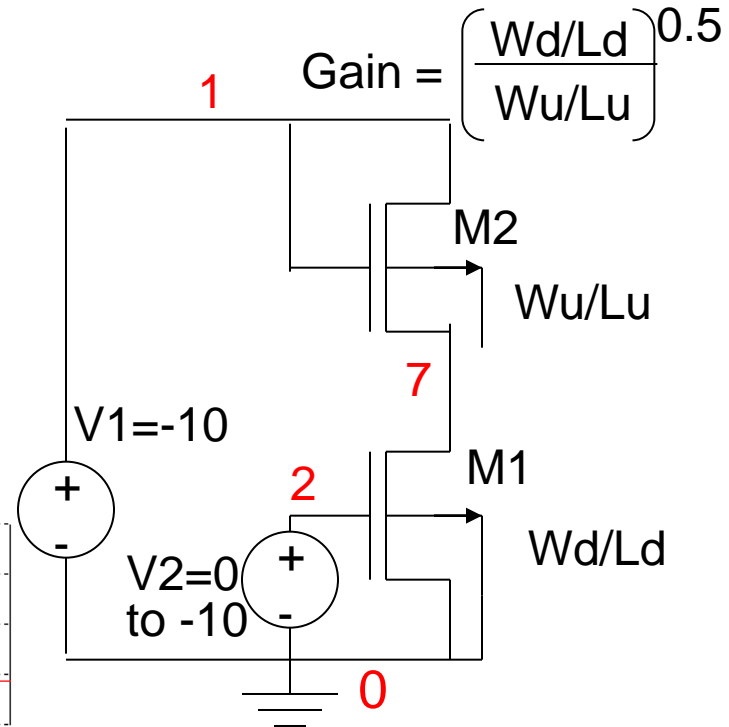



CMOS INVERTER VOUT VS VIN (VTC)

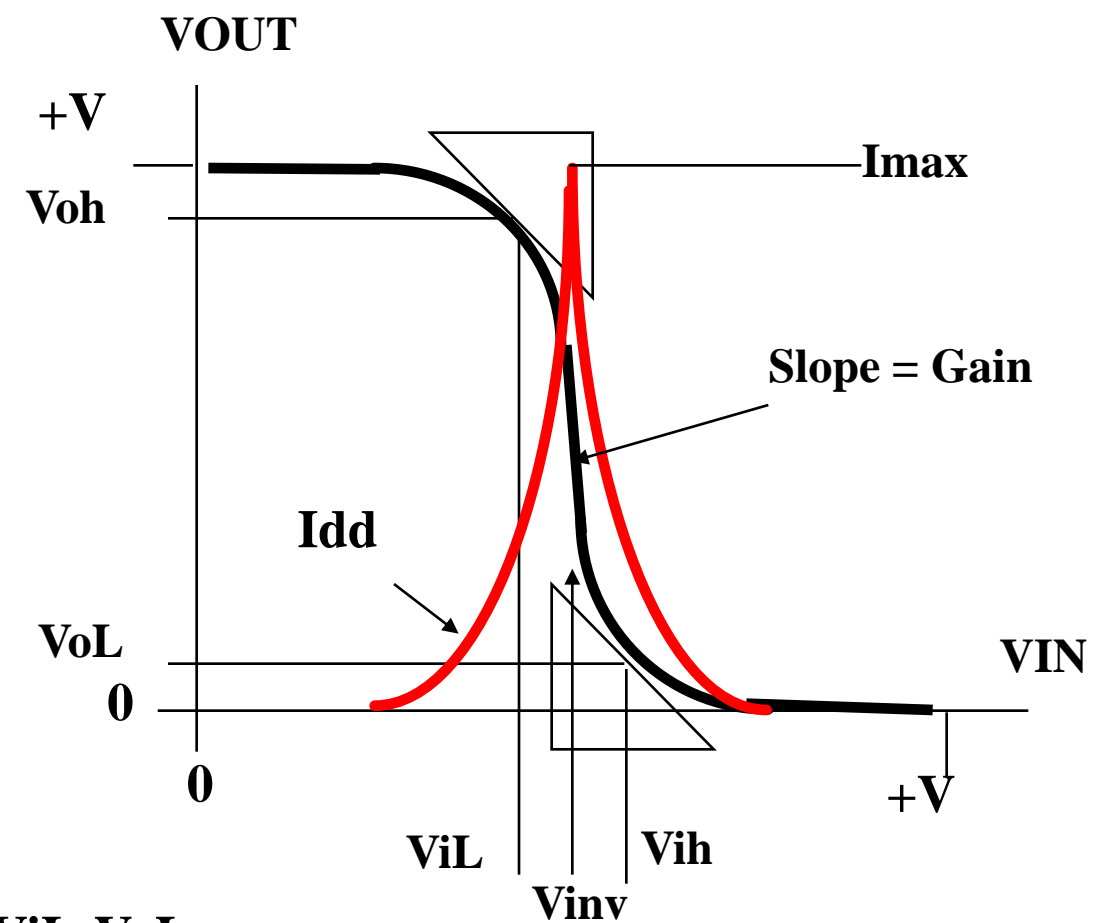  


 
$\Delta 0$ noise margin = $V_{iL} - V_{oL}$
 $\Delta 1$ noise margin = $V_{oH} - V_{iH}$




MEASURED CMOS INVERTER VOUT & I VS VIN

 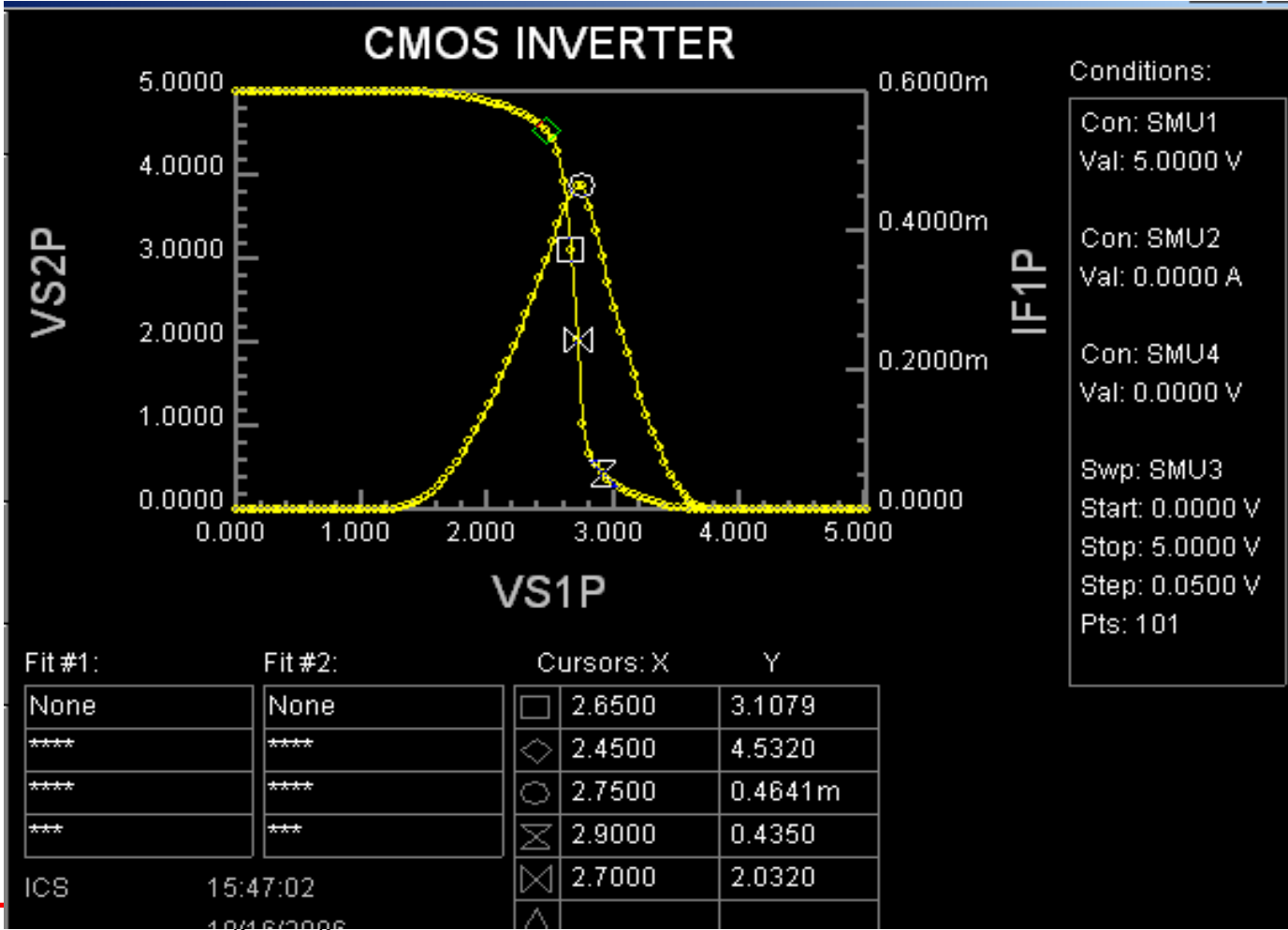

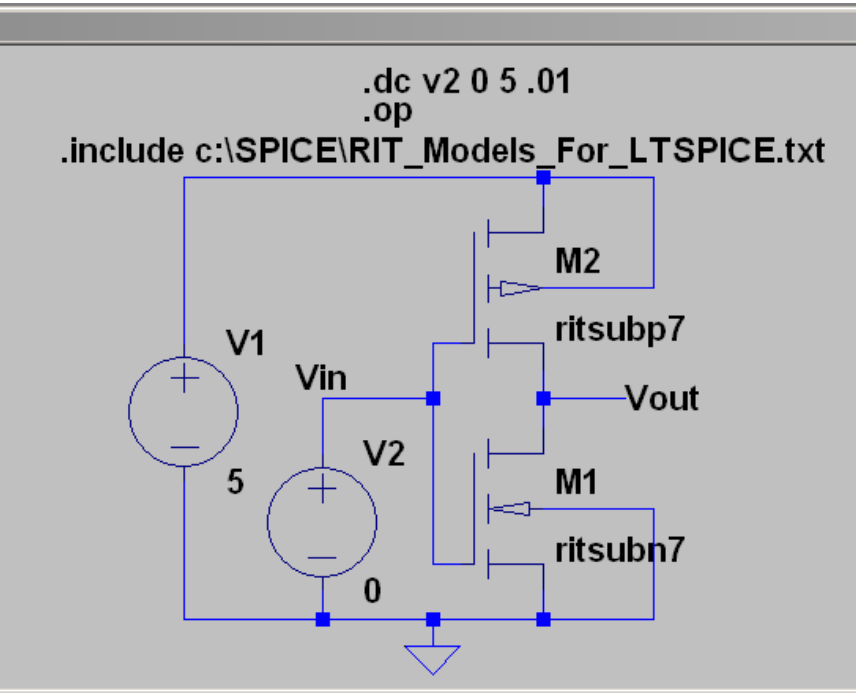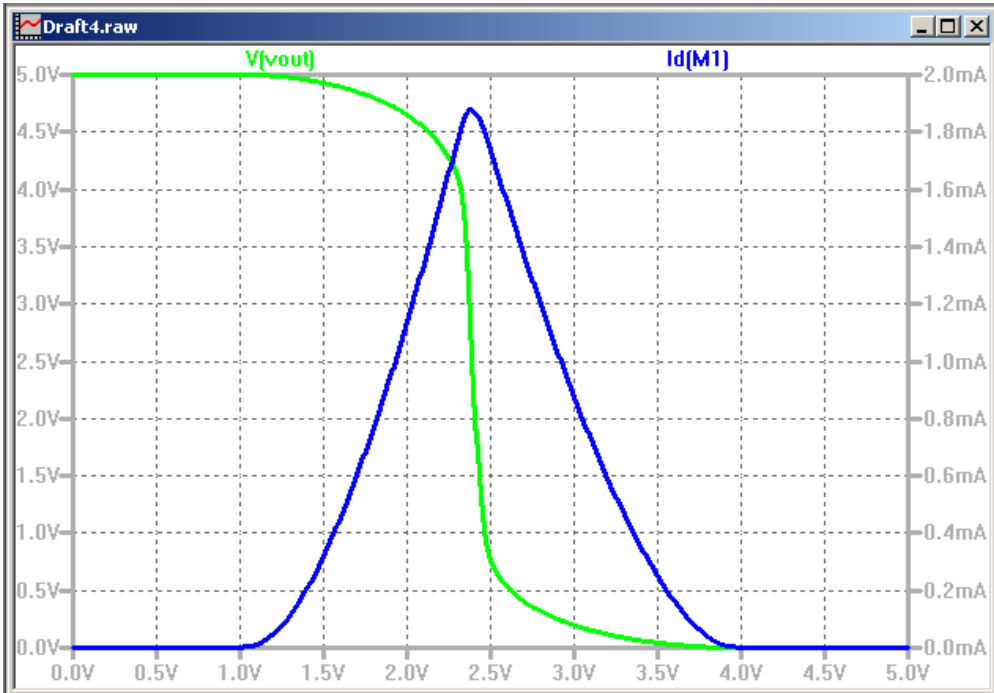DC SIMULATION OF INVERTER VOUT & I VS VIN



 What happens to the voltage transfer curve (VTC) and noise margins when one of the threshold voltages is changed by 0.3 volts? What happens when width of transistors is changed.



SIMPLE AND ADVANCED SPICE MODEL

* From Electronics II EEEE482 FOR ~100nm Technology

```
.model EECMOSN  NMOS (LEVEL=8  
+VERSION=3.1 CAPMOD=2 MOBMOD=1  
+TOX=5E-9 XJ=1.84E-7 NCH=1E17 NSUB=5E16 XT=5E-8  
+VTH0=0.4 U0= 200 WINT=1E-8 LINT=1E-8  
+NGATE=5E20 RSH=1000 JS=3.23E-8 JSW=3.23E-8 CJ=6.8E-4 MJ=0.5 PB=0.95  
+CJSW=1.26E-10 MJSW=0.5 PBSW=0.95 PCLM=5  
+CGSO=3.4E-10 CGDO=3.4E-10 CGBO=5.75E-10)  
*
```

* From Electronics II EEEE482 FOR ~100nm Technology


```
.model EECMOSP  PMOS (LEVEL=8  
+TOX=5E-9 XJ=0.05E-6 NCH=1E17 NSUB=5E16 XT=5E-8  
+VTH0=-0.4 U0= 100 WINT=1E-8 LINT=1E-8  
+NGATE=5E20 RSH=1000 JS=3.51E-8 JSW=3.51E-8 CJ=5.28E-4 MJ=0.5 PB=0.94  
+CJSW=1.19E-10 MJSW=0.5 PBSW=0.94 PCLM=5  
+CGSO=4.5E-10 CGDO=4.5E-10 CGBO=5.75E-10)  
*
```

* From Electronics II EEEE482 SIMPLE MODEL


```
.model EENMOS  NMOS (VTO=0.4 KP=432E-6 GAMMA=0.2 PHI=.88)  
*
```

* From Electronics II EEEE482 SIMPLE MODEL

 
```
.model EEPMOS  PMOS (VTO=-0.4 KP=122E-6 GAMMA=0.2 PHI=.88)
```




CMOS INVERTER WITH LEVEL 1 SPICE MODEL

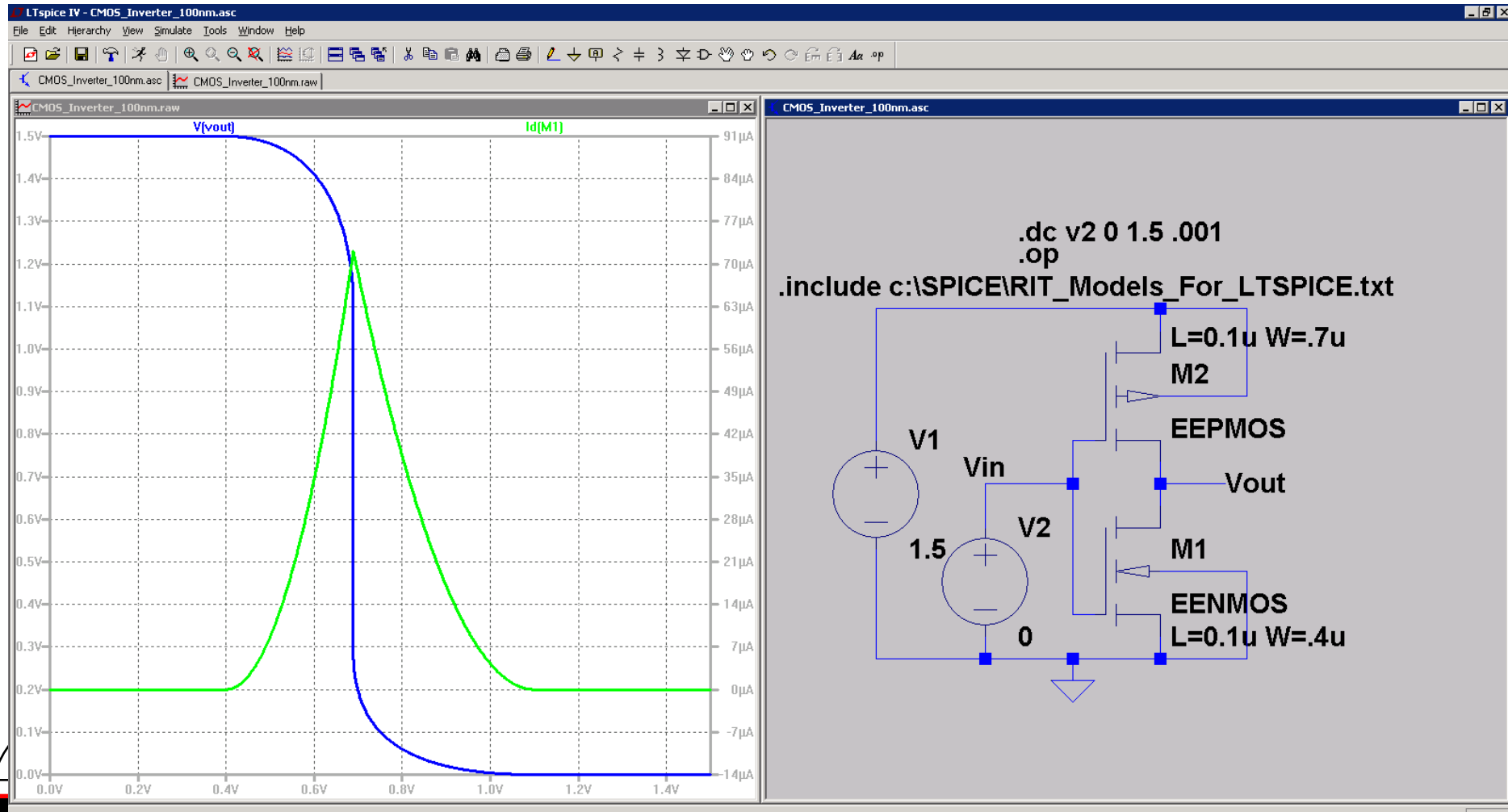

CMOS INVERTER WITH LEVEL 8 SPICE MODEL

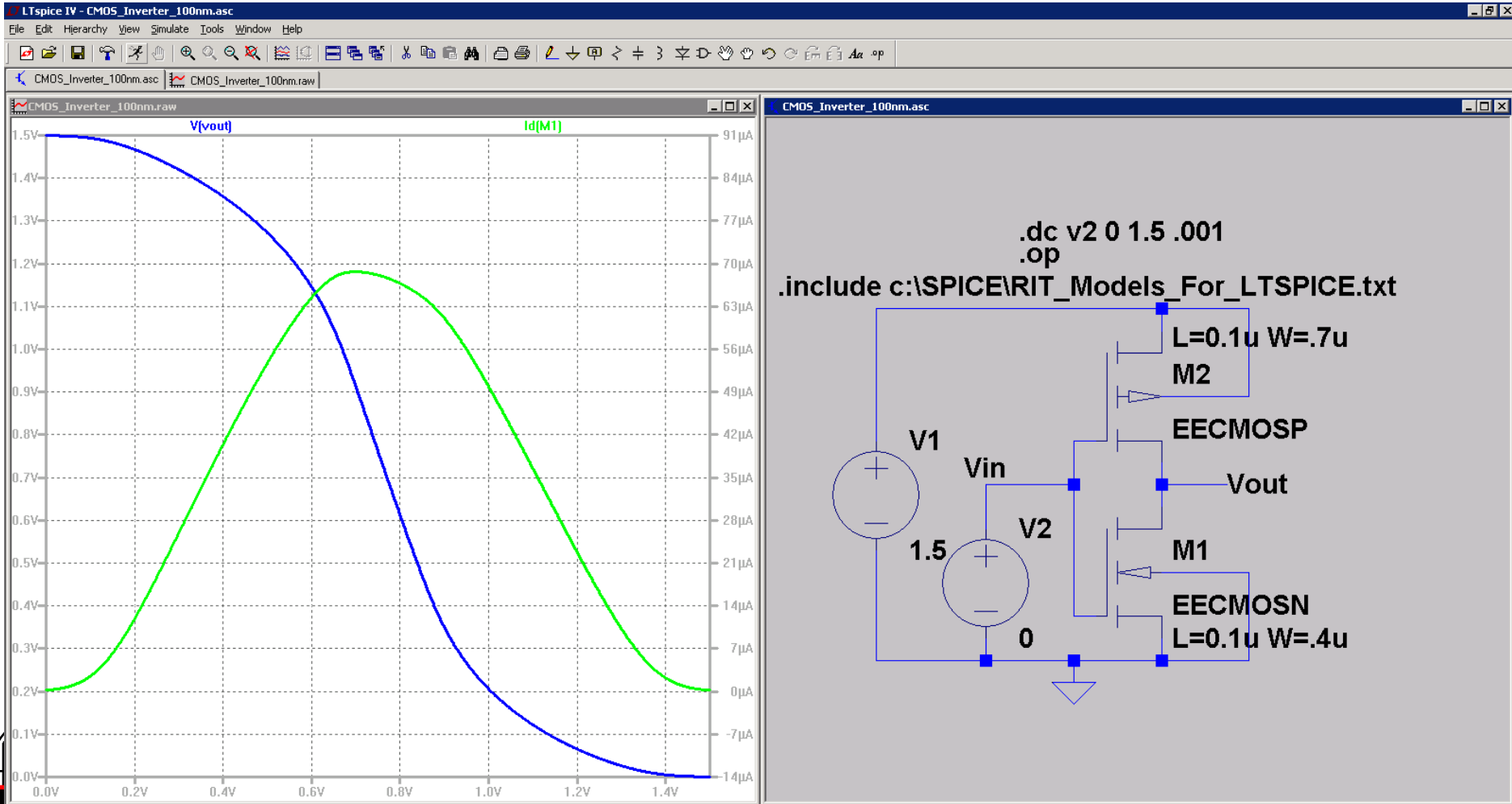

SPICE LEVEL-1 MOSFET MODEL

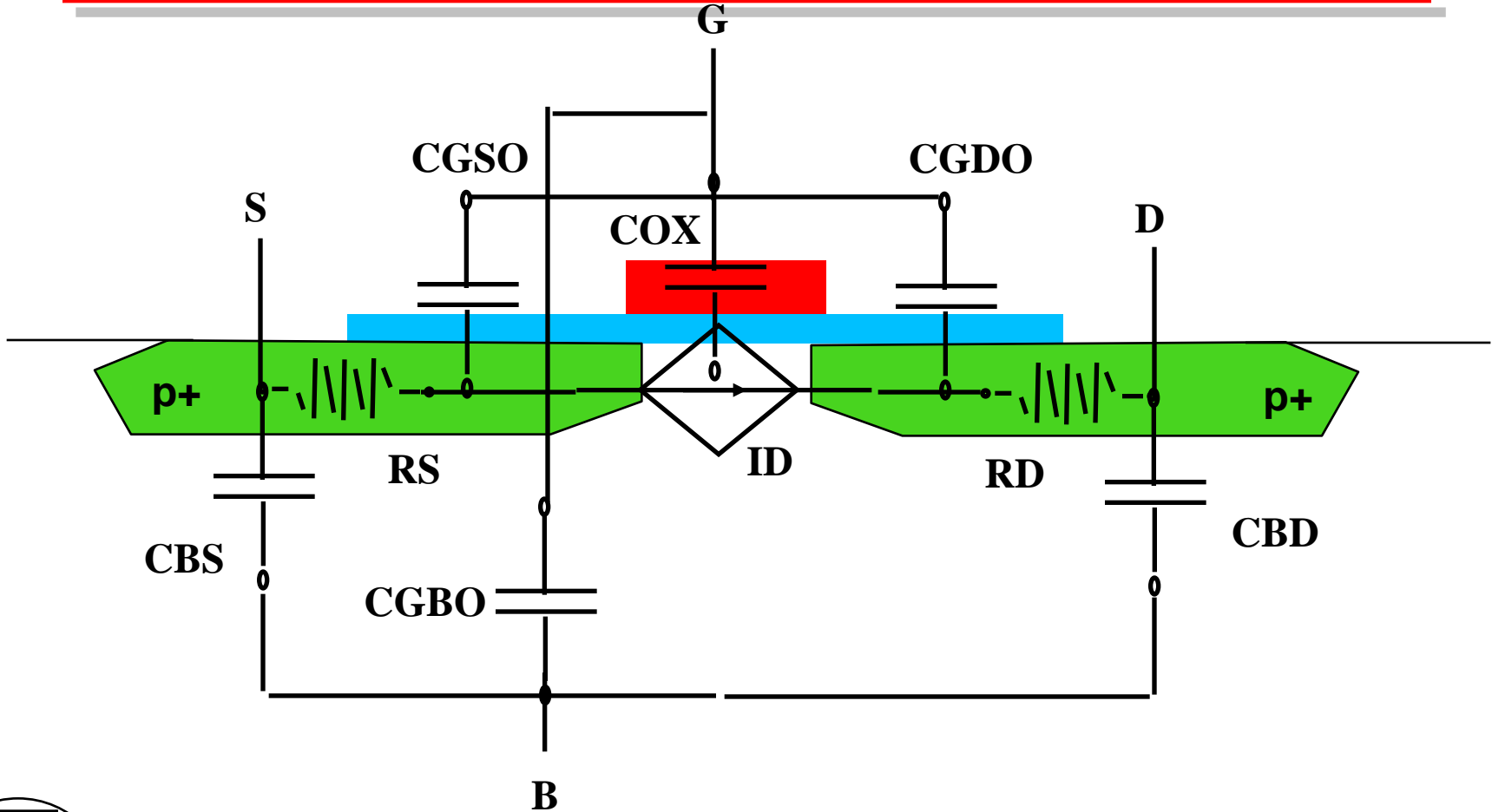

where ID is a dependent current source using simple long channel equations.


AC MODEL FOR MOSFETS

The SPICE model parameters that effect the AC response of a MOSFET are the resistance and capacitance parameters shown here:



RS,RS	Source/Drain Series Resistance, ohms
RSH	Sheet Resistance of Drain/Source, ohms
CGSO,CGDO	Zero Bias Gate-Source/Drain Capacitance, F/m of width
CGBO	Zero Bias Gate-Substrate Capacitance, F/m of length
CJ	DS Bottom Junction Capacitance, F/m ²
CJSW	DS Side Wall Junction Capacitance, F/m of perimeter
MJ	Junction Grading Coefficient, 0.5
MJSW	Side Wall Grading Coefficient, 0.5

These are combined with the transistors properties to obtain the internal resistance and capacitance values for each transistor.


L, W	Length and Width
AS,AD	Area of the Source/Drain
PS,PD	Perimeter of the Source/Drain
NRS,NRD	Number of squares Contact to Channel

 

INVERTER LAYOUT

  

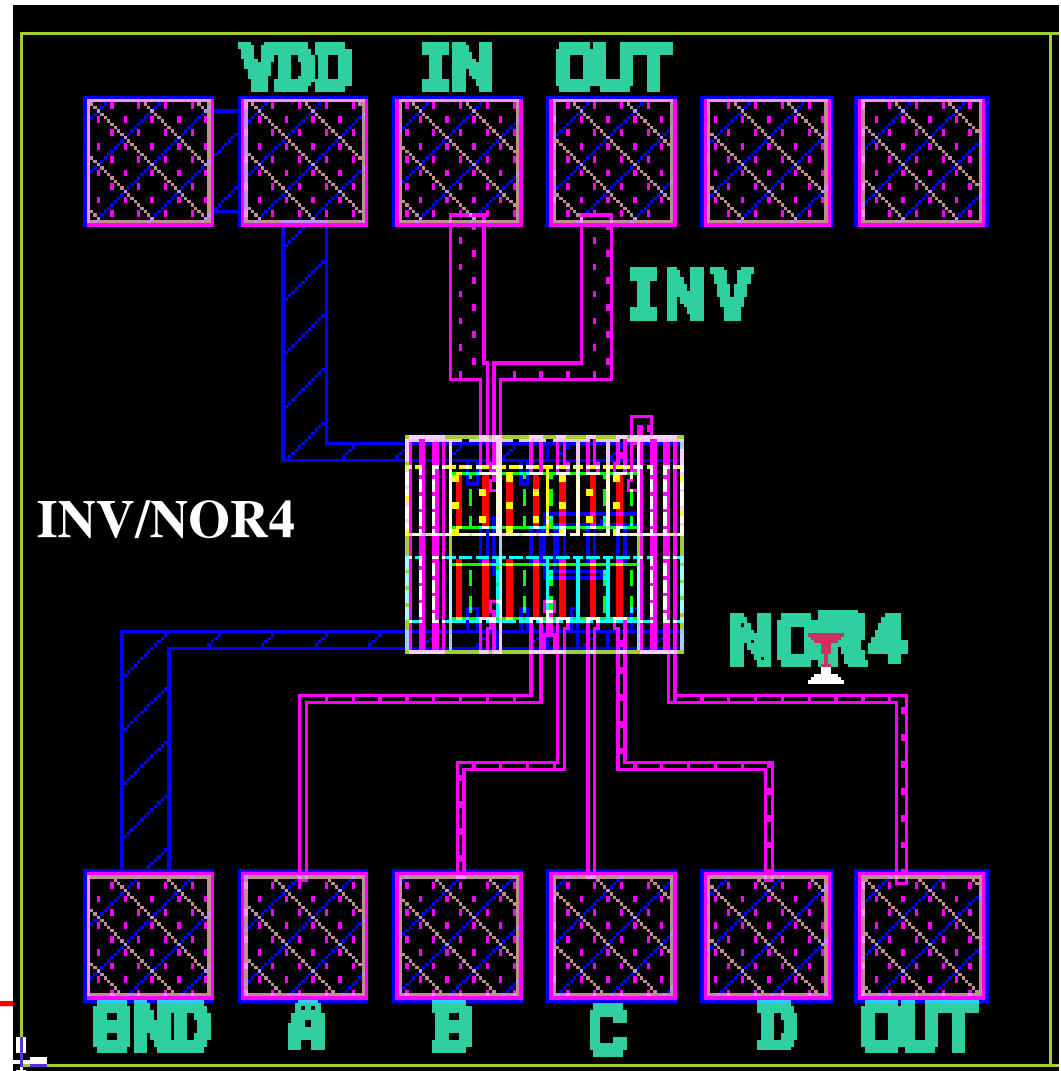$W = 40 \mu\text{m}$
 $L_{\text{drawn}} = 2.5 \mu\text{m}$
 $L_{\text{poly}} = 1.5 \mu\text{m}$
 $L_{\text{eff}} = 1.0 \mu\text{m}$
 $P_d = 680\text{p}$
 $A_d = 114\text{u}$




FIND DIMENSIONS OF THE TRANSISTORS




Inverter

	NMOS	PMOS
L	1.5u	1.5u
W	40u	40u
AD	17u x 40u = 680p	17u x 40u = 680p
AS	17u x 40u = 680p	17u x 40u = 680p
PD	2x(17u+40u) = 114u	2x(17u+40u) = 114u
PS	2x(17u+40u) = 114u	2x(17u+40u) = 114u


 
Right mouse click on each transistor and add these values to the properties.



 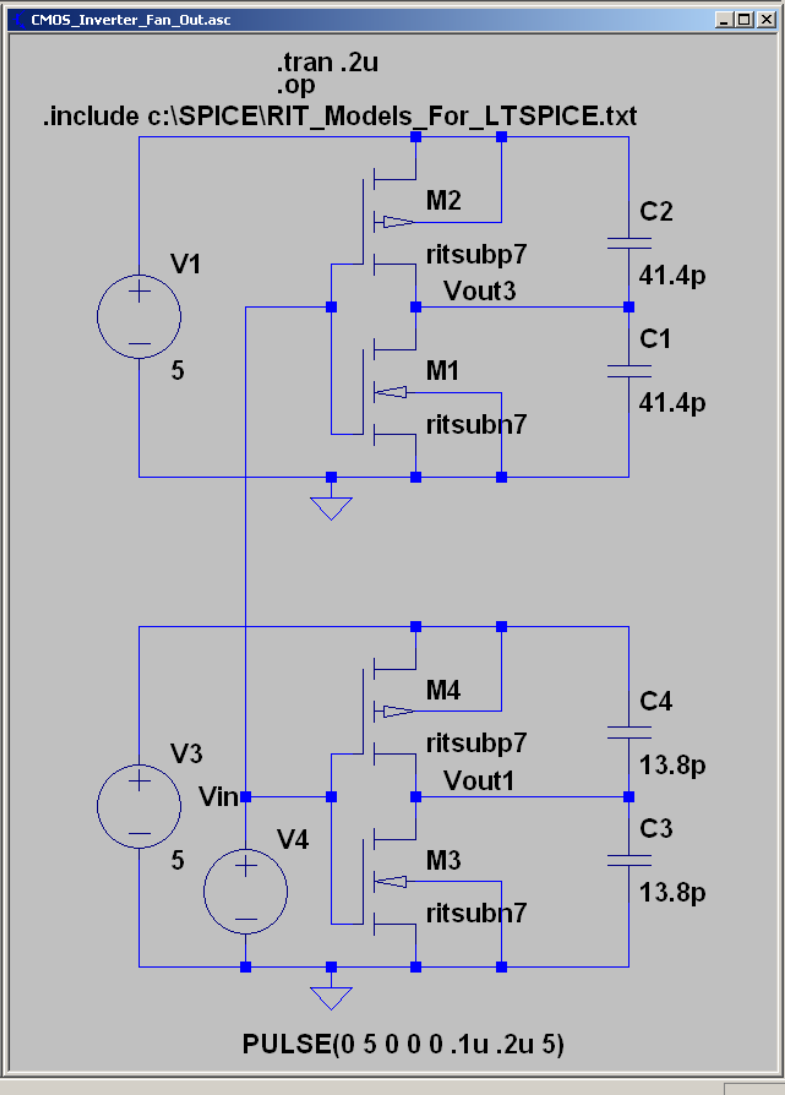 RISE TIME AND FALL TIME LTSPICE SIMULATION



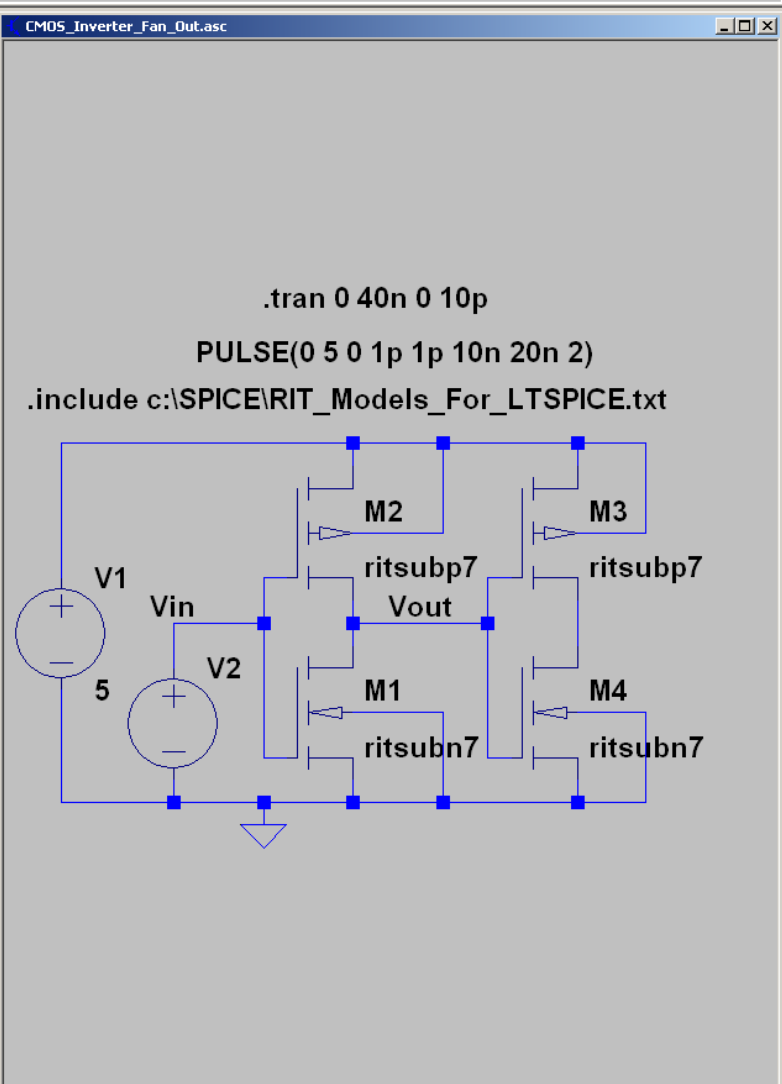 SIMULATION OF GATE DELAY IN SINGLE INVERTER



RING OSCILLATOR, *td*, THEORY



**Seven stage ring oscillator
with two output buffers**

$td = T / 2 N$


$td =$ gate delay

$N =$ number of stages



$T =$ period of oscillation

  

T = period of oscillation

 


MEASURED RING OSCILLATOR OUTPUT

  

$$t_d = 104.8\text{ns} / 2(73) = 0.718\text{ ns}$$

SPICE LEVEL-1 MOSFET MODEL

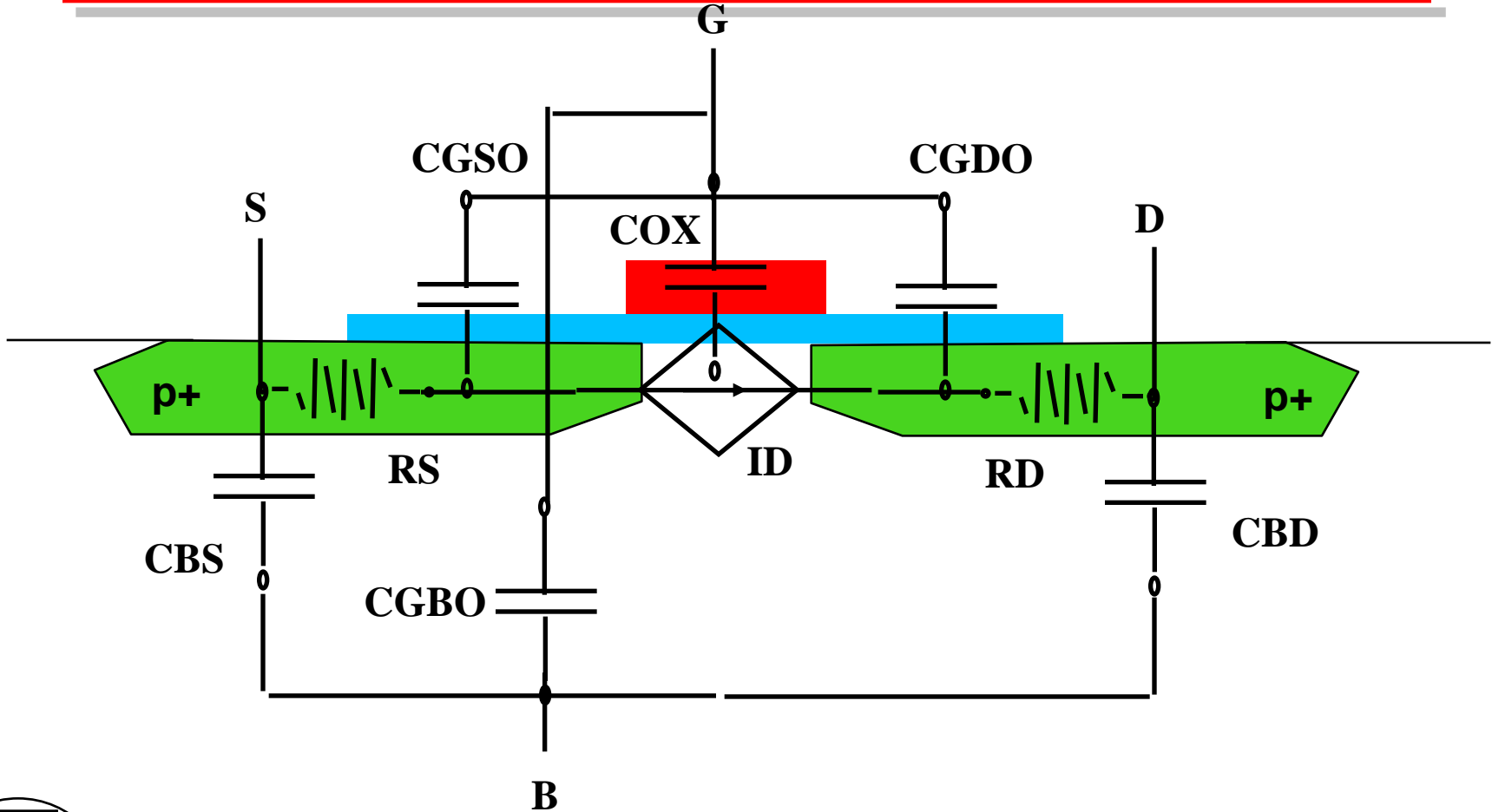

where ID is a dependent current source using simple long channel equations.


AC MODEL FOR MOSFETS

The SPICE model parameters that effect the AC response of a MOSFET are the resistance and capacitance parameters shown here:

RS,RS	Source/Drain Series Resistance, ohms
RSH	Sheet Resistance of Drain/Source, ohms
CGSO,CGDO	Zero Bias Gate-Source/Drain Capacitance, F/m of width
CGBO	Zero Bias Gate-Substrate Capacitance, F/m of length
CJ	DS Bottom Junction Capacitance, F/m ²
CJSW	DS Side Wall Junction Capacitance, F/m of perimeter
MJ	Junction Grading Coefficient, 0.5
MJSW	Side Wall Grading Coefficient, 0.5

These are combined with the transistors properties to obtain the internal resistance and capacitance values for each transistor.


L, W	Length and Width
AS,AD	Area of the Source/Drain
PS,PD	Perimeter of the Source/Drain
NRS,NRD	Number of squares Contact to Channel

 

RING OSCILLATOR LAYOUTS

17 Stage Un-buffered Output

L/W=2/30 Buffered Output

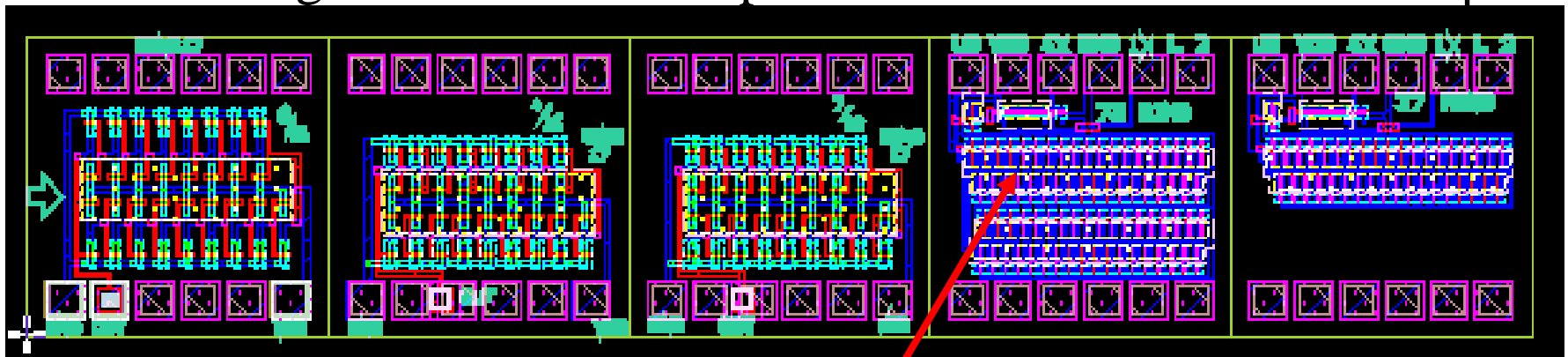


L/W 8/16

4/16


2/16

73 Stage

37 Stage

 


 Rochester Institute of Technology
Microelectronics Center




MOSFETS IN THE INVERTER OF 73 RING OSCILLATOR

nmosfet

 

pmosfet

 


73 Stage Ring Oscillator

FIND DIMENSIONS OF THE TRANSISTORS

	NMOS	PMOS
L	2u	2u
W	12u	30u
AD	12u x 12u = 144p	12u x 30u = 360p
AS	12u x 12u = 144p	12u x 30u = 360p
PD	2x(12u + 12u) = 48u	2x(12u + 30u) = 84u
PS	2x(12u + 12u) = 48u	2x(12u + 30u) = 84u
NRS	1	0.3
NRD	1	0.3

73 Stage

 Right mouse click on each transistor and add these values to the properties.



LEVEL = 7

*2-15-2009



```
.MODEL RITSUBN7 NMOS (LEVEL=7  
+VERSION=3.1 CAPMOD=2 MOBMOD=1  
+TOX=1.5E-8 XJ=1.84E-7 NCH=1.45E17 NSUB=5.33E16 XT=8.66E-8 NSS=3E11  
+VTH0=1.0 U0= 600 WINT=2.0E-7 LINT=1E-7  
+NGATE=5E20 RSH=50 JS=3.23E-8 JSW=3.23E-8 CJ=6.8E-4 MJ=0.5 PB=0.95  
+CJSW=1.26E-10 MJSW=0.5 PBSW=0.95 PCLM=5  
+CGSO=3.4E-10 CGDO=3.4E-10 CGBO=5.75E-10)
```

*

*2-17-2009

```
.MODEL RITSUBP7 PMOS (LEVEL=7  
+VERSION=3.1 CAPMOD=2 MOBMOD=1  
+TOX=1.5E-8 XJ=2.26E-7 NCH=7.12E16 NSUB=3.16E16 XT=8.66E-8 NSS=3E11 PCLM=5  
+VTH0=-1.0 U0= 376.72 WINT=2.0E-7 LINT=2.26E-7 NGATE=5E20  
+RSH=50 JS=3.51E-8 JSW=3.51E-8 CJ=5.28E-4 MJ=0.5 PB=0.94  
+CJSW=1.19E-10 MJSW=0.5 PBSW=0.94  
+CGSO=4.5E-10 CGDO=4.5E-10 CGBO=5.75E-10)
```


SIMULATED OUTPUT AT 10 VOLTS

 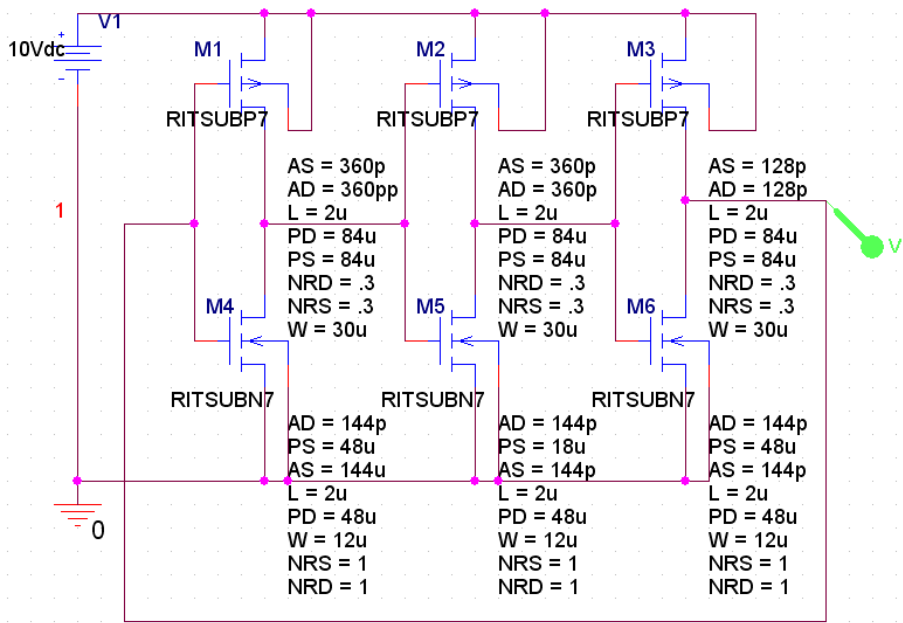



Three Stage Ring Oscillator with Transistor Parameters for 73 Stage Ring Oscillator and Supply of 10 volts

$$t_d = T / 2N = 3.5\text{nsec} / 2 / 3$$

$$t_d = 0.583 \text{ nsec}$$

 

SIMULATED OUTPUT AT 5 VOLTS

 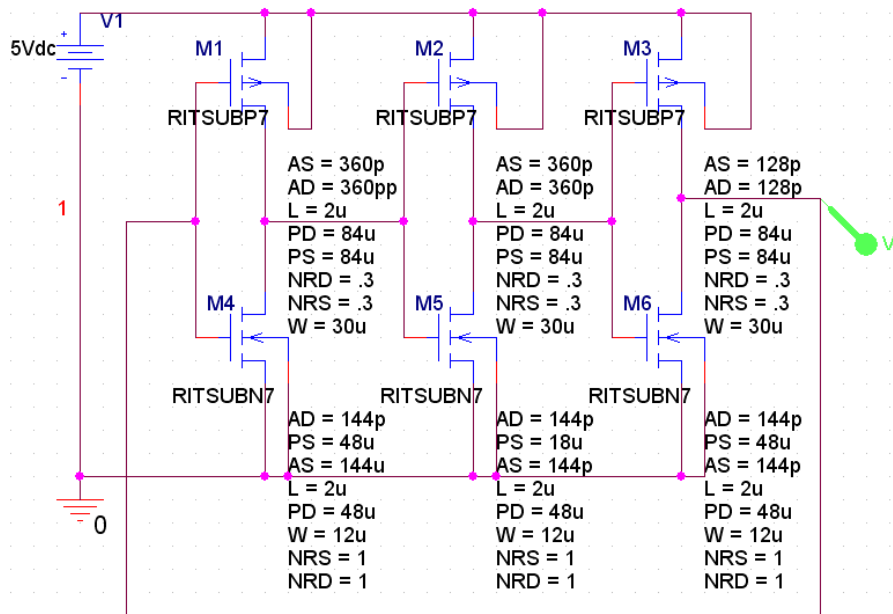


Three Stage Ring Oscillator with Transistor Parameters for 73 Stage Ring Oscillator and Supply of 5 volts


Measured $t_d = 0.718 \text{ nsec @ } 5 \text{ V}$

$$t_d = T / 2N = 5.5\text{nsec} / 2 / 3$$

$$t_d = 0.92 \text{ nsec}$$

 

RING OSCILLATOR USING LTSPICE

 

Monolithic MOSFET - M4

Model Name: ritsubp7

Length(L): 2u

Width(W): 30u

Drain Area(AD): 360p


Source Area(AS): 360p

Drain Perimeter(PD): 84u

Source Perimeter(PS): 84u

No. Parallel Devices(M):

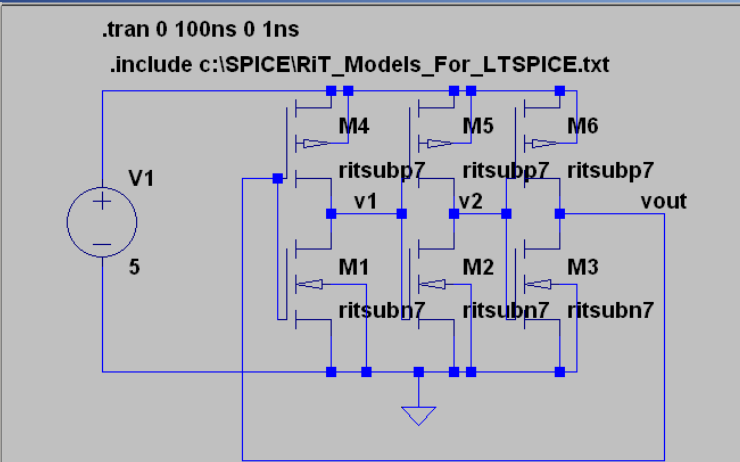ritsubp7 l=2u w=30u ad=360p as=360p pd=84u ps=84u nrs=0.3 nrd



Monolithic MOSFET - M1

Model Name: ritsubn7

Length(L): 2u

Width(W): 12u

Drain Area(AD): 144p

Source Area(AS): 144p

Drain Perimeter(PD): 48u

Source Perimeter(PS): 48u

No. Parallel Devices(M):

ritsubn7 l=2u w=12u ad=144p as=144p pd=48u ps=48u nrs=1 nrd

CONCLUSION

Since the measured and the simulated gate delays, t_d are close to correct, then the SPICE model must be close to correct. The inverter gate delay depends on the values of the internal capacitors and resistances of the transistor.

Specifically:

RS, RS, RSH

CGSO, CGDO, CGBO

CJ, CJSW

These are combined with the transistors

L, W Length and Width

AS,AD Area of the Source/Drain


PS,PD Perimeter of the Source/Drain

NRS,NRD Number of squares Contact to Channel

VTC FOR THREE INPUT NAND GATE

TRUTH TABLE


Va	Vb	Vc	Vout
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

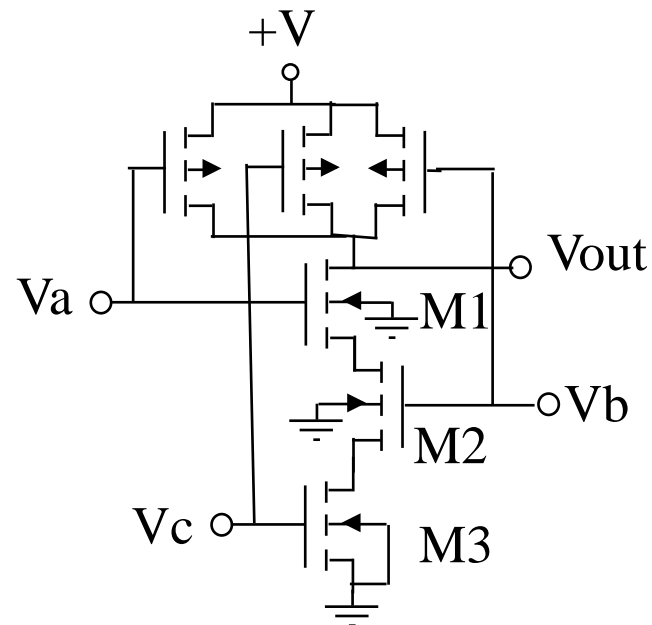


M3 has $V_t = V_{to}$
 M1 has $V_t = V_{to} + \text{Body Effect}$

Thus the Voltage Transfer Curve (VTC) is different depending on which transistor is going from low to high (with other two high)


3-INPUT NAND- BODY EFFECT

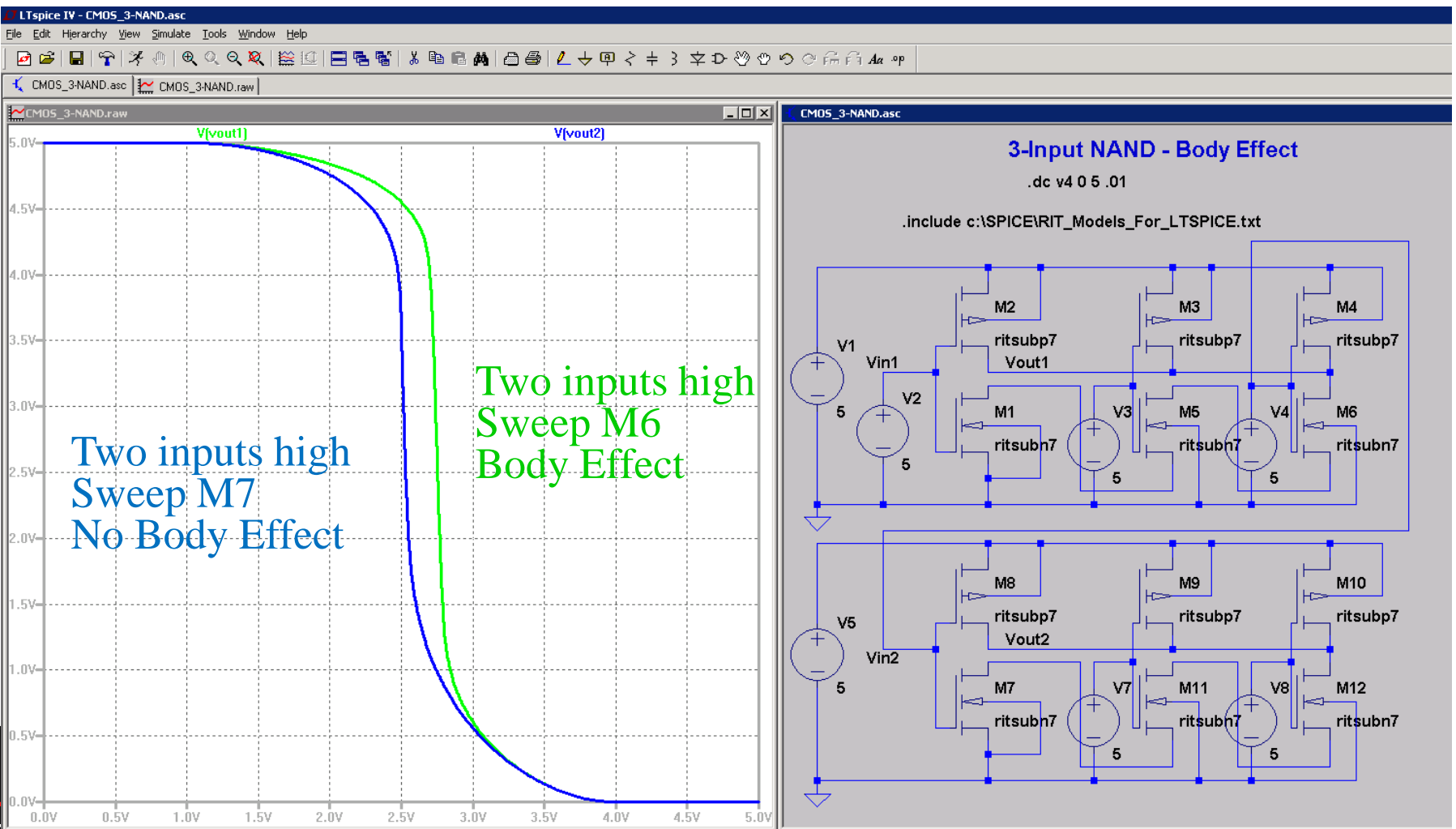


GATE LEVEL SIMULATION OF XOR – ALL/NOR

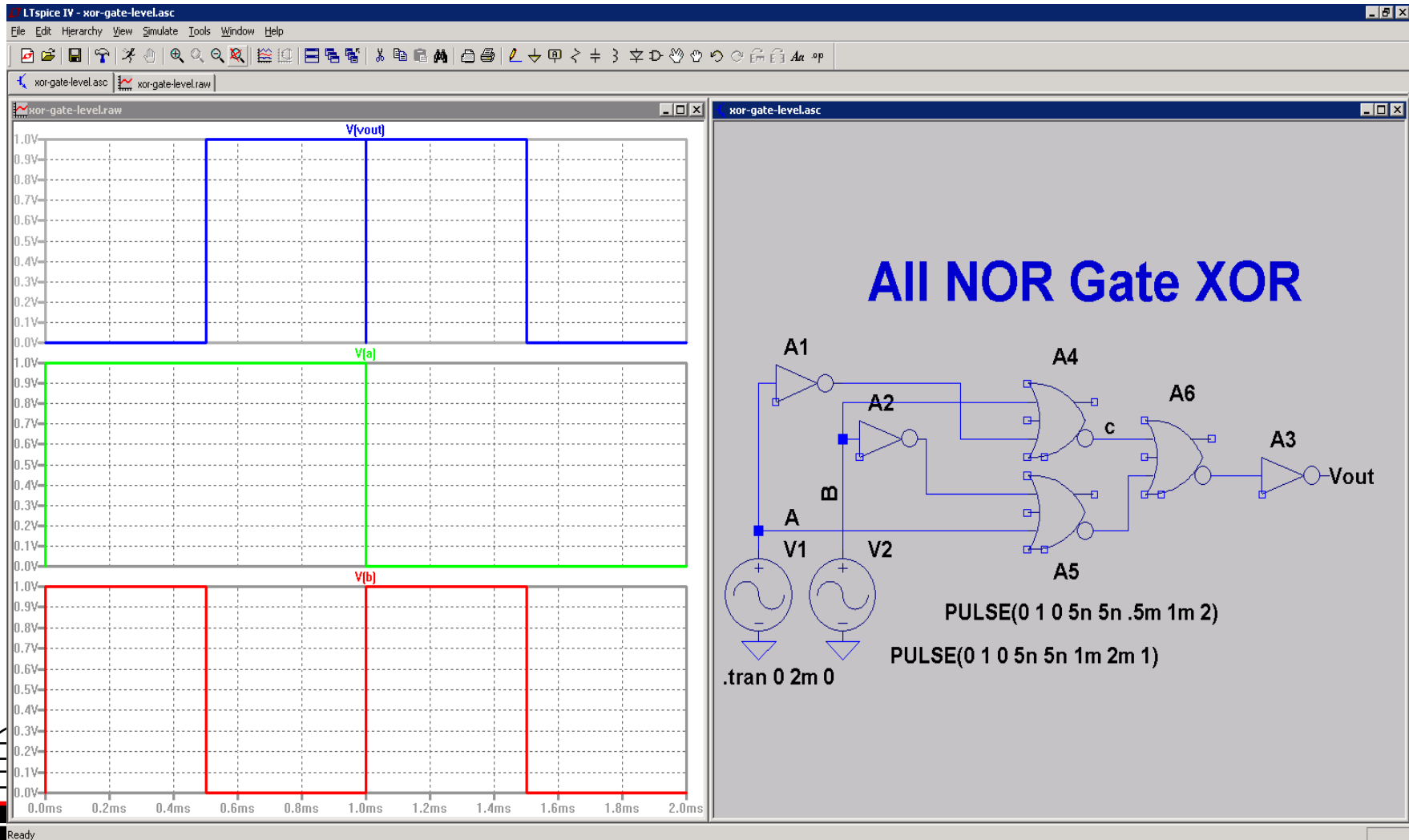

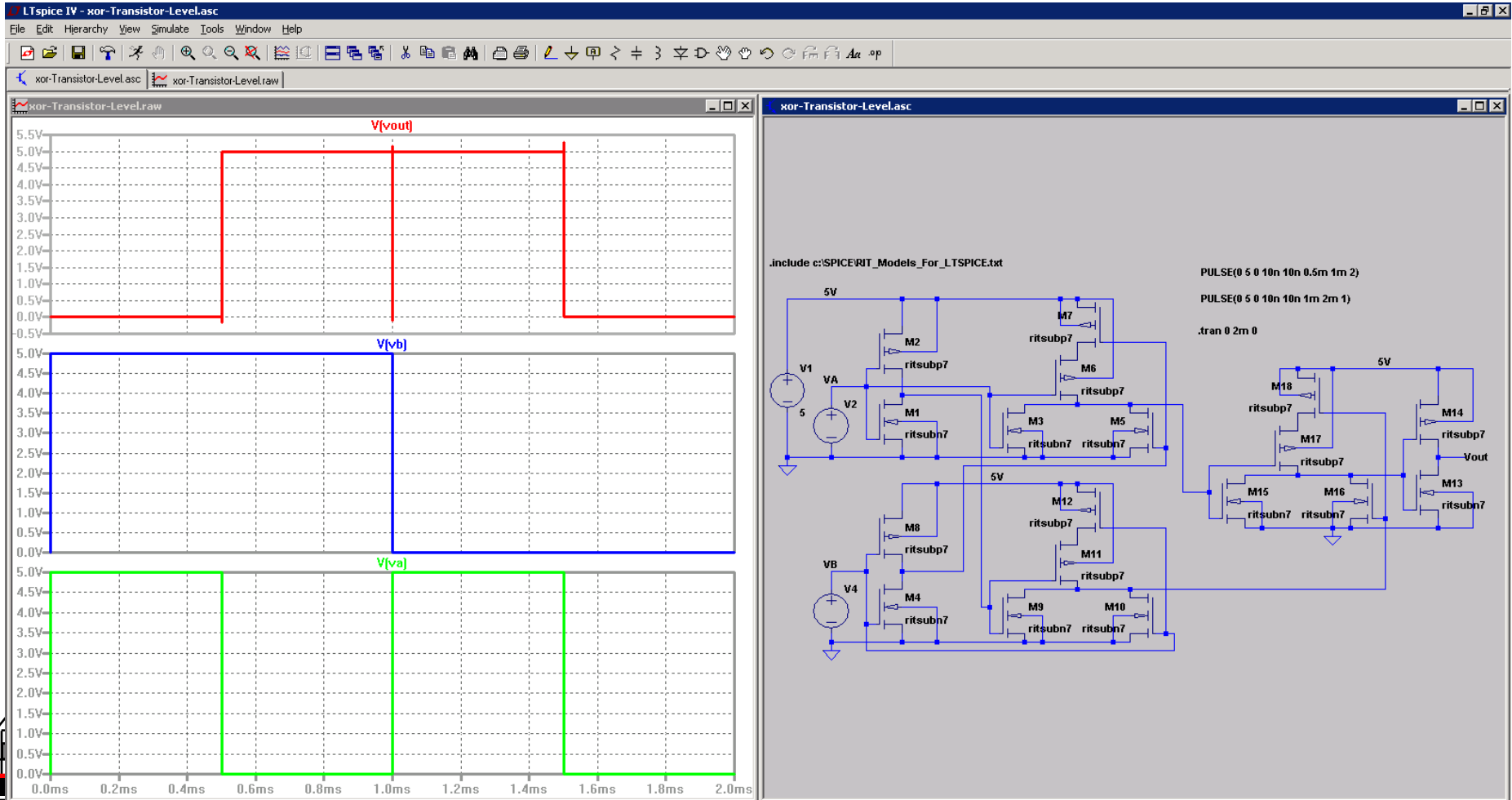TRANSISTOR LEVEL SIMULATION OF XOR – ALL/NOR




4 TO 1 MULTIPLEXER

 


Digital signals A and B control which of the four inputs is directed to the output


A	B	Out
0	0	I0
0	1	I1
1	0	I2
1	1	I3

 


4 TO 1 MUX - GATE LEVEL SIMULATION

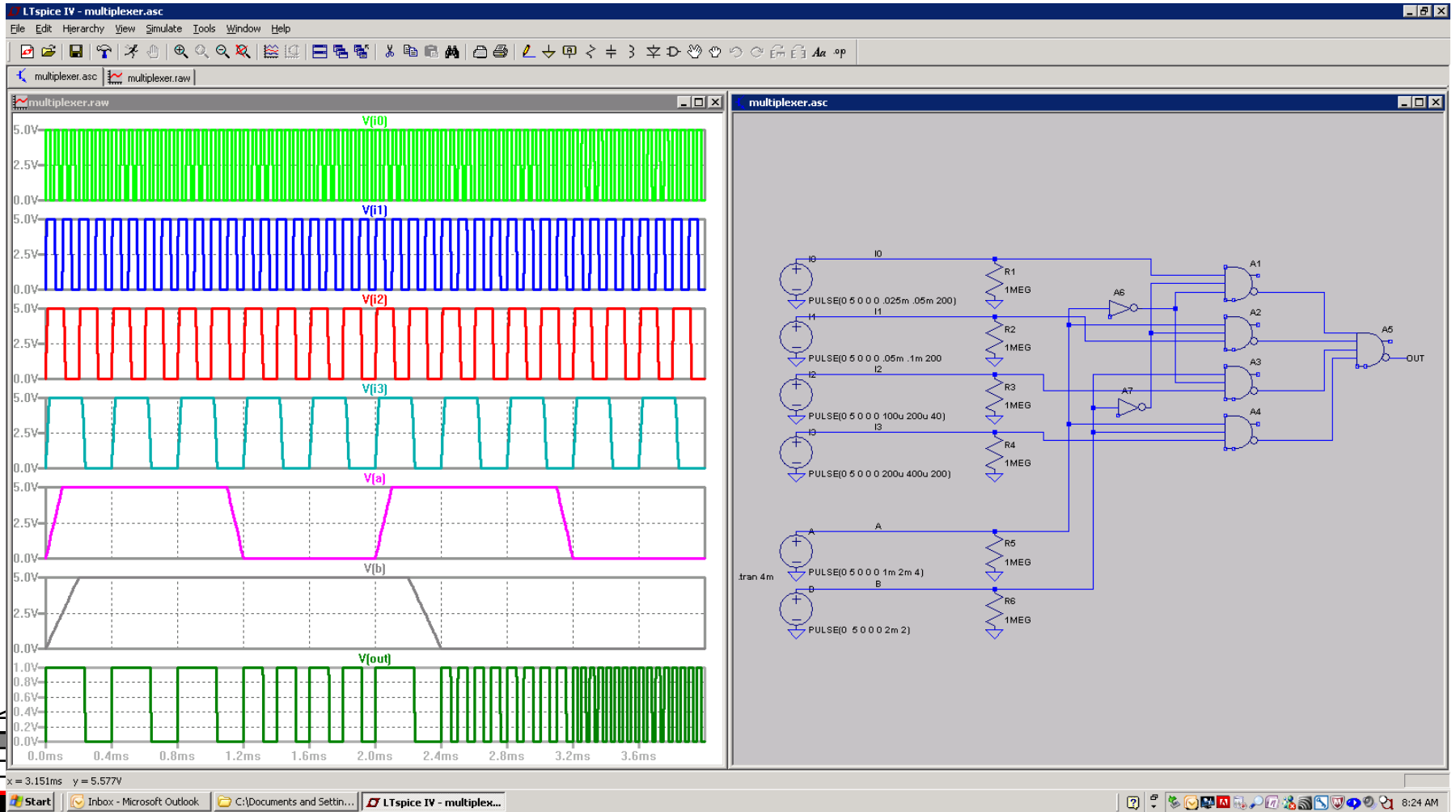

ANALOG SWITCH

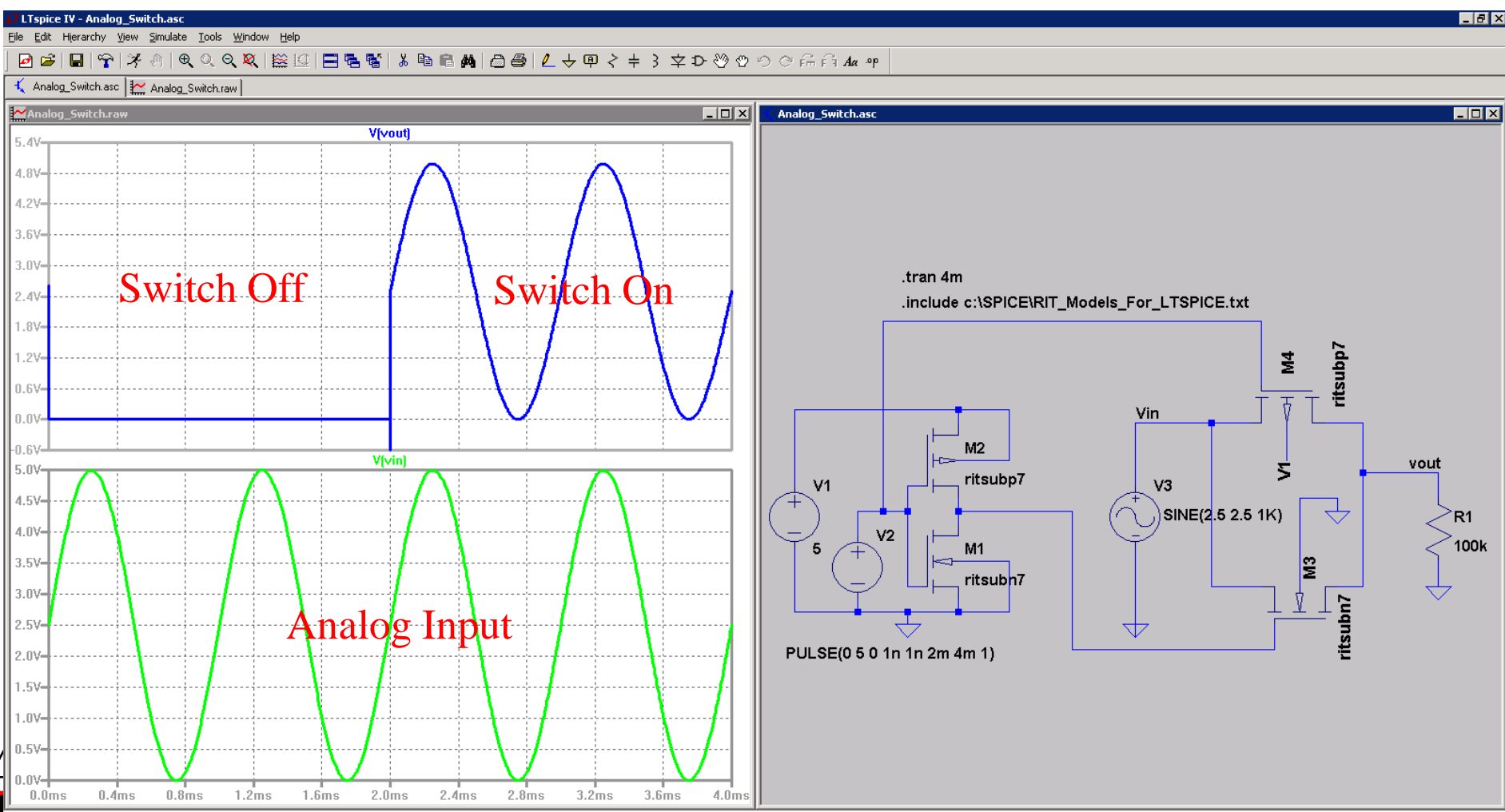

BASIC TWO STAGE OPERATIONAL AMPLIFIER

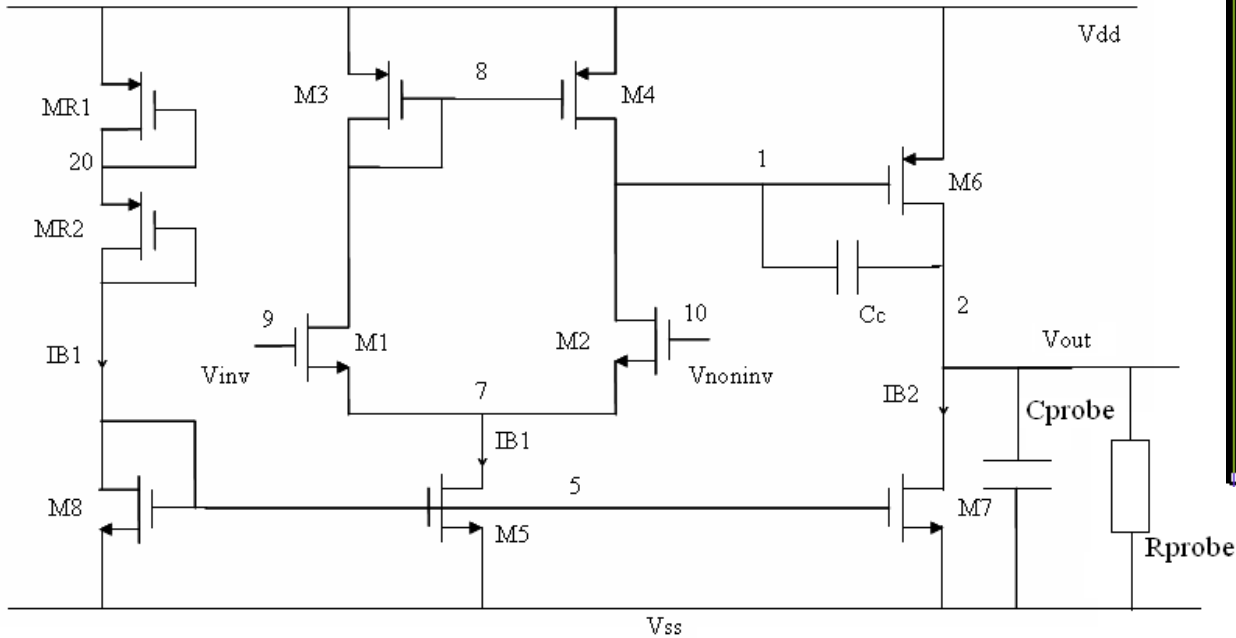

Schematic




Layout

SPICE ANALYSIS OF OP AMP


```
.incl rit_sub_param.txt
m1 8 9 7 6 cmosn w=9u l=5u nrd=1 nrs=1 ad=45p pd=28u as=45p ps=28u
m2 1 10 7 6 cmosn w=9u l=5u nrd=1 nrs=1 ad=45p pd=28u as=45p ps=28u
m3 8 8 4 4 cmosp w=21u l=5u nrd=1 nrs=1 ad=102p pd=50u as=102p ps=50u
m4 1 8 4 4 cmosp w=21u l=5u nrd=1 nrs=1 ad=102p pd=50u as=102p ps=50u
m5 7 5 6 6 cmosn w=40u l=5u nrd=1 nrs=1 ad=205p pd=90u as=205p ps=90u
m6 2 1 4 4 cmosp w=190u l=5u nrd=1 nrs=1 ad=950p pd=400u as=950p ps=400u
m7 2 5 6 6 cmosn w=190u l=5u nrd=1 nrs=1 ad=950p pd=400u as=950p ps=400u
m8 5 5 6 6 cmosn w=40u l=5u nrd=1 nrs=1 ad=205p pd=90u as=205p ps=90u
vdd 4 0 3
vss 6 0 -3
cprobe 2 0 30p
Rprobe 2 0 1meg
cc 1 2 0.6p
mr1 20 20 4 4 cmosp w=6u l=10u nrd=1 nrs=1 ad=200p pd=60u as=200p ps=60u
mr2 5 5 20 4 cmosp w=6u l=10u nrd=1 nrs=1 ad=200p pd=60u as=200p ps=60u
```

```
*****
*****
```

 


```
*** dc open loop
gain *****
vi1 9 0 0
vi2 10 0 0
*.dc vi2 -0.002 0.002 1u
.dc vi2 -1 1 0.1m
**** open loop frequency
characteristics ****
*vi1 9 0 0
*vi2 10 0 dc 0 ac 1u
*.ac dec 100 10 1g
.end
```

BASIC TWO STAGE OP AMP - LOADING

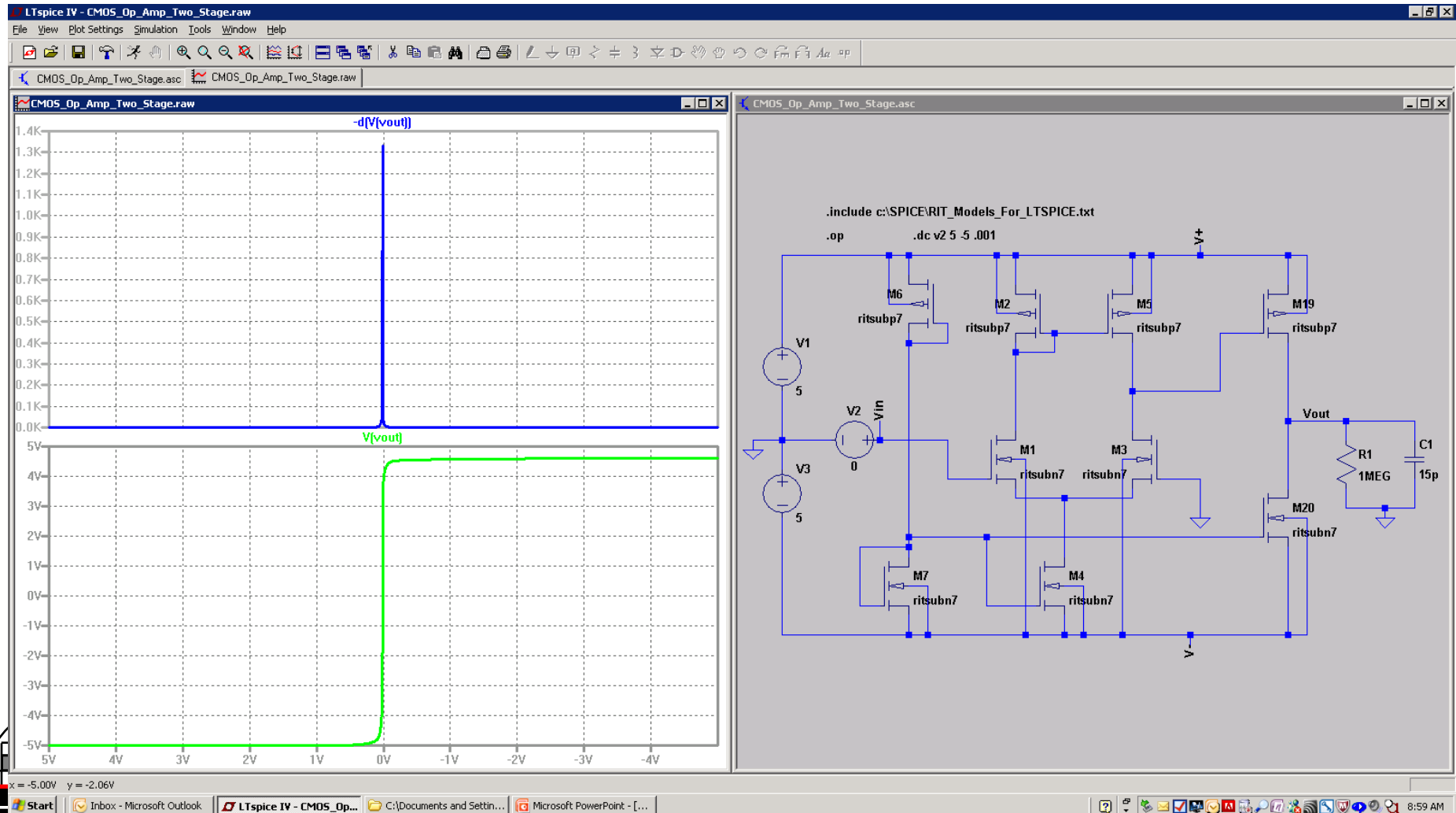

RIT OP AMP WITH OUTPUT STAGE – W/L


99

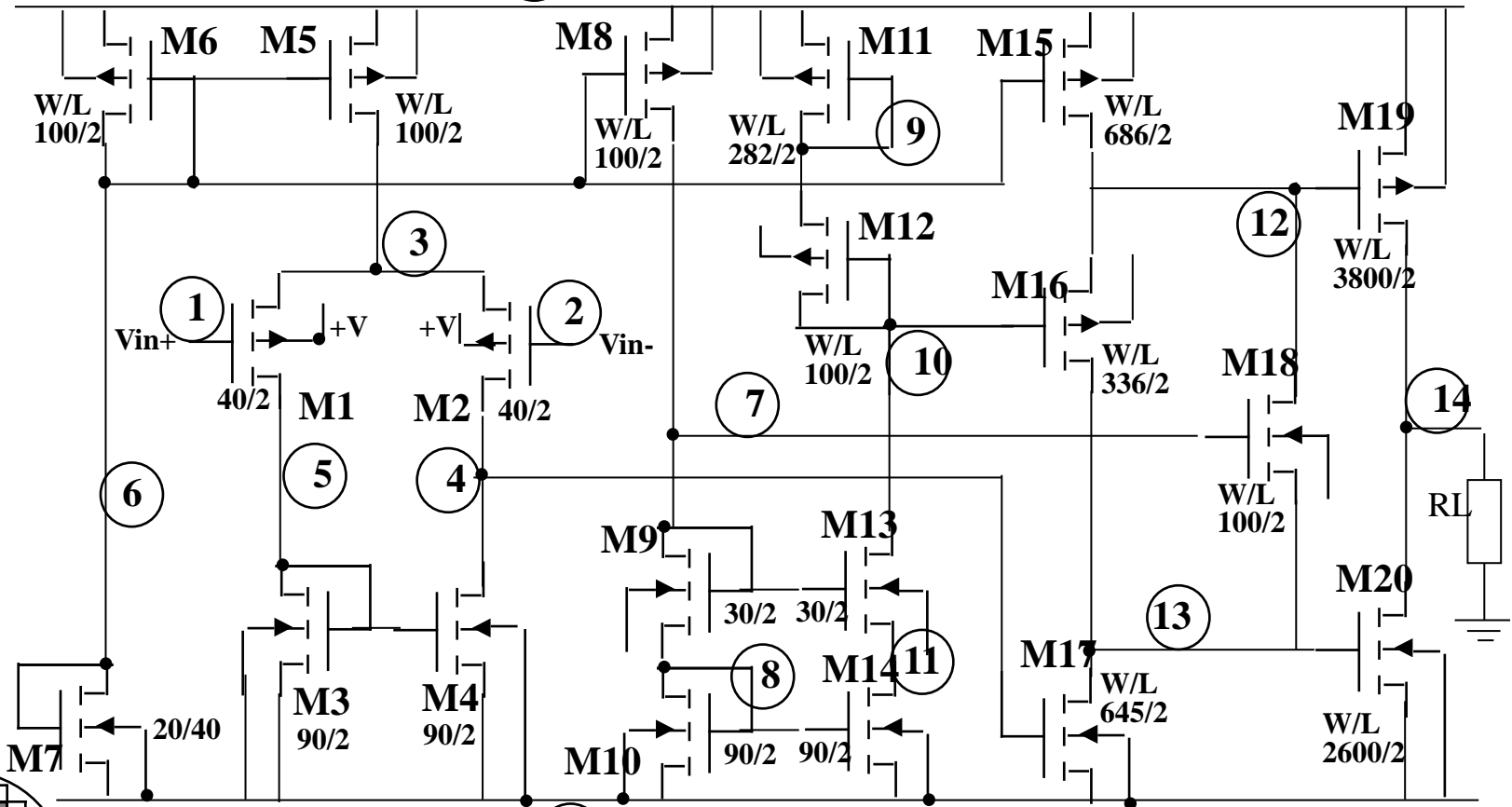


98

Rochester Institute of Technology
Microelectronic Engineering


W/L

 

RIT OP AMP WITH OUTPUT STAGE

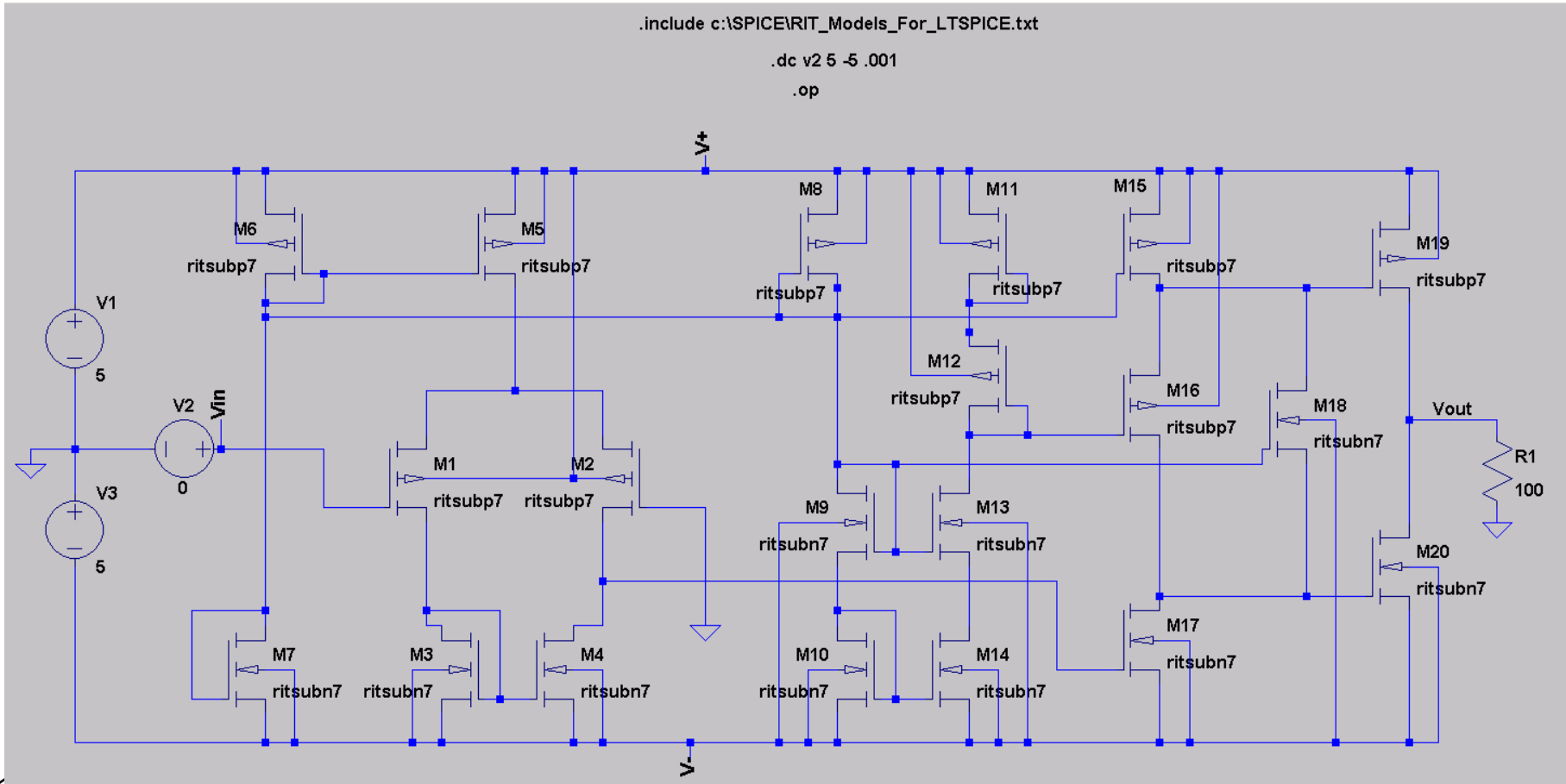


RIT OP AMP WITH OUTPUT STAGE – RL=100

 


OTHER RESULTS

 
Voltage Gain for 1 MEG Load
Voltage Gain vs RL
Output Resistance
Gain versus Frequency (Gain Bandwidth Product)
Lowest Supply Voltage
Single Supply Operation
Rail-to-Rail Operation
Offset Voltage
Effect of variation of V_t , temperature
more




SIMPLE BJT OP AMP

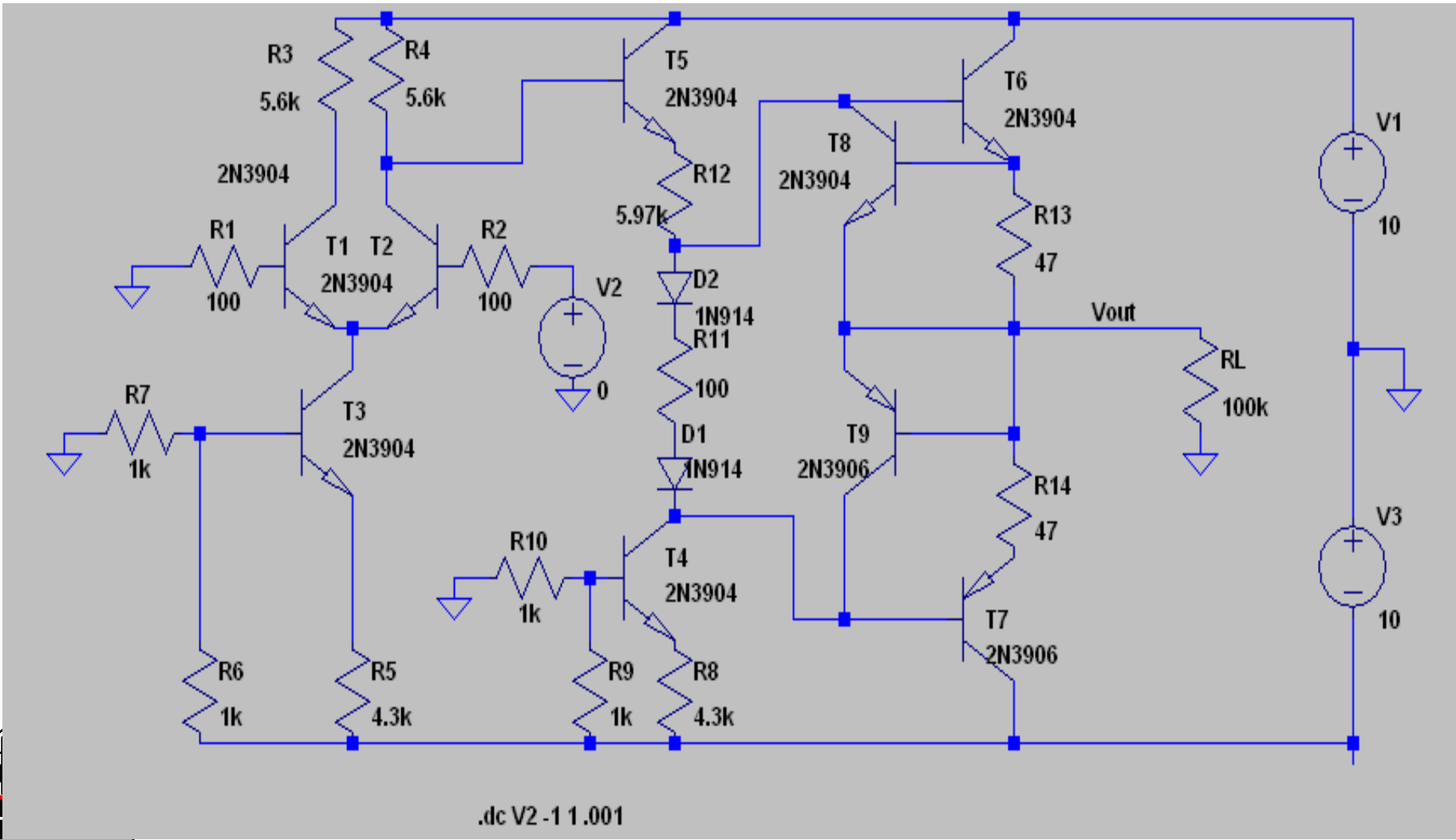

SIMPLE BJT OP AMP

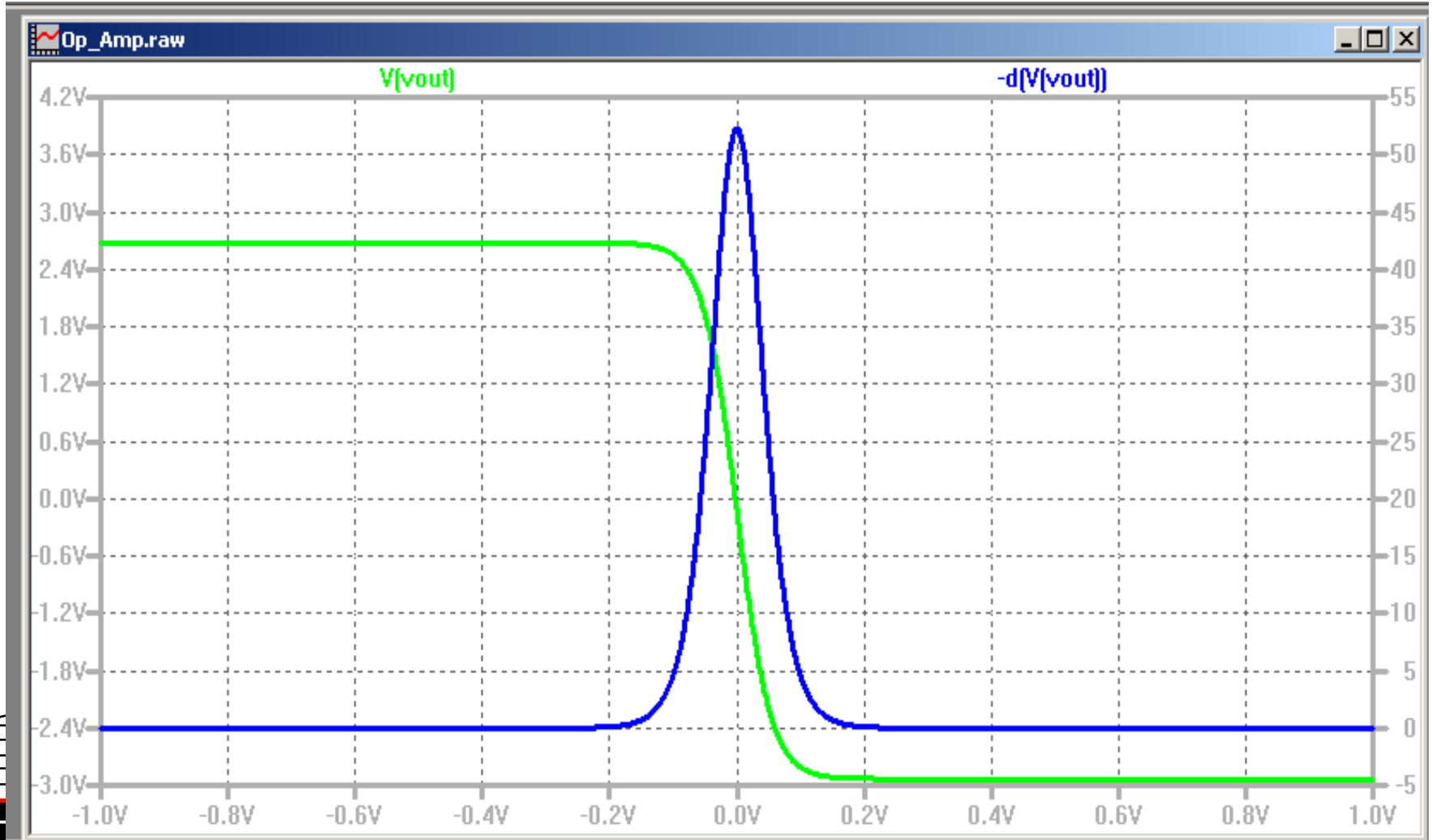



BJT OP AMP USE IN ELECTRONICS LAB

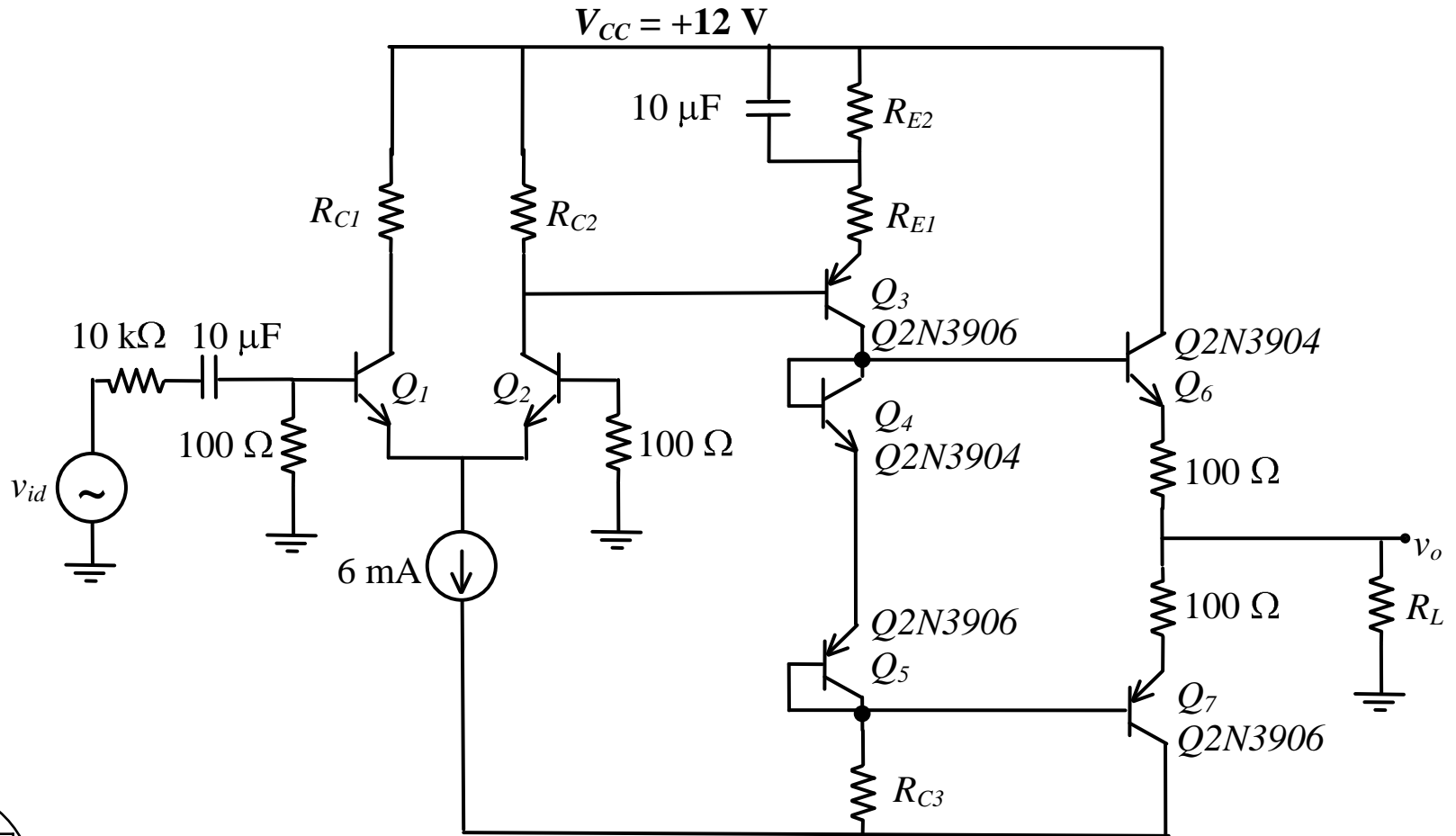


BJT OP AMP SPICE SIMULATION

Electronics II
Lab Assignment


WAVEFORM GENERATOR

 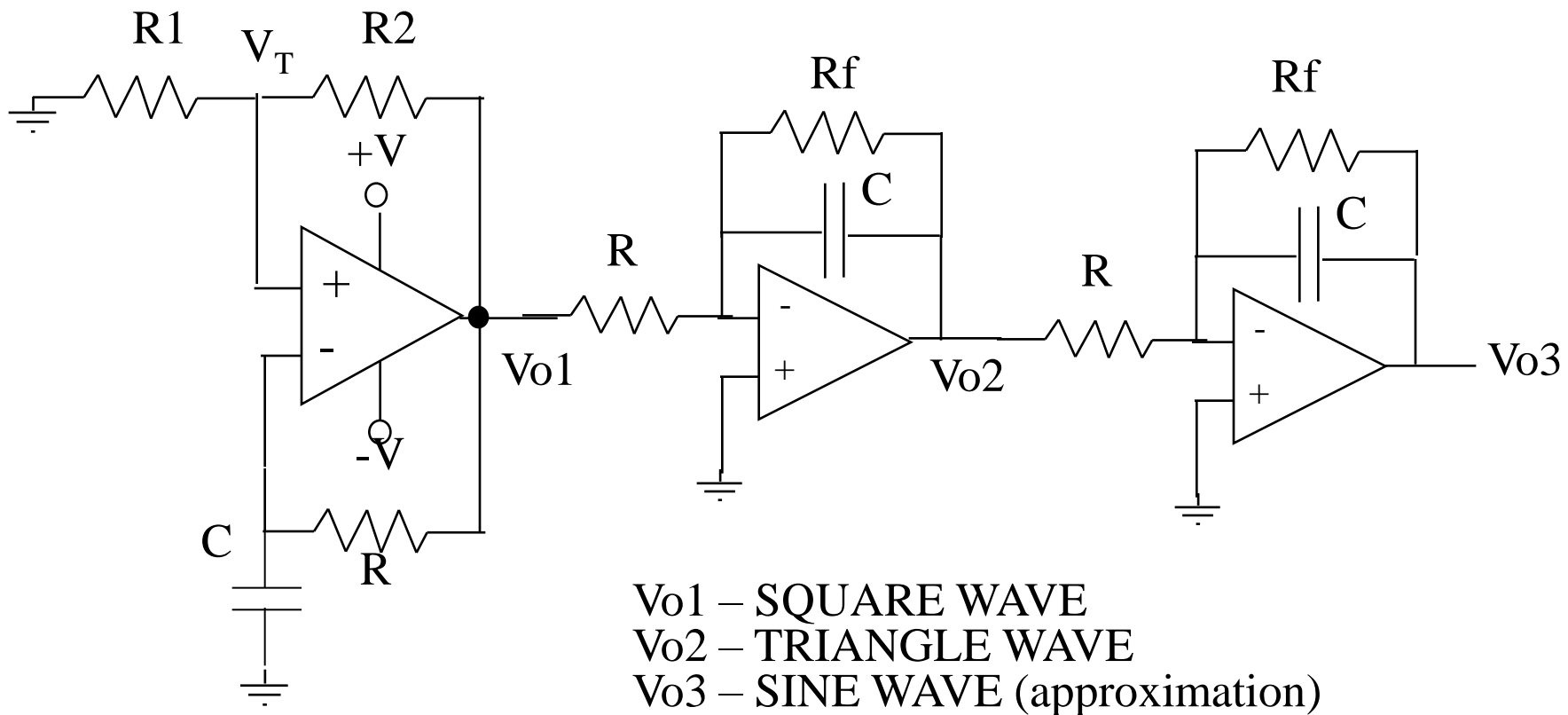

WAVEFORM GENERATOR

 


AM RECEIVER


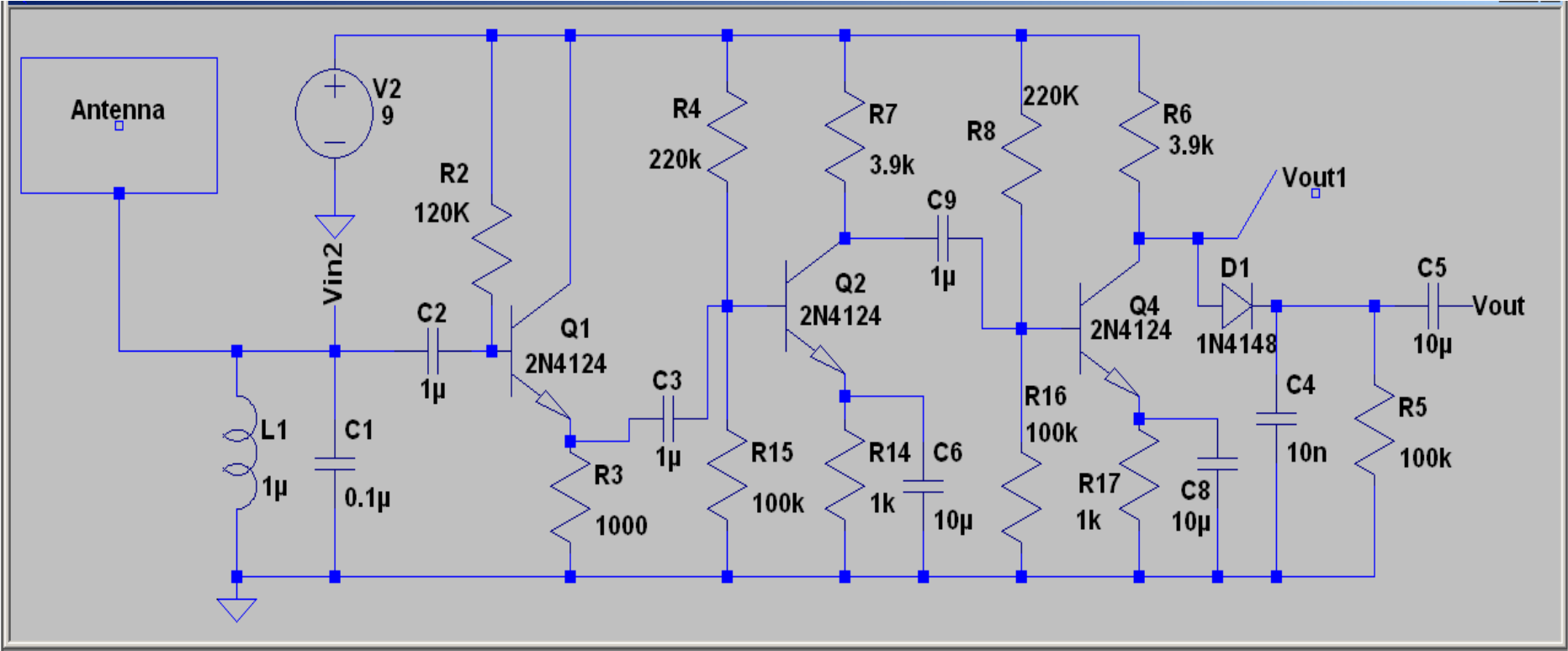


LC Filter


 
Three Stage Amplifier
Input 10's of uV Output 100's of mV



AM RECEIVER SIMULATION

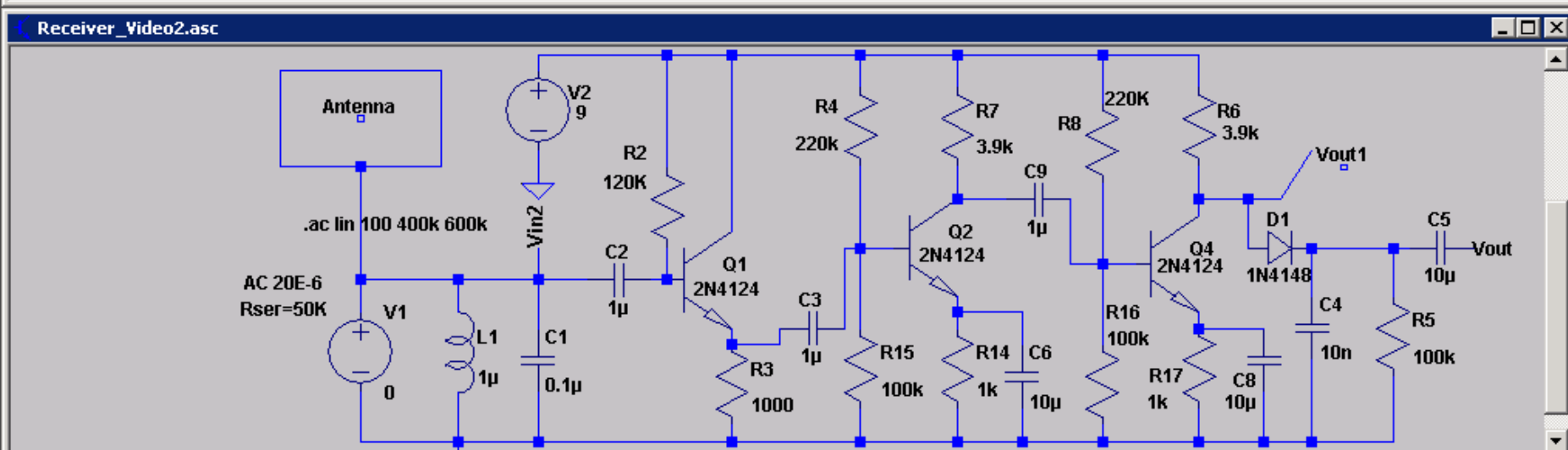 


AM RECEIVER SIMULATION

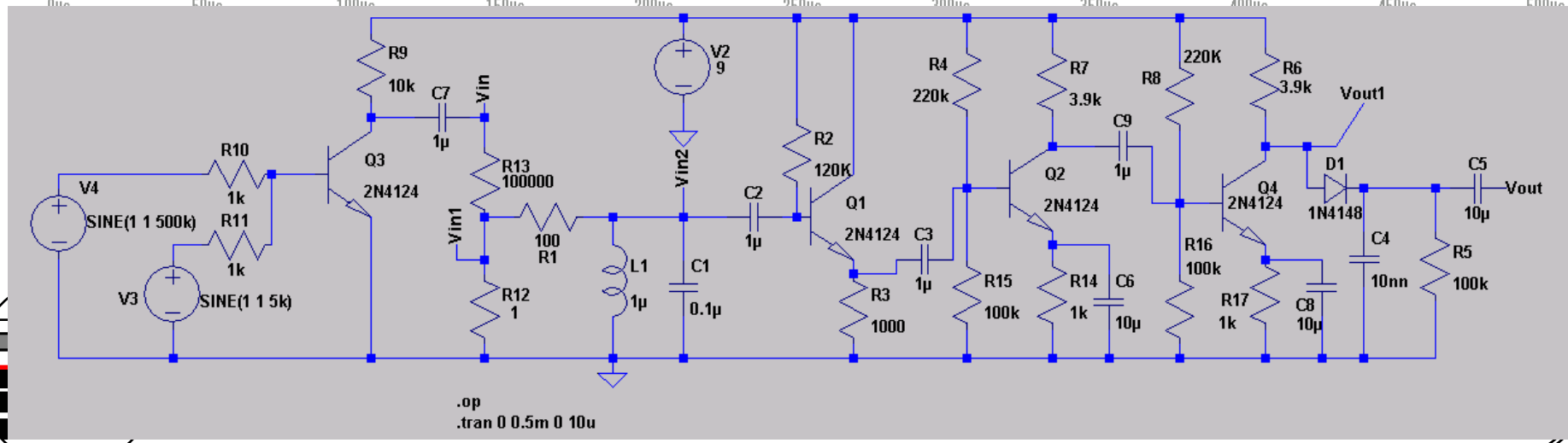 

REFERENCES

 1. MOSFET Modeling with SPICE, Daniel Foty, 1997, Prentice Hall, ISBN-0-13-227935-5
2. Operation and Modeling of the MOS Transistor, 2nd Edition, Yannis Tsividis, 1999, McGraw-Hill, ISBN-0-07-065523-5
3. UTMOST III Modeling Manual-Vol.1. Ch. 5. From Silvaco International.
4. ATHENA USERS Manual, From Silvaco International.
5. ATLAS USERS Manual, From Silvaco International.
6. Device Electronics for Integrated Circuits, Richard Muller and Theodore Kamins, with Mansun Chan, 3rd Edition, John Wiley, 2003, ISBN 0-471-59398-2
7. ICCAP Manual, Hewlet Packard
8. PSpice Users Guide.



HOMWORK – SPICE EXAMPLES

Do SPICE for one of the following:

1. Do a SPICE simulation for one of the more complicated examples shown in this document.
2. Do a SPICE simulation for a completely different circuit not shown in this document.

