

ROCHESTER INSTITUTE OF TECHNOLOGY
MICROELECTRONIC ENGINEERING

Introduction to Modeling MOSFETS in SPICE

Dr. Lynn Fuller

**Electrical and Microelectronic Engineering
Rochester Institute of Technology**

**82 Lomb Memorial Drive
Rochester, NY 14623-5604**


Tel (585) 475-2035

Fax (585) 475-5041

Dr. Fuller's Webpage: <http://people.rit.edu/lffeee>


Email: Lynn.Fuller@rit.edu

 Dept Webpage: <http://www.microe.rit.edu>



ADOBE PRESENTER

 This PowerPoint module has been published using Adobe Presenter. Please click on the **Notes** tab in the left panel to read the instructors comments for each slide. Manually advance the slide by clicking on the **play** arrow or pressing the **page down** key.



OUTLINE

Introduction
MOSFET
SPICE
Shichman and Hodges Model
MOSFET Attributes
Changing MOSFET SPICE Model
Ids-Vds Family of Curves
Ids-Vgs
Measured MOSFET Characteristics
AC Attributes
Ring Oscillator
Summary
References
Homework

INTRODUCTION


PSpice Lite 9.2 is one of the OrCAD family of products, from Cadence Design Systems, Inc., offering a complete suite of electronic design tools. It is free and includes limited versions of OrCAD Capture, for schematic capture, PSpice for analog circuit simulation and Pspice A/D for mixed analog and digital circuit simulation. PSpice Lite 9.2 is limited to 64 nodes, 10 transistors, two operational amplifiers and 65 primitive digital devices. See page 35 (xxxv) of the PSpice Users Guide.

LT SPICE – is a free SPICE simulator with schematic capture from Linear Technology. It is quite similar to PSpice Lite but is not limited in the number of devices or nodes. Linear Technology (LT) is one of the industry leaders in analog and digital integrated circuits. Linear Technology provides a complete set of SPICE models for LT components.


MOSFET DEVICE MODELS

MOSFET Device models used by SPICE (Simulation Program for Integrated Circuit Engineering) simulators can be divided into three classes: First Generation Models (Level 1, Level 2, Level 3 Models), Second Generation Models (BISM, HSPICE Level 28, BSIM2) and Third Generation Models (BSIM3, Level 7, Level 8, Level 49, etc.) The newer generations can do a better job with short channel effects, local stress, transistors operating in the sub-threshold region, gate leakage (tunneling), noise calculations, temperature variations and the equations used are better with respect to convergence during circuit simulation.

 In general first generation models are recommended for MOSFETs with gate lengths of 10 μ m or more. If not specified most SPICE MOSFET Models default to level=1 (Shichman and Hodges)




SPICE LEVEL-1 MOSFET MODEL

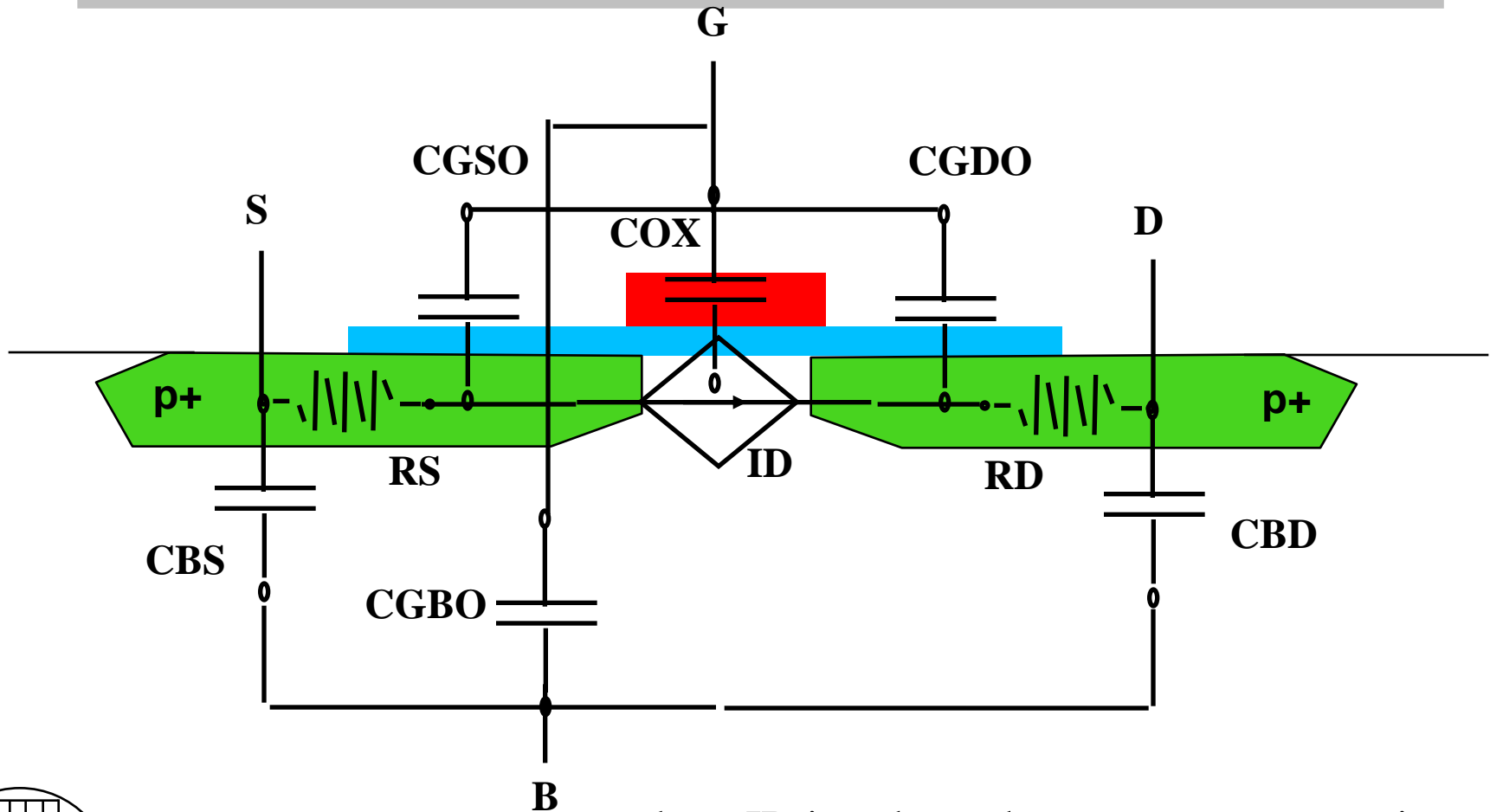

where ID is a dependent current source using the equations on the next page

SPICE LEVEL 1 - SHICHMAN AND HODGES

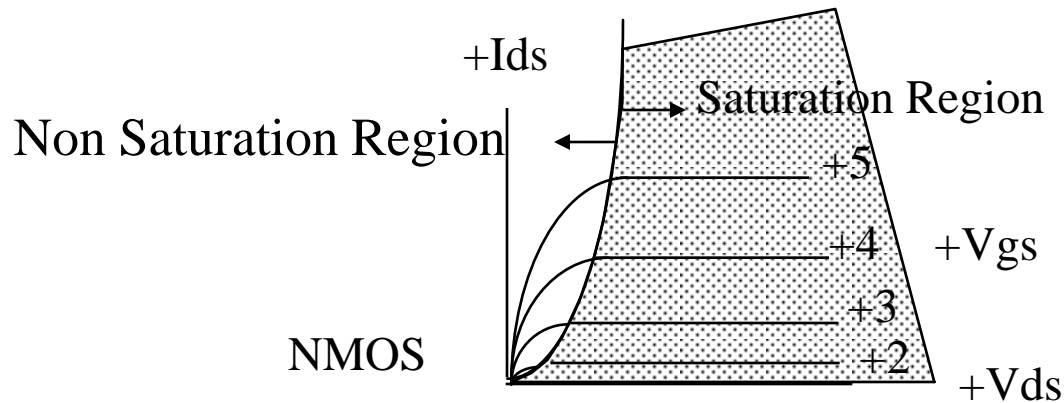

$$I_{Dsat} = \frac{\mu W Cox'}{2L} (Vg - Vt)^2$$

Saturation Region

$$I_D = \frac{\mu W Cox'}{L} (Vg - Vt - V_d/2) V_d$$

Non Saturation Region

where μ , Cox' and Vt are given in equations on the next pages

SPICE LEVEL-1 EQUATIONS FOR μ_0 , V_{TO} AND C_{OX}'

Mobility:
(cm²/V-s)

$$\mu = \mu_{\min} + \frac{(\mu_{\max} - \mu_{\min})}{\{1 + (N/N_{\text{ref}})^\alpha\}}$$

Parameter	Arsenic	Phosphorous	Boron
μ_{\min}	52.2	68.5	44.9
μ_{\max}	1417	1414	470.5
N_{ref}	9.68×10^{16}	9.20×10^{16}	2.23×10^{17}
α	0.680	0.711	0.719

Threshold Voltage:
+/-
nmos/pmos

$$V_{TO} = \Phi_{ms} - q \text{NSS}/C_{ox}' \pm 2[\Phi F] \pm 2 (q\epsilon_0\epsilon_{rsi} \text{NSUB} [\Phi F])^{0.5}/C_{ox}'$$

$$[\Phi F] = (KT/q) \ln(\text{NSUB}/n_i) \quad \text{where } n_i = 1.45E10 \text{ and } KT/q = 0.026$$

Absolute value


Gate Capacitance
per unit area C_{ox}'

$$C_{ox}' = \epsilon_{rox} \epsilon_0 / TOX = 3.9 \epsilon_0 / TOX$$


$$\text{PHI} = 2 [\Phi F]$$

where $\epsilon_{rsi} = 11.7$ and $\epsilon_{rox} = 3.9$

 $\epsilon_0 = 8.85E-12$ F/m or $8.8E-14$ F/cm
 $q = 1.6E-19$



MOBILITY MODEL

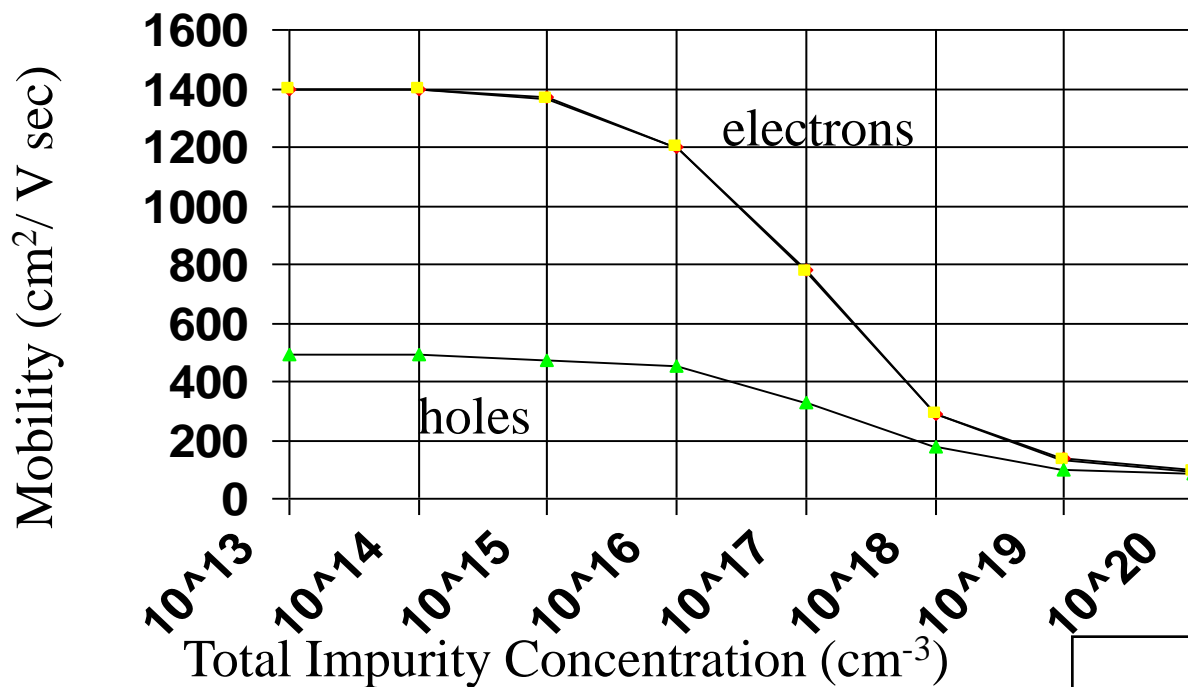


Electron and hole mobilities in silicon at 300 K as functions of the total dopant concentration (N). The values plotted are the results of the curve fitting measurements from several sources. The mobility curves can be generated using the equation below with the parameters shown:

$$\mu(N) = \mu_{mi} + \frac{(\mu_{max} - \mu_{min})}{\{1 + (N/N_{ref})^\alpha\}}$$

From Muller and Kamins, 3rd Ed., pg 33

Rochester Institute of Technology
Microelectronic Engineering

Parameter	Arsenic	Phosphorous	Boron
μ_{min}	52.2	68.5	44.9
μ_{max}	1417	1414	470.5
N_{ref}	9.68×10^{16}	9.20×10^{16}	2.23×10^{17}
α	0.680	0.711	0.719

 

LONG CHANNEL THRESHOLD VOLTAGE, V_T

Flat-band Voltage $V_{FB} = \phi_{ms} - \frac{Q_{ss}}{C'_{ox}} - \frac{1}{C'_{ox}} \int_0^{X_{ox}} \frac{X \rho(x)}{X_{ox}} dx$

p-type substrate
(n-channel)
n-type substrate
(p-channel)
 $Q_{ss} = q N_{ss}$

Bulk Potential : $\phi_p = -KT/q \ln (N_A/n_i)$

$\phi_n = +KT/q \ln (N_D/n_i)$

Work Function Difference $\phi_{MS} = \phi_M - (X + Eg/2q + [\phi_p])$


$\phi_{MS} = \phi_M - (X + Eg/2q - [\phi_n])$

Maximum Depletion Width:
(W_{dmax}) $\sqrt{\frac{4 \epsilon_s [\phi_p]}{qNa}}$

$\sqrt{\frac{4 \epsilon_s [\phi_n]}{qNd}}$



Threshold Voltage:
p-type substrate $V_T = V_{FB} + 2 [\phi_p] + \frac{1}{C'_{ox}} \sqrt{2 \epsilon_s q Na (2[\phi_p] + V_{sb})}$

 Threshold Voltage:
n-type substrate $V_T = V_{FB} - 2 [\phi_n] - \frac{1}{C'_{ox}} \sqrt{2 \epsilon_s q Nd (2[\phi_n] + V_{bs})}$



BACK-BIASING EFFECTS – GAMMA

Body Effect coefficient GAMMA or γ :

  

$$\gamma = \frac{1}{C'_{ox}} \sqrt{2q\epsilon_{si} N_{sub}}$$

$$V_T = \Phi_{MS} - \frac{Q_{SS}}{C'_{ox}} + 2\phi_F + \gamma \sqrt{2\phi_F + V_{SB}}$$

where

$$\begin{aligned} \epsilon_{r\ si} &= 11.7 \text{ and } \epsilon_{r\ ox} = 3.9 \\ \epsilon_0 &= 8.8eE-14F/cm \\ q &= 1.6E-19 \end{aligned}$$

VT ADJUST IMPLANT

The threshold voltage can be adjusted with an ion implant. If total implant dose is shallow (within W_{dmax}) then the change in V_t is:


$$\pm \Delta V_t = q \text{Dose}^* / C_{ox}'$$

where Dose^* is the dose that is added to the Si
 C_{ox}' is gate oxide capacitance/cm²
 $C_{ox}' = \epsilon_0 \epsilon_r / X_{ox}$

Boron gives + shift
 Phosphorous gives - shift

Maximum Depletion Width:
 
$$W_{dmax} = \sqrt{\frac{4 \epsilon_s [\phi_p]}{qN}}$$





CHANNEL LENGTH MODULATION - LAMBDA

Channel Length Modulation

Parameter λ

  $\lambda = \text{Slope} / I_{\text{dsat}}$



$$I_{\text{Dsat}} = \frac{\mu W C_{\text{ox}}'}{2L} (V_{\text{g}} - V_{\text{t}})^2 (1 + \lambda V_{\text{ds}})$$


Saturation Region

$$I_{\text{D}} = \frac{\mu W C_{\text{ox}}'}{L} (V_{\text{g}} - V_{\text{t}} - V_{\text{d}}/2) V_{\text{d}} (1 + \lambda V_{\text{ds}})$$


Non Saturation Region

NMOS Transistor

 DC Model, λ is the channel length modulation parameter and is different for each channel length, L. Typical value might be 0.02



TRANSISTOR PROPERTIES OR ATTRIBUTES

 


$$\begin{aligned} L &= 2u \\ W &= 8u \\ A_d &= 8u \times 10u = 80p \\ A_s &= A_d = 80p \\ P_d &= 8u + 10u + 8u + 10u = 36u \\ P_s &= P_d = 36u \\ N_{rs} &= 1 \\ N_{rd} &= 1 \end{aligned}$$

NMOS 2/8

Rochester Institute of Technology
Microelectronic Engineering


LTSPICE MOSFET ATTRIBUTES

MOSFETS are four terminal devices (Drain, Gate, Source and Substrate). L and W are channel length and width in meters, A_d and A_s are area of drain and source in square meters. If not specified default values are used. (see next page) Perimeter of Drain and source (P_D and P_S) in meters is used to calculate drain and source side wall capacitance. If P_D and P_S are not given the default is zero. N_{RD} and N_{RS} are multiplied by the drain and source sheet resistance to give series resistance R_D and R_S . The default value for N_{RD} and N_{RS} is one.

 

LTSPICE MOSFET ATTRIBUTE DEFAULT VALUES

Name	Description	Unit	Default	Example
L	Default Length	m	defl	100u
W	Default Width	m	defw	100u
Ad	Default drain area	m ²	defad	1000p
As	Default source area	m ²	defas	1000p
Pd	Default drain perimeter	m	0	200u
Ps	Default source perimeter	m	0	200u
Nrd	Default drain squares	-	1	1
Nrs	Default source squares	-	1	1
Nrg	Default gate squares	-	0	1
Nrb	Default bulk squares	-	0	1
Lmin	Bin length lower limit	m	0	10u
Lmax	Bin length upper limit	m	0	20u
Wmin	Bin width lower limit	m	0	10u
Wmax	Bin width upper limit	m	0	20u

 




MOSFET DEFINITION - LTSPICE

For example:

- * SPICE Input File
- * MOSFET names start with M.... **M2** is the name for the MOSFET below and its drain, gate, source and substrate is connected to nodes 3,2,0,0 respectively. The model name is **RITSUBN7**.
- * The parameters/attributes is everything after that.

M2 3 2 0 0 **RITSUBN7** L=2U W=16U ad=96e-12 as=96e-12 pd=44e-6 ps=44e-6 nrd=1.0 nrs=1.0

*
*

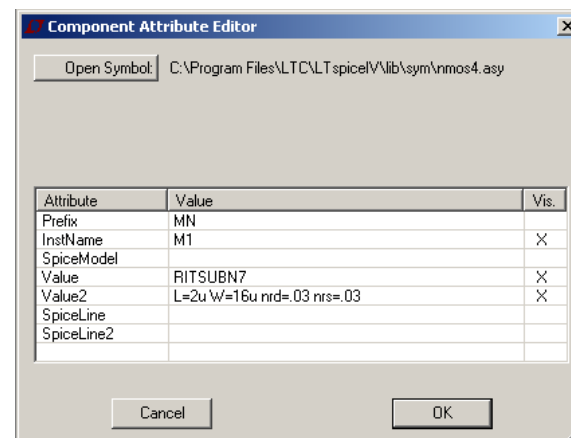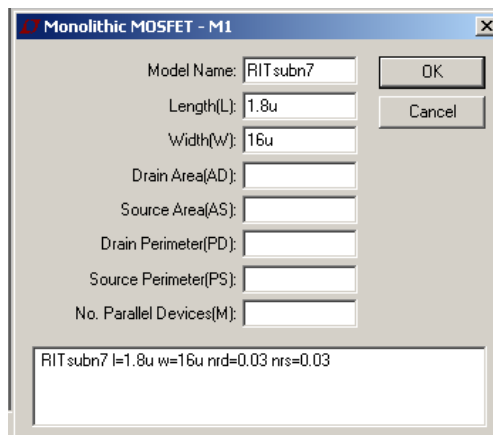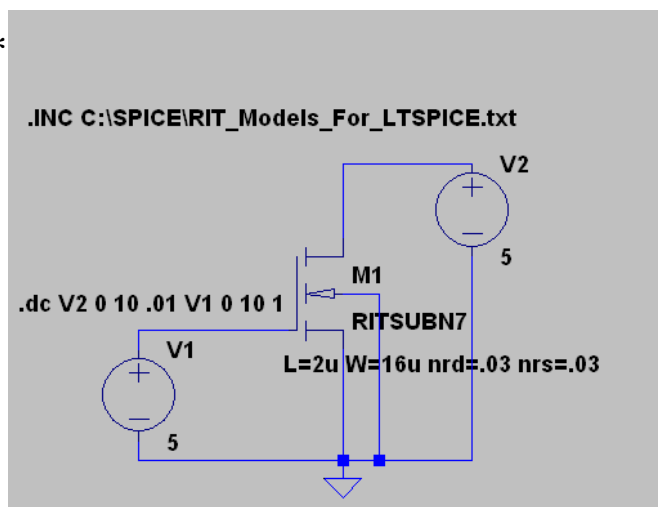

LTSPICE schematic showing **.Include** and **.dc** sweep commands. Properties dialog box to define L and W values. Note: attributes with no entry field **nrs** and **nrd** are typed in bottom box. Attribute Editor (CTRL R-click on the transistor) allows attributes with Vis.=X to be displayed on the schematic.

MOSFET DEFINITION - PSPICE


For example:

- * SPICE Input File
- * MOSFET names start with M.... **M2** is the name for the MOSFET below and its drain, gate, source and substrate is connected to nodes 3,2,0,0 respectively. The model name is **RITSUBN7**.
- * The parameters/attributes is everything after that.

```
M2 3 2 0 0 RITSUBN7 L=2U W=16U ad=96e-12 as=96e-12 pd=44e-6 ps=44e-6 nrd=1.0 nrs=1.0
```

*


*

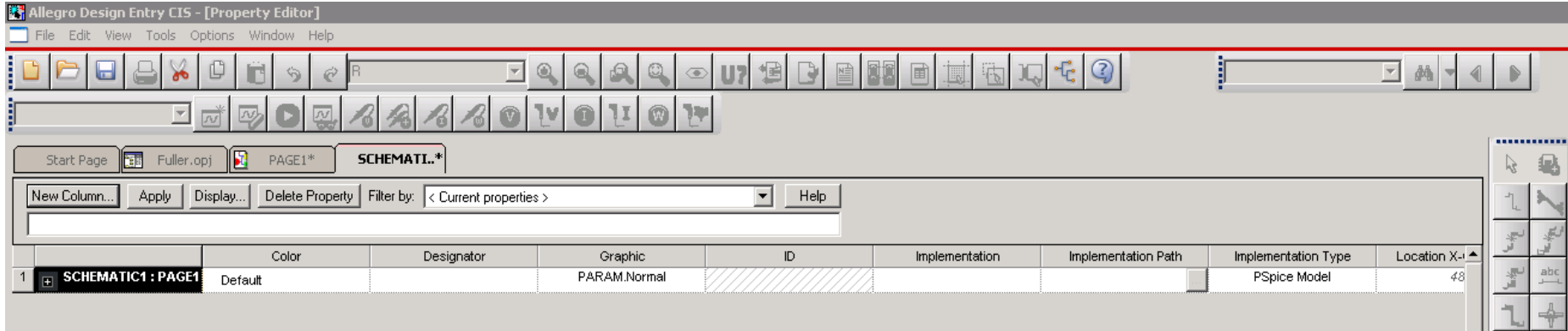

In PSPICE the Attribute Editor (CTRL R-click on the transistor) allows attributes values to be set, new attribute columns to be created, and attributes can be selected to be displayed on the schematic..

MOSFET DEFINITION - PSPICE

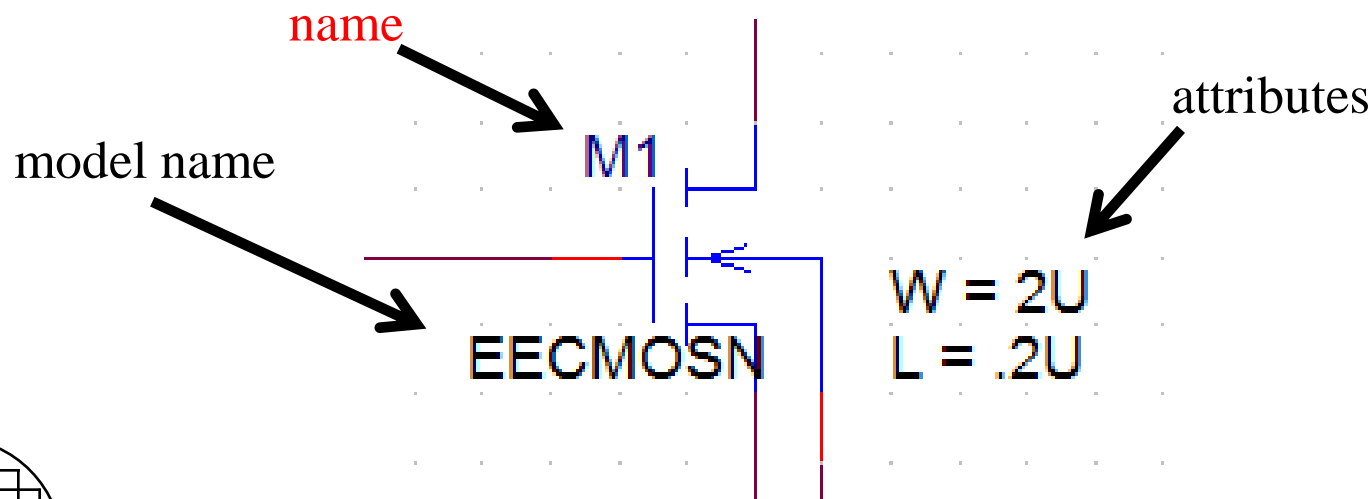In SPICE a transistor is defined by its **name** and associated **properties or attributes** and its **model**. MOSFET names start with M, attributes (L, W, Ad, As, etc.) are specified by the user and shown in the input file net list. Some attributes can be displayed on the schematic. The model is specified in a file in a given location or is defined in a library.



CHANGING THE MOSFET SPICE MODEL IN LTSPICE

There are several ways to change the MOSFET SPICE model. A good way to do it is to create a text file on your computer and put your models in that text file and save it in some folder. You can copy models from Dr. Fuller's webpage to start your collection of models.

See: <http://people.rit.edu/lffeee/CMOS.htm>


Example contents of that file is shown on the page below.

Next you change the model name for your transistor by right click on the model name shown in your schematic and typing the model name used in the model file. (for example: RITSUBN7)

Finally you place a SPICE directive on your schematic by clicking on the .op icon on the top banner and type the following command:

```
.include Drive:\path\folder\filename
```

 For example ***.include C:\SPICE\RIT_Models_For_LTSPICE.txt***



SIMPLE AND ADVANCED SPICE MODELS

* From Electronics II EEEE482 FOR ~100nm Technology

```
.model EECMOSN NMOS (LEVEL=8  
+VERSION=3.1 CAPMOD=2 MOBMOD=1  
+TOX=5E-9 XJ=1.84E-7 NCH=1E17 NSUB=5E16 XT=5E-8  
+VTH0=0.4 U0= 200 WINT=1E-8 LINT=1E-8  
+NGATE=5E20 RSH=1000 JS=3.23E-8 JSW=3.23E-8 CJ=6.8E-4 MJ=0.5 PB=0.95  
+CJSW=1.26E-10 MJSW=0.5 PBSW=0.95 PCLM=5  
+CGSO=3.4E-10 CGDO=3.4E-10 CGBO=5.75E-10)  
*
```

* From Electronics II EEEE482 FOR ~100nm Technology


```
.model EECMOSP PMOS (LEVEL=8  
+TOX=5E-9 XJ=0.05E-6 NCH=1E17 NSUB=5E16 XT=5E-8  
+VTH0=-0.4 U0= 100 WINT=1E-8 LINT=1E-8  
+NGATE=5E20 RSH=1000 JS=3.51E-8 JSW=3.51E-8 CJ=5.28E-4 MJ=0.5 PB=0.94  
+CJSW=1.19E-10 MJSW=0.5 PBSW=0.94 PCLM=5  
+CGSO=4.5E-10 CGDO=4.5E-10 CGBO=5.75E-10)  
*
```

* From Electronics II EEEE482 SIMPLE MODEL

```
.model EENMOS NMOS (VTO=0.4 KP=432E-6 GAMMA=0.2 PHI=.88)  
*
```

* From Electronics II EEEE482 SIMPLE MODEL
 
```
.model EEPMOS PMOS (VTO=-0.4 KP=122E-6 GAMMA=0.2 PHI=.88)
```



CHANGING THE MOSFET SPICE MODEL IN PSPICE

The screenshot displays the Cadence AMS Model Editor interface. The main window shows the model definition for 'Mbreakn' as an NMOS device with the following parameters: `.model Mbreakn NMOS vto=0.4 kp=432u gamma=0.2 phi=0.88 l=0.1u`. The parameters `l=0.1u` and `kp=432u` are underlined in red. A red arrow points to the text 'Right click and select EDIT SPICE MODEL to type in underlined parameters'. Below this, a schematic diagram shows a MOSFET model named 'M1' with parameters 'W = 2U' and 'L = .2U'. The schematic includes a 0Vdc source (V1), a MOSFET (M1), and a 0.1V source (V2). A red box highlights the schematic with the text 'L and W shown on the schematic override default values'. On the right, a list of model parameters is shown, including LEVEL, L, W, VTC, KP, GAMMA, PHI, LAMBDA, IS, JS, PB, PBSW, CJ, CJSW, CGSC, CGDC, CGBC, TOX, XJ, UCRIT, DIOMOD, VFB, LETA, WETA, UO, TEMP, VDD, and XPART.

Models List

Model Name	Type
Mbreakn	MOS

```
.model Mbreakn NMOS vto=0.4 kp=432u gamma=0.2 phi=0.88 l=0.1u
```

Right click and select EDIT SPICE MODEL to type in underlined parameters


L and W shown on the schematic override default values

View output file to see this listing of spice model parameters including default values for L and W

```
63:          LEVEL      1
64:          L          100.000000E-09
65:          W          100.000000E-06
66:          VTC        .4
67:          KP          432.000000E-06
68:          GAMMA       .2
69:          PHI         .88
70:          LAMBDA      0
71:          IS          10.000000E-15
72:          JS          0
73:          PB          .8
74:          PBSW        .8
75:          CJ          0
76:          CJSW        0
77:          CGSC        0
78:          CGDC        0
79:          CGBC        0
80:          TOX         0
81:          XJ          0
82:          UCRIT       10.000000E+03
83:          DIOMOD      1
84:          VFB         0
85:          LETA        0
86:          WETA        0
87:          UO          0
88:          TEMP        0
89:          VDD         5
90:          XPART       0
91:
92:
```

CHANGING THE MOSFET SPICE MODEL IN PSPICE

```
RIT_Models_For_LTSPICE.txt - Notepad
File Edit Format View Help
*SPICE MODELS FOR RIT DEVICES - DR. LYNN FULLER 12-9-2013
*LOCATION DR.FULLER'S COMPUTER DESKTOP/SPICE/MODELS/
*and also at: http://people.rit.edu/lffeee/CMOS.htm
*.model RITMEMDIODE D IS=3.02E-9 N=1 RS=207
+VJ=0.6 CJO=200e-12 M=0.5 BV=400
*.
*.model solarcell D IS=235e-9 N=1 RS=6.85 CJO=200e-12 M=0.5 BV=400
*.
*4-4-2013
.MODEL RITSUBN7 NMOS (LEVEL=7
+VERSION=3.1 CAPMOD=2 MOBMOD=1
+TOX=1.5E-8 XJ=1.84E-7 NCH=1.45E17 NSUB=5.33E16 XT=8.66E-8
+VTH0=1.0 U0= 600 WINT=2.0E-7 LINT=1E-7
+NGATE=5E20 RSH=1082 JS=3.23E-8 JSW=3.23E-8 CJ=6.8E-4 MJ=0.5 PB=0.95
+CJSW=1.26E-10 MJSW=0.5 PBSW=0.95 PCLM=5
+CGSO=3.4E-10 CGDO=3.4E-10 CGBO=5.75E-10)
*.
*4-4-2013
.MODEL RITSUBP7 PMOS (LEVEL=7
+VERSION=3.1 CAPMOD=2 MOBMOD=1
+TOX=1.5E-8 XJ=2.26E-7 NCH=7.12E16 NSUB=3.16E16 XT=8.66E-8
+VTH0=-1.0 U0= 376.72 WINT=2.0E-7 LINT=2.26E-7
+NGATE=5E20 RSH=1347 JS=3.51E-8 JSW=3.51E-8 CJ=5.28E-4 MJ=0.5 PB=0.94
+CJSW=1.19E-10 MJSW=0.5 PBSW=0.94
+CGSO=4.5E-10 CGDO=4.5E-10 CGBO=5.75E-10)
*.
* From Electronics I EEEE481
.model1 EENMOS2 NMOS LEVEL=2
+VTO=0.7 KP=25E-6 LAMBDA=0.02 GAMMA=0.9 TOX=90E-9 NSUB=3.7E15
*.
* From Electronics II EEEE482
.MODEL QRITNPN NPN (BF=416 IKF=.06678 ISE=6.734E-15 IS=6.734E-15 NE=1.259 RC=1 RB=10 VA=109)
*.
* From Electronics II EEEE482 FOR ~100nm Technolog
.model1 EECMOSN NMOS (LEVEL=8
+VERSION=3.1 CAPMOD=2 MOBMOD=1
+TOX=5E-9 XJ=1.84E-7 NCH=1E17 NSUB=5E16 XT=5E-8
+VTH0=0.4 U0= 200 WINT=1E-8 LINT=1E-8
+NGATE=5E20 RSH=1000 JS=3.23E-8 JSW=3.23E-8 CJ=6.8E-4 MJ=0.5 PB=0.95
+CJSW=1.26E-10 MJSW=0.5 PBSW=0.95 PCLM=5
+CGSO=3.4E-10 CGDO=3.4E-10 CGBO=5.75E-10)
*.
* From Electronics II EEEE482 FOR ~100nm Technology
.model1 EECMOSP PMOS (LEVEL=8
+TOX=5E-9 XJ=0.05E-6 NCH=1E17 NSUB=5E16 XT=5E-8
+VTH0=-0.4 U0= 100 WINT=1E-8 LINT=1E-8
+NGATE=5E20 RSH=1000 JS=3.51E-8 JSW=3.51E-8 CJ=5.28E-4 MJ=0.5 PB=0.94
+CJSW=1.19E-10 MJSW=0.5 PBSW=0.94 PCLM=5
+CGSO=4.5E-10 CGDO=4.5E-10 CGBO=5.75E-10)
*.
* From Electronics II EEEE482 SIMPLE MODEL
.model1 EENMOS NMOS (VTO=0.4 KP=432E-6 GAMMA=0.2 PHI=.88)
*.
* From Electronics II EEEE482 SIMPLE MODEL
.model1 EEPMOS PMOS (VTO=-0.4 KP=122E-6 GAMMA=0.2 PHI=.88)
```

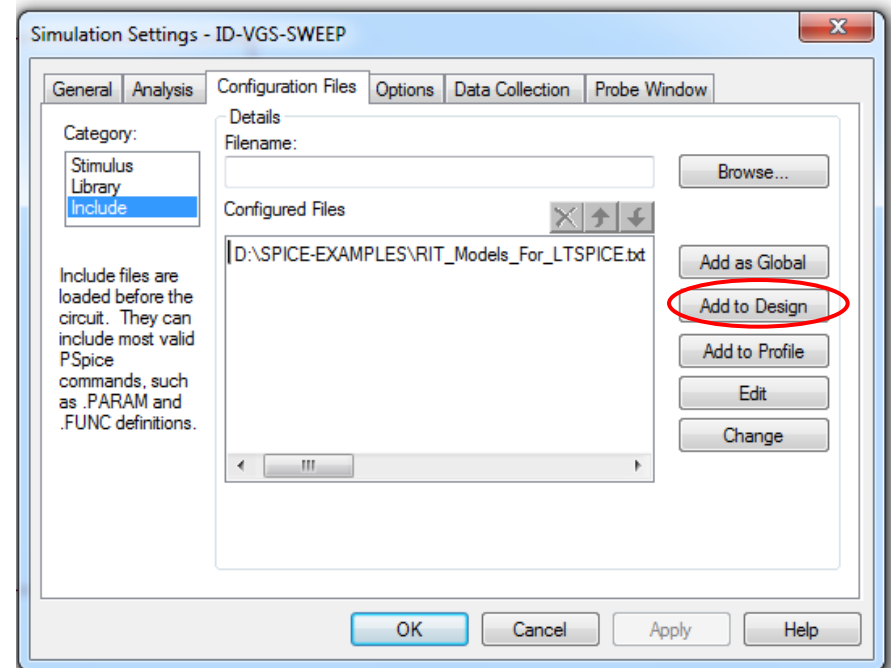


In PSPICE models saved in a text file can be included as a configuration file in the Simulation Settings dialog box as shown above. Change the component model name to the model name in the text file.

COMPARISON OF MOSFET CHARACTERISTICS

The circuit shown can be used to see the transistor family of I_{ds} - V_{ds} curves, I_{ds} - V_{gs} plot and I_{ds} - V_{gs} (I_{ds} on log scale) Subthreshold plot. We can investigate the effect of changing attributes, SPICE model and model parameters.

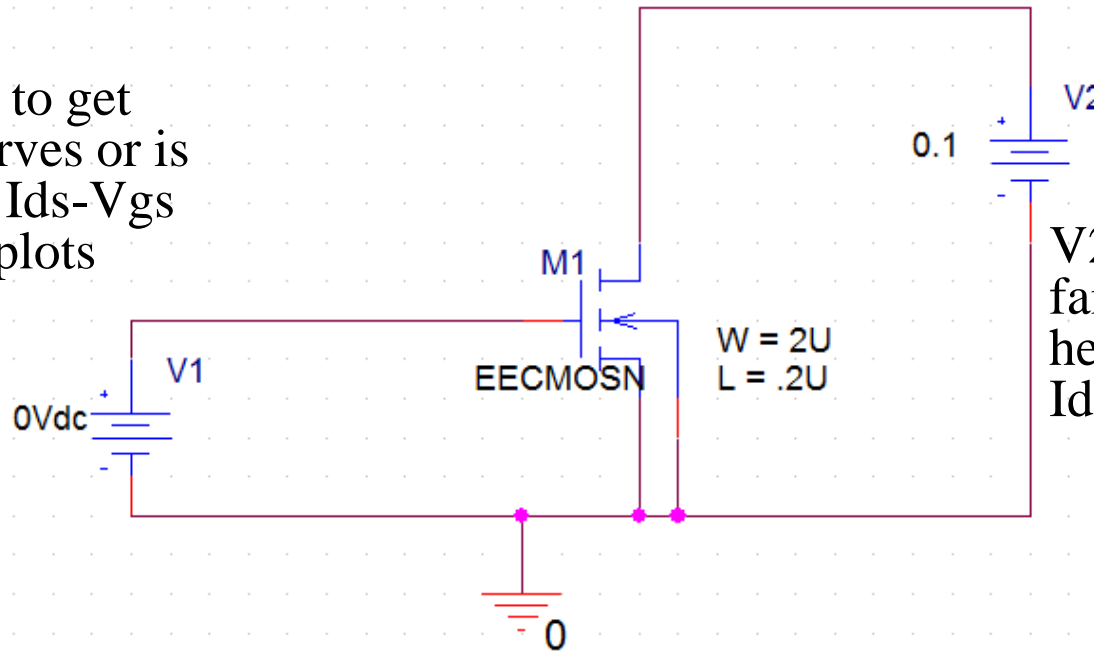V_1 is stepped to get family of curves or is swept to get I_{ds} - V_{gs} and Sub- V_t plots



V_2 is swept to get family of curves or is held constant to get I_{ds} - V_{gs} plots

PSPICE MOSFET MODEL PARAMETERS

95 mosfet model parameters used by cadence PSPICE for **Level 8** BSIM

31 mosfet model parameters used by cadence PSPICE for **Level 1** Shichman and Hodges

```


Start Page FullerMOS... PAGE1*
280:          EECMOSP
281:          FMOS
282:          LEVEL      8
283:          L      100.000000E-06
284:          W      100.000000E-06
285:          VTC      -.4
286:          KP      414.377300E-06
287:          GAMMA      0
288:          PHI
289:          LAMBDA      0
290:          RSH      1.000000E+03
291:          IS      1.000000E-15
292:          JS      35.100000E-09
293:          JSSW      35.100000E-09
294:          PB      .94
295:          PBSW      .94
296:          CJ      528.000000E-06
297:          CJSW      119.000000E-12
298:          MJSW      .5
299:          CGSC      450.000000E-12
300:          CGDC      450.000000E-12
301:          CGBC      575.000000E-12
302:          NSUB      50.000000E+15
303:          TOX      5.000000E-09
304:          XJ      50.000000E-09
305:          UCRIT      10.000000E+03
306:          DIOMOD      1
307:          VFB      -1
308:          LETA      0
309:          WETA      0
310:          UO      100
311:          TEMP
312:          VDD
313:          XPART      0
314:          VTH0      -.4
315:          UA      1.000000E-09
316:          UB      100.000000E-21
317:          UC      -46.500000E-12
318:          VSAT      80.000000E+03
319:          RDSW      200
320:          VOFF      -.08
321:          PCLM      5
322:          A0      1
323:          A1      0
324:          A2      1
325:          NPEAK      100.000000E+15
326:          XT      50.000000E-09
327:          LDD      0
328:          LITL      27.386130E-09
329:          UA1      1.000000E-09
330:          UB1      -1.000000E-18
331:          UC1      .025
332:          DSUB      .56
333:          NGATE      500.000000E+18
334:          MOBMOD      0
335:          PRWG      1
336:          LINT      10.000000E-09
337:          WINT      10.000000E-09
338:          DLC      10.000000E-09
339:          DWC      10.000000E-09
340:          CF      107.725800E-12
341:          NOIA      9.900001E+18
342:          NOIB      2.400000E+03
343:          NOIC      1.400000E-12
344:          VERSION      4.1
345:          PBSWG      .94
346:          MJSWG      .5
347:          CJSWG      119.000000E-12
348:          JTSKD      35.100000E-09
349:          JSTSCD      35.100000E-09
350:          TOXM      3.000000E-09
351:          LLC      0
352:          LNC      0
353:          LWLC      0
354:          WLC      0
355:          WWC      0
356:          WWLC      0
357:          BSIM4oxideTrapDensityC      8.750000E+09
358:          toxp      3.000000E-09
359:          eu      1
360:          aigc      .31
361:          bigc      .024
362:          cigc      .03
363:          aigsd      .31
364:          bigsd      .024
365:          cigsd      .03
366:          dlcig      10.000000E-09
367:          dwj      10.000000E-09
368:          CJSWGD      500.000000E-12
369:          PBSWGD      1
370:          CJSWGS      500.000000E-12
368:          CJSWGD      500.000000E-12
369:          PBSWGD      1
370:          CJSWGS      500.000000E-12
371:          PBSWGS      1
372:          coxe      .01151
373:          coxp      .01151
374:          BSIM4factor1      94.868330E-06
    
```

View Output File

```

FullerMOS... PAGE1* ID-VGS-SW... SCHEMATI... ID-VGS-5...
          EENMOS          EEPMOS
          NMOS          FMOS
          LEVEL          1          1
          L      100.000000E-06      100.000000E-06
          W      100.000000E-06      100.000000E-06
          VTC          .4          -.4
          KP      432.000000E-06      122.000000E-06
          GAMMA          .2          .2
          PHI          .88          .88
          LAMBDA          0          0
          RSH
          IS      10.000000E-15      10.000000E-15
          JS          0          0
          JSSW
          PB          .8          .8
          PBSW          .8          .8
          CJ          0          0
          CJSW          0          0
          MJSW
          CGSC          0          0
          CGDC          0          0
          CGBC          0          0
          NSUB
          TOX          0          0
          XJ          0          0
          UCRIT          10.000000E+03      10.000000E+03
          DIOMOD          1          1
          VFB          0          0
          LETA          0          0
          WETA          0          0
          UO          0          0
          TEMP          0          0
          VDD          5          5
          XPART          0          0
    
```

LTSPICE CIRCUIT SCHEMATIC

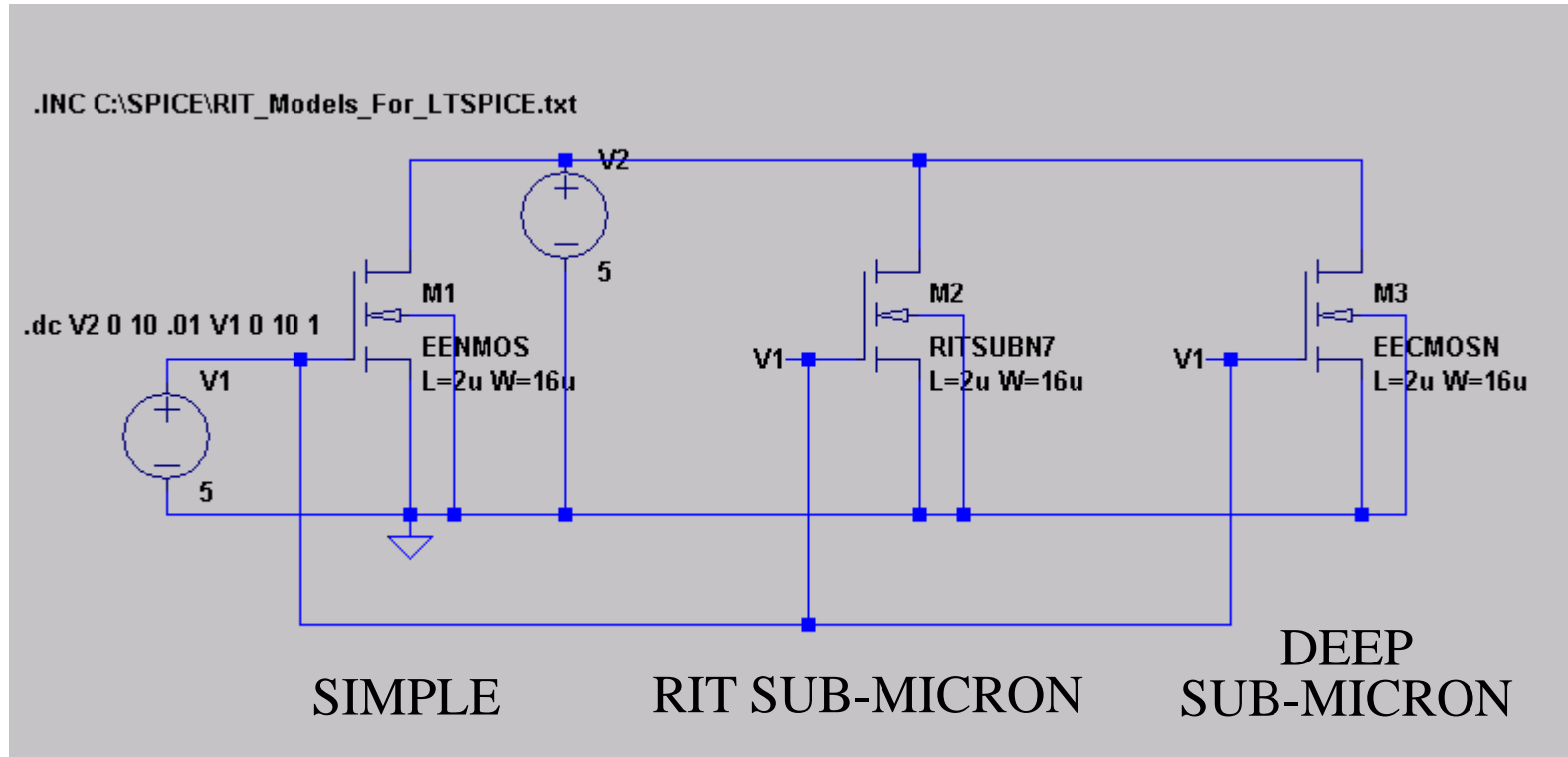

Three transistor all the same $L=2\mu$ and $W=16\mu$ but with different SPICE models. (SIMPLE, RIT SUB-MICRON and 100nm DEEP SUB-MICRON)

THREE DIFFERENT NMOS SPICE MODELS

* From Sub-Micron CMOS Manufacturing Classes in MicroE

```
.MODEL RITSUBN7 NMOS (LEVEL=7  
+VERSION=3.1 CAPMOD=2 MOBMOD=1  
+TOX=1.5E-8 XJ=1.84E-7 NCH=1.45E17 NSUB=5.33E16 XT=8.66E-8  
+VTH0=1.0 U0= 600 WINT=2.0E-7 LINT=1E-7  
+NGATE=5E20 RSH=1082 JS=3.23E-8 JSW=3.23E-8 CJ=6.8E-4 MJ=0.5 PB=0.95  
+CJSW=1.26E-10 MJSW=0.5 PBSW=0.95 PCLM=5  
+CGSO=3.4E-10 CGDO=3.4E-10 CGBO=5.75E-10)
```

*

* From Electronics II EEEE482 FOR ~100nm Technology Deep Sub-Micron



```
.model EECMOSN NMOS (LEVEL=8  
+VERSION=3.1 CAPMOD=2 MOBMOD=1  
+TOX=5E-9 XJ=1.84E-7 NCH=1E17 NSUB=5E16 XT=5E-8  
+VTH0=0.4 U0= 200 WINT=1E-8 LINT=1E-8  
+NGATE=5E20 RSH=1000 JS=3.23E-8 JSW=3.23E-8 CJ=6.8E-4 MJ=0.5 PB=0.95  
+CJSW=1.26E-10 MJSW=0.5 PBSW=0.95 PCLM=5  
+CGSO=3.4E-10 CGDO=3.4E-10 CGBO=5.75E-10)
```

*

* From Electronics II EEEE482 SIMPLE MODEL



```
.model EENMOS NMOS (VTO=0.4 KP=432E-6 GAMMA=0.2 PHI=.88)
```

LTSPICE OUTPUT FOR ID-VDS AND ID-VG

 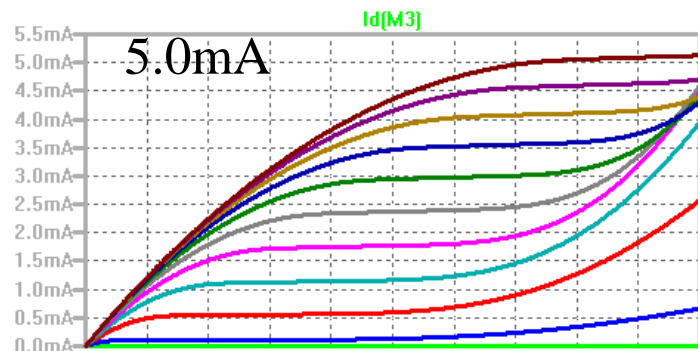



Model is EECMOSN
L=2u W=16u

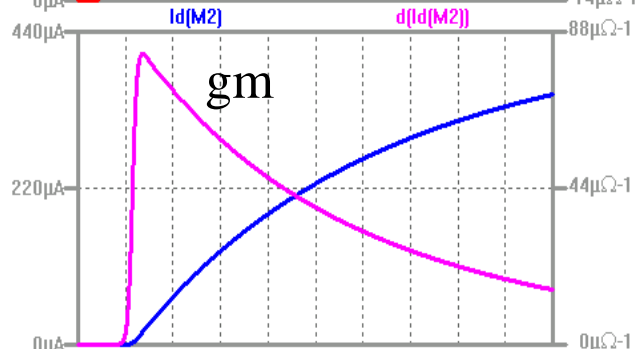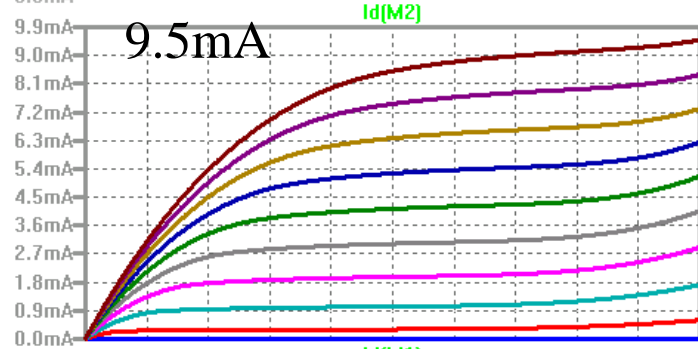Model not good.
Current low and only good out to 3 volts.



Model is RITSUBN7
L=2u W=16u



Model good for RIT
Sub-Micron MOSFETs

  

Model is EENMOS
L=2u W=16u


Model not good current
too large

MEASURED MOSFET ID-VDS AND ID-VGS

 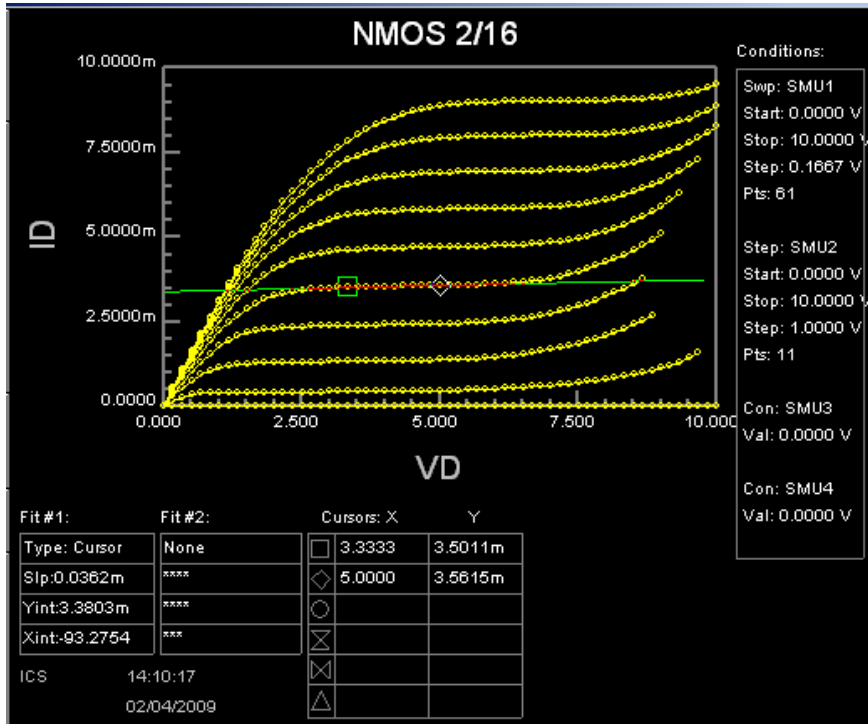

$$I_{max} = 9.5\text{mA}$$

 LTSPICE OUTPUT FOR SUBTHRESHOLD I_D - V_{GS}



Model is EECMOSN
 $L=2\mu$ $W=16\mu$

Model not good MOSFET does not turn off, V_t too low



Model is RITSUBN7
 $L=2\mu$ $W=16\mu$

Model good

Model is EENMOS
 $L=2\mu$ $W=16\mu$



Model incorrect in subthreshold region.
Subthreshold slope not possible.

DEEP SUB-MICRON TRANSISTOR MODELS

  



Model is EECMOSN
L=0.25u W=1.6u

Model good for Deep
Sub-Micron MOSFETs

  

Model is RITSUBN7
L=0.25u W=1.6u

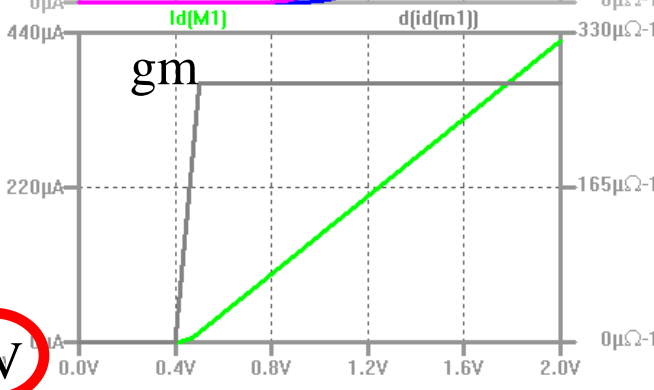 
Model not good too
much short channel
effects



Model is EENMOS
L=0.25u W=1.6u

Model not good current
too large does not show
mobility degradation

DEEP SUB-MICRON TRANSISTOR MODELS

 

Model is EECMOSN
 $L=0.25\mu$ $W=1.6\mu$

Model good for Deep Sub-Micron MOSFETs


Model is RITSUBN7
 $L=0.25\mu$ $W=1.6\mu$

Model not good too much DIBL

Model is EENMOS
 $L=0.25\mu$ $W=1.6\mu$

Model incorrect in subthreshold region


DEEP SUB-MICRON TRANSISTOR MODELS

 

Deep sub-micron transistors show punch through at drain voltages over 3.3 volts. Which is correct.

Problem is worse in the sub-micron transistor because the channel is lighter doped.

Simple model is incorrect.

 

MOSFET MODELS USED BY LTSPICE

LTSPICE uses several different types of MOSFET models including simple, deep submicrometer, Silicon On Insulator (SOI), Vertical double diffused Power MOSFET. Level = 1 is the default if a model level is not specified.

Level

- | | | | |
|----|--|---|-----------------------------------|
| 1 | Shichman and Hodges | } | 1 st generation models |
| 2 | MOS2, Vladimirescu and Liu, UC Berkeley, October 1980 | | |
| 3 | MOS3, a semi-empirical model, UC Berkeley | | |
| 4 | BSIM UC Berkeley, May 1985 | } | 2 nd generation models |
| 5 | BSIM2, UC Berkeley, October 1990 | | |
| 6 | MOS6, UC Berkeley, March 1990 | | |
| 8 | BSIM3V3.3.0, UC Berkeley 2005 | } | 3 rd generation models |
| 9 | BSIMSOI3.2, Silicon on Insulator (SOI), UC Berkeley 2004 | | |
| 14 | BSIM4.6.1, UC Berkeley 2007 | | |
| | more.... | | |

SIMPLE AND ADVANCED SPICE MODEL

* From Electronics II EEEE482 FOR ~100nm Technology

```
.model EECMOSN NMOS (LEVEL=8  
+VERSION=3.1 CAPMOD=2 MOBMOD=1  
+TOX=5E-9 XJ=1.84E-7 NCH=1E17 NSUB=5E16 XT=5E-8  
+VTH0=0.4 U0= 200 WINT=1E-8 LINT=1E-8  
+NGATE=5E20 RSH=1000 JS=3.23E-8 JSW=3.23E-8 CJ=6.8E-4 MJ=0.5 PB=0.95  
+CJSW=1.26E-10 MJSW=0.5 PBSW=0.95 PCLM=5  
+CGSO=3.4E-10 CGDO=3.4E-10 CGBO=5.75E-10)  
*
```

* From Electronics II EEEE482 FOR ~100nm Technology


```
.model EECMOSP PMOS (LEVEL=8  
+TOX=5E-9 XJ=0.05E-6 NCH=1E17 NSUB=5E16 XT=5E-8  
+VTH0=-0.4 U0= 100 WINT=1E-8 LINT=1E-8  
+NGATE=5E20 RSH=1000 JS=3.51E-8 JSW=3.51E-8 CJ=5.28E-4 MJ=0.5 PB=0.94  
+CJSW=1.19E-10 MJSW=0.5 PBSW=0.94 PCLM=5  
+CGSO=4.5E-10 CGDO=4.5E-10 CGBO=5.75E-10)  
*
```

* From Electronics II EEEE482 SIMPLE MODEL


```
.model EENMOS NMOS (VTO=0.4 KP=432E-6 GAMMA=0.2 PHI=.88)  
*
```

* From Electronics II EEEE482 SIMPLE MODEL

 
```
.model EEPMOS PMOS (VTO=-0.4 KP=122E-6 GAMMA=0.2 PHI=.88)
```




CMOS INVERTER WITH LEVEL 1 SPICE MODEL

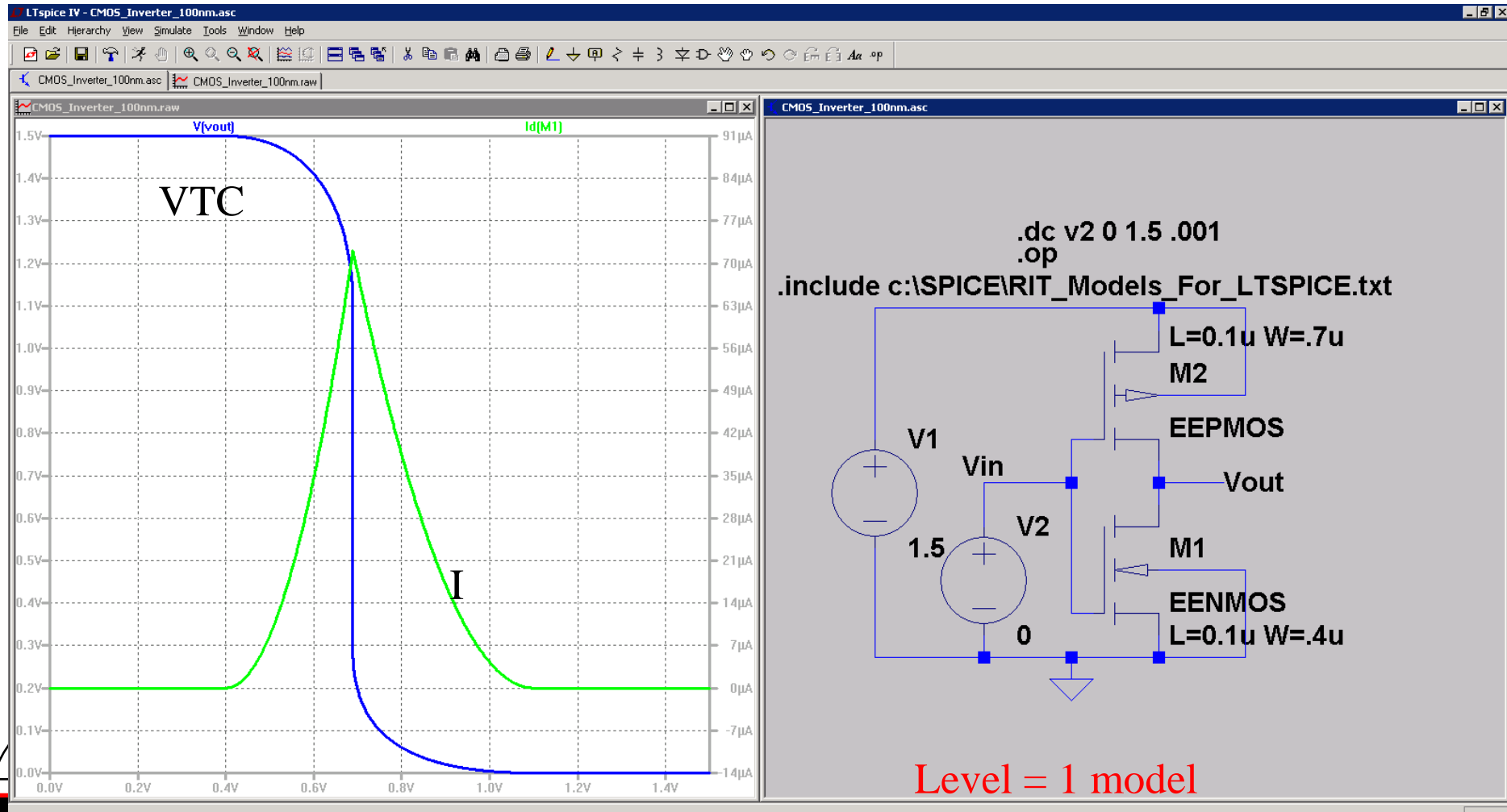

CMOS INVERTER WITH LEVEL 8 SPICE MODEL

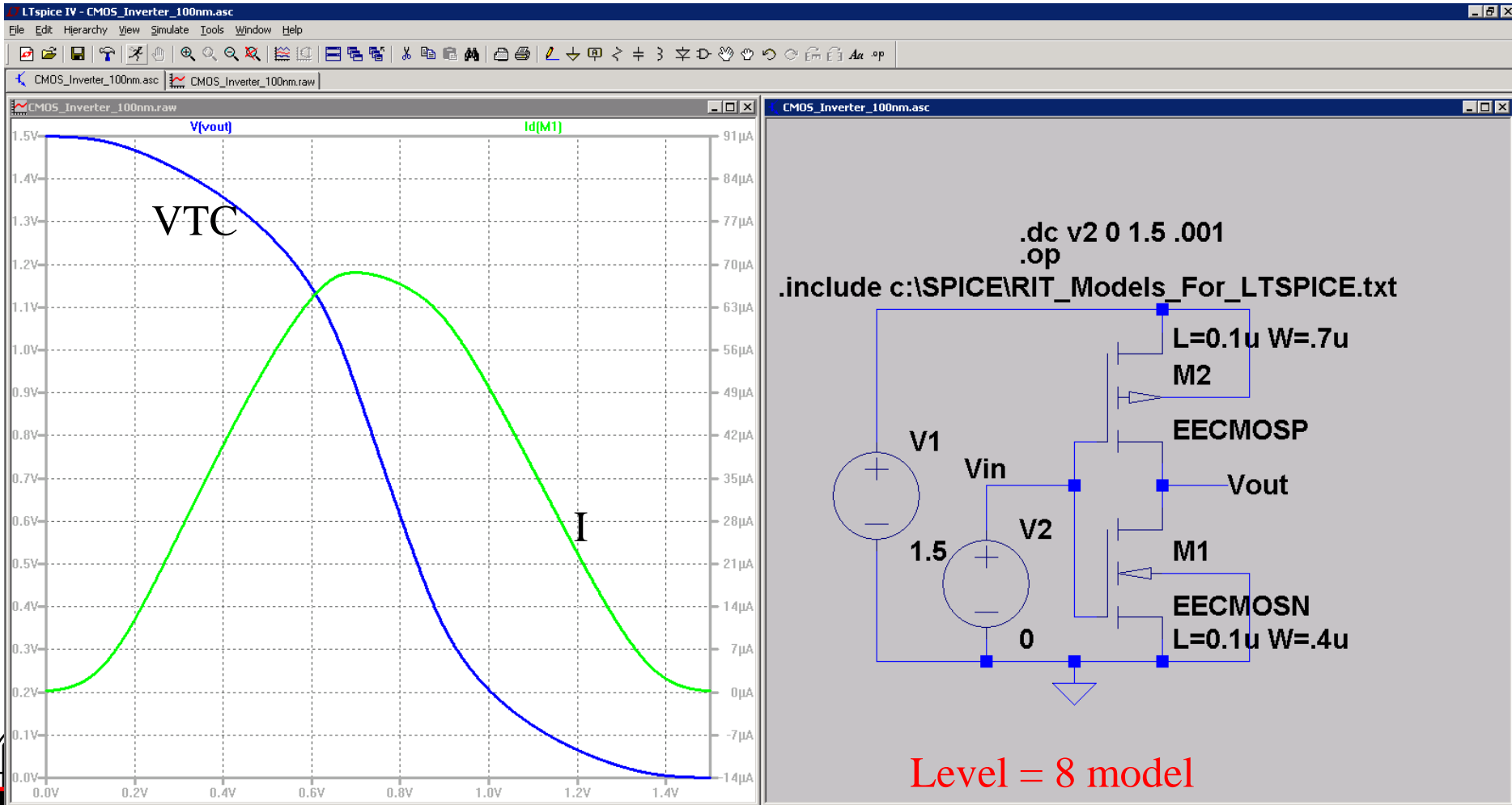

 
MEASURED VTC $L=2\mu\text{m}$ $W=40\mu\text{m}$ CMOS INVERTER



Rochester Institute of Technology
Microelectronic Engineering

$L=2\mu$ and $W=40\mu$


ADVANCED LINEAR DEVICES ALD 1103

 

PMOS


NMOS

 The Advanced Linear Devices ALD1103 is a dual NMOS and PMOS matched pair in a 14 pin package. The ALD 1101 is a dual NMOS matched pair and the ALD 1102 is a dual PMOS matched pair. The 1101/1102 are in an 8 pin package. One chip design for all three products.



MOSFET

10um

 

$L=10\mu\text{m}$

$W \text{ diameter} = 35\mu\text{m}$



$W \text{ each} = \pi D = 110\mu\text{m}$

$W \text{ total} = 8 \times 110 = 880\mu\text{m}$


8 of the donut shaped MOSFETs in parallel form one transistor.

ALD1103 LAYOUT


PIN CONFIGURATION

 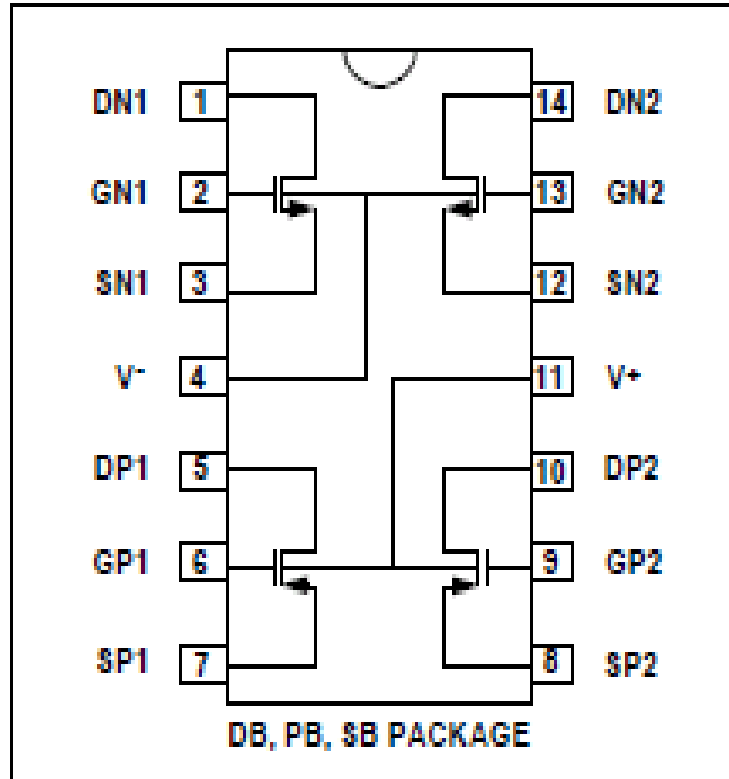

ELECTROSTATIC DISCHARGE - INPUT PAD

 


 Simulation for V_{pad} sweep from -100 to +100 volts
 V_{in} is between -1 and +6 Volts and I is through $M1$ and $M2$ if V_{pad} exceeds supply voltages



ALD1103 MATCHED NMOS AND PMOS MOSFETS

ALD1103 NMOS

 


Conditions:
 Swp: SMU1
 Start: 0.0000 V
 Stop: 5.0000 V
 Step: 0.0833 V
 Pts: 61
 Swp: SMU2
 Start: 0.0000 V
 Stop: 5.0000 V
 Step: 0.5000 V
 Pts: 11
 Con: SMU3
 Val: 0.0000 V
 Con: SMU4
 Val: 0.0000 V

Fit #1:	Fit #2:	Cursors: X	Y
Type: Linear	None	5.0000	0.0385
Slp: 0.0197m	****	4.0000	0.0380
Y-int: 1.5596m	****		
X-int: -79.1126	****		

Measured Id-Vds

ICS 15:02:58
12/16/2013

ALD1103 NMOS ID VGS

 


Conditions:
 Con: SMU1
 Val: 0.1000 V
 Swp: SMU2
 Start: 0.0000 V
 Stop: 5.0000 V
 Step: 0.0500 V
 Pts: 101
 Con: SMU3
 Val: 0.0000 V
 Con: SMU4
 Val: 0.0000 V

Fit #1:	Fit #2:	Cursors: X	Y
Type: Linear	None	0.9500	0.1401m
Slp: 0.6819m	****	1.3000	0.3781m
Y-int: -0.5079m	****	1.1000	0.6871m
X-int: 0.7449	****		

Measured Id-Vgs & gm

ICS

ALD1103 NMOS SUB VT

 

Conditions:
 Step: SMU1
 Start: 0.1000 V
 Stop: 5.0000 V
 Step: 4.9000 V
 Pts: 2
 Swp: SMU2
 Start: 0.0000 V
 Stop: 5.0000 V
 Step: 0.0500 V
 Pts: 101
 Con: SMU3
 Val: 0.0000 V
 Con: SMU4
 Val: 0.0000 V

Fit #1:	Fit #2:	Cursors: X	Y
None	None	4.8000	2.1125m
****	****	4.8000	2.1125m

Measured Sub Vt Id-Vgs

MODEL RITALDN3 NMOS (LEVEL=3
 +TPG=1 TOX=6.00E-8 LD=2.08E-6 WD=4.00E-7
 +U0= 1215 VTO=0.73 THETA=0.222 RS=0.74 RD=0.74 DELTA=2.5
 +NSUB=1.57E16 +XJ=1.3E-6 VMAX=4.38E6 ETA=0.913 KAPPA=0.074 NFS=3E11
 +CGSO=5.99E-10 CGDO=5.99E-10 CGBO=4.31E-10 PB=0.90 XQC=0.4)



Using a LEVEL=3 model should give good results since L is long,
 LEVEL 1 OR 2 will not work

Rochester Institute of Technology
 Microelectronic Engineering


From Dr. Fullers SPICE MOSFET Model
 Parameter Calculator. xls.

ALD1103 LEVEL=3 NMOS SPICE MODEL AND SIMULATION
  
```
.MODEL RITALDN3 NMOS (LEVEL=3 TPG=1 TOX=6.00E-8 LD=2.08E-6 WD=4.00E-7
+U0= 1215 VTO=0.73 THETA=0.222 RS=0.74 RD=0.74 DELTA=2.5 NSUB=1.57E16
+XJ=1.3E-6 VMAX=4.38E6 ETA=0.913 KAPPA=0.074 NFS=3E11
+CGSO=5.99E-10 CGDO=5.99E-10 CGBO=4.31E-10 PB=0.90 XQC=0.4)
```



 This SPICE model gives good matching between measured and simulated curves.



CD4007 DUAL COMPLEMENTARY PAIR + INVERTER



 
 





Figure 4(a). Enlarged CD4007 Pin-Out Diagram

 

 CD4007 DUAL COMPLEMENTARY PAIR + INVERTER





   CD4007 DUAL COMPLEMENTARY PAIR + INVERTER




**.MODEL RIT4007N8 NMOS (LEVEL=8
 +VERSION=3.1 CAPMOD=2 MOBMOD=1
 +TOX=1.5E-8 XJ=1.84E-7 NCH=1.45E17 NSUB=5.33E16 XT=8.66E-8
 +VTH0=1.0 U0= 600 WINT=2.0E-7 LINT=1E-7
 +NGATE=5E20 RSH=1082 JS=3.23E-8 JSW=3.23E-8 CJ=6.8E-4 MJ=0.5 PB=0.95
 +CJSW=1.26E-10 MJSW=0.5 PBSW=0.95 PCLM=5
 +CGSO=3.4E-10 CGDO=3.4E-10 CGBO=5.75E-10)**

  CD4007 DUAL COMPLEMENTARY PAIR + INVERTER



```
.MODEL RIT4007N8 NMOS (LEVEL=8
+VERSION=3.1 CAPMOD=2 MOBMOD=1
+TOX=1.5E-8 XJ=1.84E-7 NCH=1.45E17 NSUB=5.33E16 XT=8.66E-8
+VTH0=1.6 U0= 600 WINT=2.0E-7 LINT=1E-7
+NGATE=5E20 RSH=1082 JS=3.23E-8 JSW=3.23E-8 CJ=6.8E-4 MJ=0.5 PB=0.95
+CJSW=1.26E-10 MJSW=0.5 PBSW=0.95 PCLM=5
+CGSO=3.4E-10 CGDO=3.4E-10 CGBO=5.75E-10)
```

```
.dc V2 0 5 .001 V1 0 5 0.5
```

 

chnology
ring

SUMMARY


All of these examples are for DC characteristics but similar results would be shown for examples that depend on internal capacitors and resistors such as a study of rise-time, fall time, gate delay, oscillators, multi-vibrators, etc.

In general the third generation SPICE models for MOSFETS give better results.

Level=1 models are not good for MOSFETS with L less than 10um.

Large MOSFETS, SUB-MICRON MOSFETS and DEEP SUB MICRON MOSFET models have been introduced.

 Models should be verified by comparing measured ID-VDS, ID-VGS, and Ring Oscillator output with SPICE simulated results.



RING OSCILLATOR, t_d , THEORY



Seven stage ring oscillator
with two output buffers

$$t_d = T / 2 N$$

t_d = gate delay



N = number of stages

T = period of oscillation

  

T = period of oscillation

MEASURED RING OSCILLATOR OUTPUT

 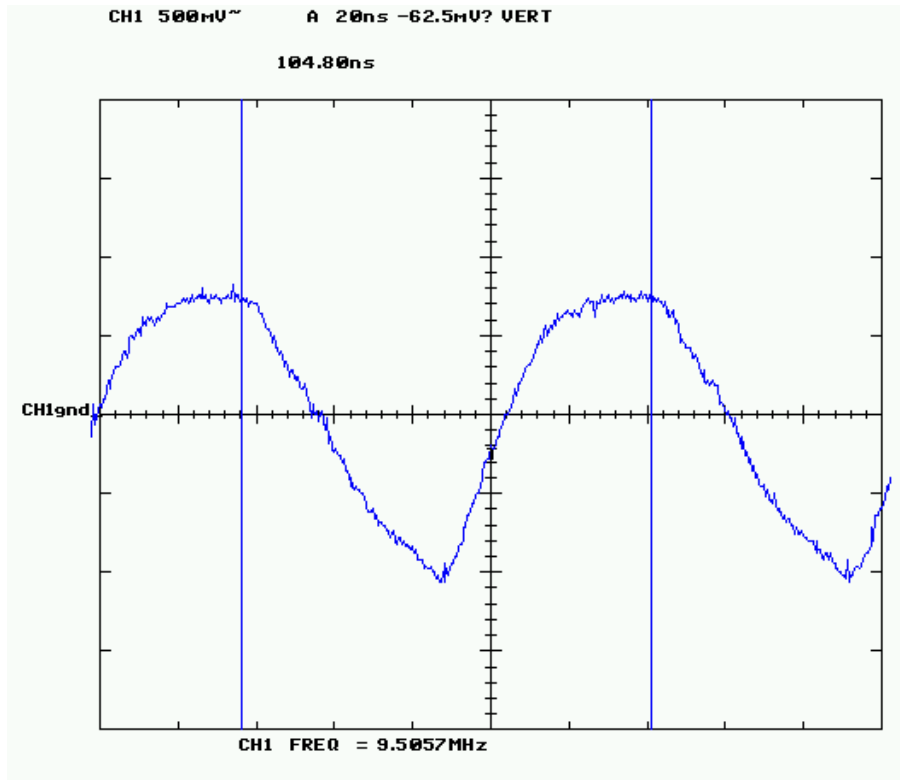

73 Stage Ring at 5V

$$t_d = 104.8\text{ns} / 2(73) = 0.718\text{ ns}$$


AC MODEL FOR MOSFETS

The parameters that effect the AC response of a MOSFET are the resistance and capacitance values.

RS,RS	Source/Drain Series Resistance, ohms
RSH	Sheet Resistance of Drain/Source, ohms
CGSO,CGDO	Zero Bias Gate-Source/Drain Capacitance, F/m of width
CGBO	Zero Bias Gate-Substrate Capacitance, F/m of length
CJ	DS Bottom Junction Capacitance, F/m ²
CJSW	DS Side Wall Junction Capacitance, F/m of perimeter
MJ	Junction Grading Coefficient, 0.5
MJSW	Side Wall Grading Coefficient, 0.5

These are combined with the transistors



L, W	Length and Width
AS,AD	Area of the Source/Drain
PS,PD	Perimeter of the Source/Drain
NRS,NRD	Number of squares Contact to Channel

 

RING OSCILLATOR LAYOUTS

17 Stage Un-buffered Output


L/W=2/30 Buffered Output

 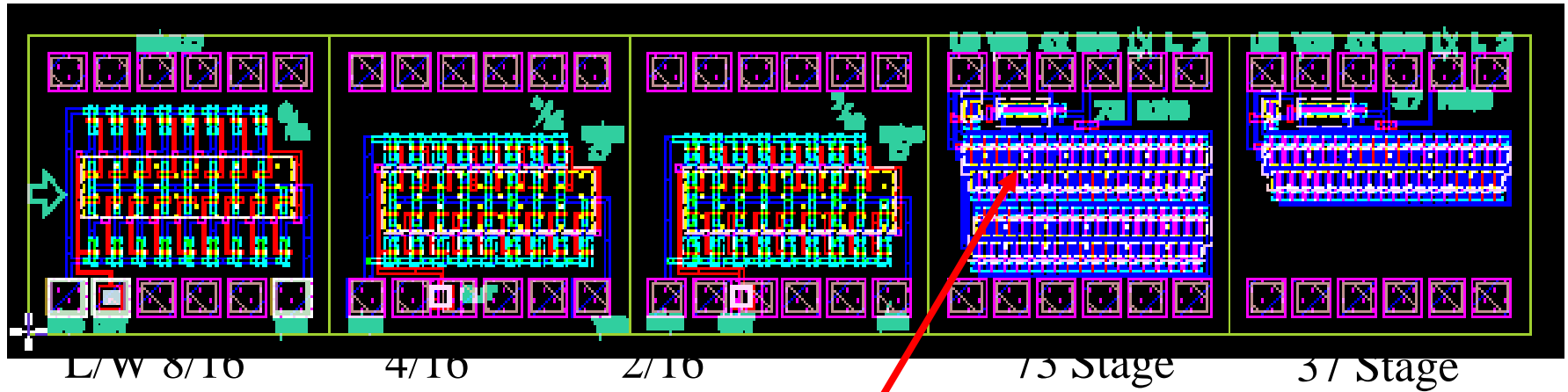


Rochester Institute of Technology
Microelectronics Center

MOSFETS IN THE INVERTER OF 73 RING OSCILLATOR

nmosfet

 

pmosfet

 


73 Stage Ring Oscillator

FIND DIMENSIONS OF THE TRANSISTORS



	NMOS	PMOS
L	2u	2u
W	12u	30u
AD	12u x 12u = 144p	12u x 30u = 360p
AS	12u x 12u = 144p	12u x 30u = 360p
PD	2x(12u + 12u) = 48u	2x(12u + 30u) = 84u
PS	2x(12u + 12u) = 48u	2x(12u + 30u) = 84u
NRS	1	0.3
NRD	1	0.3

73 Stage

 Use Ctrl Click on all NMOS on OrCad Schematic
 Use Ctrl Click on all PMOS on OrCad Schematic
 Then Enter Dimensions



SIMULATED OUTPUT AT 5 VOLTS

 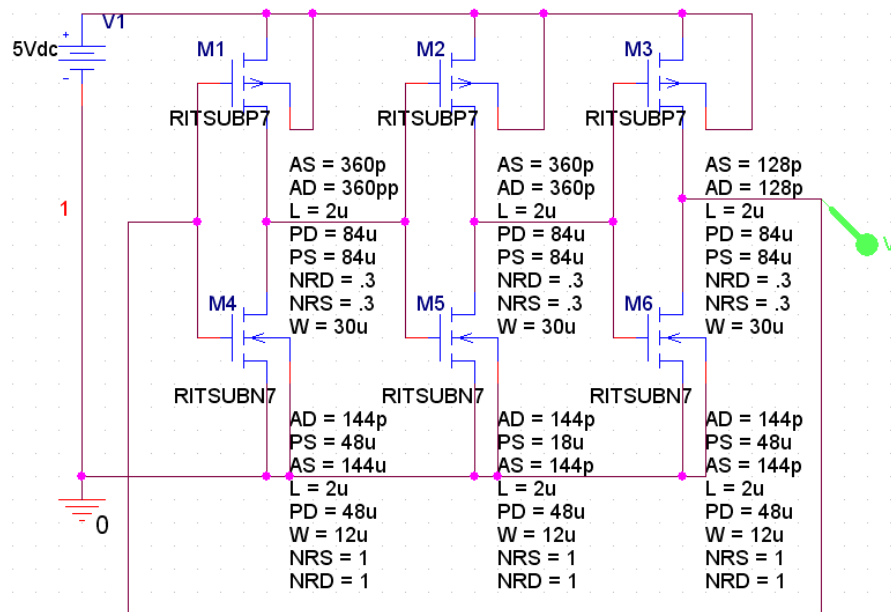

Three Stage Ring Oscillator with Transistor Parameters for 73 Stage Ring Oscillator and Supply of 5 volts

$$t_d = T / 2N = 5.5\text{nsec} / 2 / 3$$

$$t_d = 0.92 \text{ nsec}$$

Measured $t_d = 0.718 \text{ nsec} @ 5 \text{ V}$

CONCLUSION

Since the measured and the simulated gate delays, t_d are close to correct, then the SPICE model must be close to correct. The inverter gate delay depends on the values of the internal capacitors and resistances of the transistor.

Specifically:

RS, RS, RSH

CGSO, CGDO, CGBO

CJ, CJSW

These are combined with the transistors

L, W Length and Width


AS,AD Area of the Source/Drain

PS,PD Perimeter of the Source/Drain

NRS,NRD Number of squares Contact to Channel

REFERENCES

 1. MOSFET Modeling with SPICE, Daniel Foty, 1997, Prentice Hall, ISBN-0-13-227935-5
2. Operation and Modeling of the MOS Transistor, 2nd Edition, Yannis Tsividis, 1999, McGraw-Hill, ISBN-0-07-065523-5
3. UTMOST III Modeling Manual-Vol.1. Ch. 5. From Silvaco International.
4. ATHENA USERS Manual, From Silvaco International.
5. ATLAS USERS Manual, From Silvaco International.
6. Device Electronics for Integrated Circuits, Richard Muller and Theodore Kamins, with Mansun Chan, 3rd Edition, John Wiley, 2003, ISBN 0-471-59398-2
7. ICCAP Manual, Hewlet Packard
8. PSpice Users Guide.



HOMEWORK – INTRO TO MOSFET SPICE MODELS

Do SPICE for one of the following:

1. Inverter gate delay is the time it takes for the output voltage to get to $\frac{1}{2}$ of the supply voltage. Use SPICE to get a value for gate delay for rising and falling output. Let $L=2\mu\text{m}$ and $W=40\mu\text{m}$ for both NMOS and PMOS transistors. State other assumptions. Compare these values to gate delay measured from a ring oscillator.
2. Do a SPICE simulation for the CMOS inverter shown on page 38 and compare to measured VTC and I vs V_{in} .

